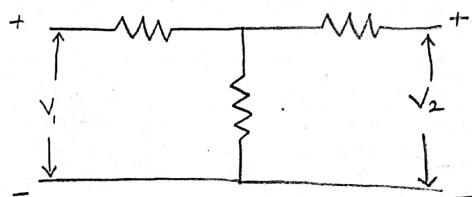


Aim: To determine 'z' & 'Y' parameters of the given two port network.



### Observations

Circuit	<u><math>V_1(V)</math></u>	<u><math>I_1(mA)</math></u>	<u><math>V_2</math></u>	<u><math>I_2</math></u>	<u>Practical Value (<math>\Omega^{-1}</math>)</u>
---------	----------------------------	-----------------------------	-------------------------	-------------------------	---

Input short circuit	0	3.2	10.21	6.6	$Y_{11} = 0.313 \times 10^{-3}$
Output short circuit	10.22	6.5	0	3.2	$Y_{22} = 0.646 \times 10^{-3}$

$$Y_{11} = 0.313 \times 10^{-3}$$

$$Y_{22} = 0.646 \times 10^{-3}$$

$$Y_{12} = 0.636 \times 10^{-3}$$

$$Y_{21} = 0.313 \times 10^{-3}$$

### Calculations

$$V_1 = 10.22V ; V_2 = 0V \Rightarrow I_1 = \frac{10.22}{1.5 \times 10^3} = 6.83 \text{ mA}$$

$$I_2 = 3.4065 \text{ mA}$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{6.83 \times 10^{-3}}{10.22} = 0.666 \times 10^{-3}$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{3.4065 \times 10^{-3}}{10.22} = 0.333 \times 10^{-3}$$

Page No. \_\_\_\_\_  
Date \_\_\_\_\_

### Experiment 1(a)

Aim: To determine Y parameter of the given two port network.

Apparatus: Two port T-network, ammeter, voltmeter, power supply, wires.

for 'y' - parameter,  $I_1$  &  $I_2$  are defined and  $V_1$  &  $V_2$  are expressed in terms of  $I_1$  &  $I_2$ .

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

in matrix form:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Case I:  $Y_{11} = I_1/V_1$  when  $V_2 = 0$  &  $Y_{11}$  is called short circuit input admittance.

Case II:  $Y_{21} = I_2/V_1$  when  $V_2 = 0$  &  $Y_{21}$  is short circuit reverse transfer admittance.

Case III:  $Y_{12} = I_1/V_2$  when  $V_1 = 0$  forward transfer admittance.

### Calculations

$$V_1 = 0V, V_2 = 10.21V$$

$$I_1 = 3.4065 \text{ mA}$$

$$I_2 = 6.813 \text{ mA}$$

$$Y_{12} = \frac{I_1}{V_2} = \frac{3.4065 \times 10^{-3}}{10.21} = 0.33 \times 10^{-3} \Omega^{-1}$$

$$Y_{22} = \frac{I_2}{V_2} = \frac{6.813 \times 10^{-3}}{10.21} = 0.667 \times 10^{-3} \Omega^{-1}$$

### Theoretical Values

$$Y_{11} = 0.66 \times 10^{-3} \Omega^{-1}$$

$$Y_{21} = 0.33 \times 10^{-3} \Omega^{-1}$$

$$Y_{12} = 0.33 \times 10^{-3} \Omega^{-1}$$

$$Y_{22} = 0.667 \times 10^{-3} \Omega^{-1}$$

Page No. \_\_\_\_\_  
Date \_\_\_\_\_

Case 4:  $Y_{22} = I_2/V_2$  when  $V_1=0$  &  $Y_{22}$  is short circuit output admittance.

These parameters are called short circuit admittance parameters.

### Percentage Error

$$Y_{11} = \frac{|0.66 - 0.636| \times 10^{-3}}{0.66 \times 10^{-3}} \times 100 = 4.5\%$$

$$Y_{21} = \frac{|0.33 - 0.31| \times 10^{-3}}{0.33 \times 10^{-3}} \times 100 = 6\%$$

$$Y_{12} = \frac{|0.333 - 0.313| \times 10^{-3}}{0.33 \times 10^{-3}} \times 100 = 6\%$$

$$Y_{22} = \frac{|0.667 - 0.646| \times 10^{-3}}{0.667 \times 10^{-3}} \times 100 = 3.148\%$$

### Result

Theoretical & practical values of  $y$ -parameter have been verified.

## Experiment - I(b)

- Aim - To Calculate & verify z-parameters of two port network.
- Apparatus : Power supply, voltmeter, ammeter, two port T-network.
- Theory

Expressing two port voltage in terms of current

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Case I

When output is open circuit &  $I_2 = 0$   
 $Z_{11} = V_1 / I_1$ ,  $Z_{11}$  is input impedance.

Case II

When output is open circuit &  $I_2 = 0$   
 $Z_{21} = V_2 / I_1$ ,  $Z_{21}$  is forward transfer impedance.

Case III

When output is open ckt. &  $I_1 = 0$   
 $Z_{12} = \frac{V_1}{I_2}$ ,  $Z_{12}$  is reverse transfer impedance.

Case IV

$Z_{22} = \frac{V_2}{I_2}$ ,  $Z_{22}$  is open ckt. impedance.

### Theoretical Values

$$Z_{11} = 2 \text{ k}\Omega$$

$$Z_{21} = 1 \text{ k}\Omega$$

$$Z_{12} = 1 \text{ k}\Omega$$

$$Z_{22} = 2 \text{ k}\Omega$$

### Percentage Error

$$Z_{11} = \frac{2 \times 10^3 - 1.9 \times 10^3}{2 \times 10^3} \times 100 = 5\%$$


$$Z_{21} = \frac{|1 - 0.9| \times 10^3}{1 \times 10^3} \times 100 = 9\%$$


$$Z_{22} = \frac{|2 - 2.05| \times 10^3}{2 \times 10^3} \times 100 = 2.5\%$$

$$Z_{12} = \frac{|1 \times 10^3 - 0.96 \times 10^3|}{1 \times 10^3} \times 100 = 3.02\%$$
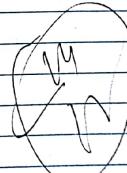
### Result

Theoretical & practical values of z parameter have been verified.



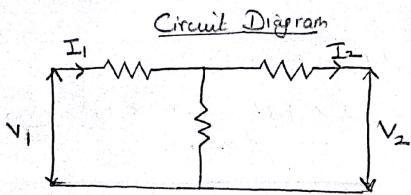

Observations

	V <sub>1</sub>	V <sub>2</sub>	I <sub>1</sub>	I <sub>2</sub>
O/P Port Open Circuit	8.1V	4.01V	4.1mA	0mA
O/P Port Short Circuit	8V	0V	5.1mA	2.7mA

CLASSTIME / Page No.  
Date / /

Experiment 2

Aim: To calculate & verify "ABCD" parameters of a two port network.

Apparatus: Breadboard, resistance, supply, voltmeter, ammeter, wires.

Theory

The ABCD parameters serve to relate the voltage & current at one port to voltage & current at the other port.

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

In matrix form,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

For a given network, these parameters are determined

$$A = \frac{V_1}{V_2}, I_2 = 0$$

A → Reverse voltage gain with output port (open circuited)  
 $C = \frac{I_2}{V_2}, I_2 = 0$

C → Transfer Impedance with output port (open circuited).

### Calculations

$$A = \frac{V_1}{V_2} = \frac{8.1}{4.01} = 2.02$$

$$C = \frac{I_1}{V_2} = \frac{4.1 \times 10^{-3}}{4.02} = 1.02 \times 10^{-3} \text{ at } I_2 = 0$$

$$B = \frac{V_1}{-I_2} = \frac{8}{2.7 \times 10^{-3}} = 2.96 \times 10^3 \text{ at } V_2 = 0$$

$$D = \frac{I_1}{-I_2} = \frac{5.1 \times 10^{-3}}{2.7 \times 10^{-3}} = 1.88 \text{ at } V_2 = 0$$

### Percentage Error

$$A = \frac{|2.02 - 2|}{2} \times 100 = 1\%$$

$$B = \frac{|2.96 \times 10^3 - 3 \times 10^3|}{3 \times 10^3} \times 100 = 1.3\%$$

$$C = \frac{|1.02 \times 10^{-3} - 10^{-3}|}{10^{-3}} \times 100 = 2\%$$

$$D = \frac{|1.88 - 2|}{2} \times 100 = 6\%$$

CLASSTIME / PAGE NO.  
Date / /

$$B = \frac{V_1}{-I_2}, V_2 = 0 \quad D = \frac{I_1}{-I_2}, V_2 = 0$$

B → Transfer Impedance with output port short circuited.

D → Reverse current gain with o/p port short.

These parameters are called transmission parameters.

#### Procedure

1. Make the circuit according to the network.
2. Calculate "ABCD" parameters.
3. Verify the result with theoretical values.

#### Result

The theoretical and experimental values of "ABCD" parameters are calculated & verified.

14  
1

## Experiment 3

- Object: To determine hybrid parameters of two-port network.
- Apparatus: Hybrid Parameters Kit, Multimeter.

### Theory

Expressing 2-port voltage in terms of h-parameters:

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

In matrix form -


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Case I  $h_{11} = \frac{V_1}{I_1}$ , when  $V_2 = 0$  [ $h_{11}$  = input impedance with output short circuit.]

Case II  $h_{21} = \frac{I_2}{V_1}$ , when  $V_2 = 0$  [ $h_{21}$  = forward current gain with output port SC]

Case III  $h_{12} = \frac{V_1}{V_2}$ , when  $I_1 = 0$  [ $h_{12}$  = Rev. voltage gain with I/P port open circuited]

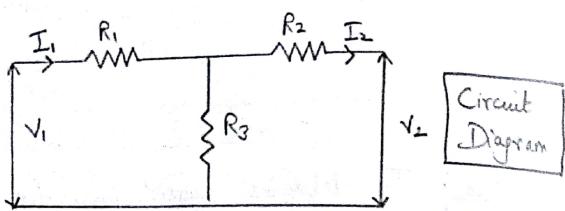Case IV  $h_{22} = \frac{I_2}{V_2}$ , when  $I_1 = 0$  [ $h_{22}$  = o/p admittance with I/P port open circuited]



### Observations

Circuit	$V_1$ (V)	$I_1$ (mA)	$V_2$ (V)	$I_2$ (mA)
I/P Open Circuit	4.93	0	10	4.8
O/P Short Circuit	10	0.3	3.1	0

### Calculations

Input Open Circuit

$$V_1 = 4.82V \quad V_2 = 10V \quad I_2 = 13.5mA$$

$$h_{11} = \frac{4.82}{30} = 0.482, \quad h_{21} = \frac{13.5 \times 10^{-3}}{10} = 1.3 \times 10^{-3}$$

### Output Short Circuit

$$I_1 = 18mA \quad I_2 = 14.5mA \quad V_1 = 10V$$

$$h_{11} = \frac{10}{18 \times 10^{-3}} = 0.55 \times 10^3 \quad h_{21} = \frac{14.5 \times 10^{-3}}{18 \times 10^{-3}} = 0.8$$

### Percentage Error

$$h_{11} = \frac{0.55 \times 10^3 - 0.55 \times 10^3}{0.55 \times 10^3} \times 100 = 0\%$$


$$h_{21} = \frac{|0.8 - 0.75|}{0.8} \times 100 = 3.7\%$$



$$h_{12} = \frac{|0.5 - 0.482|}{0.5} \times 100 = 4\%$$

$$h_{22} = \frac{|1.45 \times 10^{-3} - 1.3 \times 10^{-3}|}{1.45 \times 10^{-3}} \times 100 = 3.3\%$$
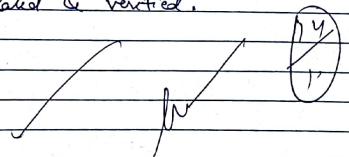
### Result

Theoretical & practical values of  $h$ -parameters have been calculated & verified.



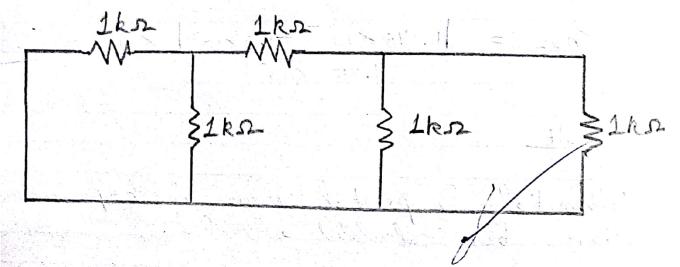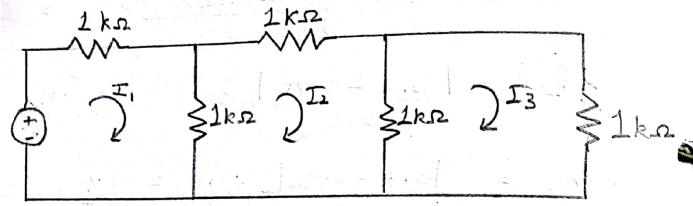

CLASSTIME \_\_\_\_\_  
Page No. \_\_\_\_\_  
Date / /

### Experiment 4

- Aim : Verification of Reciprocity Theorem.
- Apparatus : Experimental Training Board, Connecting wires, ammeter.

#### Theory

Reciprocity Theorem states that a linear network is said to be reciprocal if it remains invariant due to interchange of position of cause & effect in the network.

If we consider two loops A & B of a network N and if an ideal voltage source E in loop A produces a current  $I$  in loop B, then interchanging the positions, if an identical source in loop B produces the same current  $I$  in loop A, the network is said to be reciprocal.

#### Procedure

1. Make the circuit as per circuit disp. in fig. 1.
2. Measure the loop currents  $I_1$ ,  $I_2$  &  $I_3$ .
3. Now Connect the circuit as per fig. 2.
4. Measure the loop currents  $I'_1$ ,  $I'_2$ ,  $I'_3$ .

Observations

Current	Magnitude (mA)
$I_1$	7.5
$I_2$	2.1
$I_3$	1.0
$I_1'$	1.0
$I_2'$	2.1
$I_3'$	7.5

$$I_1 = I_3'$$

$$I_2 = I_2'$$

$$I_3 = I_1'$$

CLASSTIME / Page No.  
Date / /

Observations -

$$I_1 = 7.5 \text{ mA}$$

$$I_1' = 1.0 \text{ mA}$$

$$I_2 = 2.1 \text{ mA}$$

$$I_2' = 2.1 \text{ mA}$$

$$I_3 = 1.0 \text{ mA}$$

$$I_3' = 7.5 \text{ mA}$$


Result

$$\text{Since } I_1 = I_3'$$

$$I_2 = I_2'$$

$$I_3 = I_1'$$

∴ Reciprocity Theorem is verified.

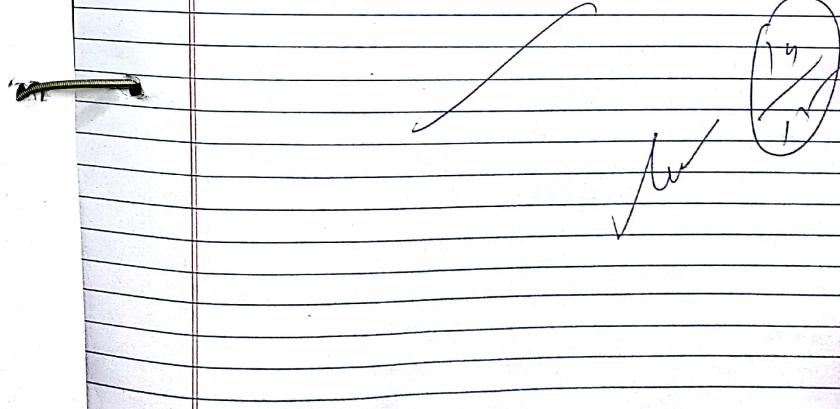

## Experiment - 5

- Aim : Determination of ABCD parameters for a cascade connection.
- Apparatus : Breadboard, resistance, power supply, wires, multimeter.
- Theory : The transmission parameters serve to relate the voltage & current at one port to voltage & current at the other port.

In equation form,  $V_1 = AV_2 - BI_1$ ,  
 $I_1 = CV_2 - DI_1$ ,

In matrix form,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

In two port networks, they are said to be connected in cascade. The output port of the first become the input port of the second.

For the network No. the transmission parameters equation are -

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

for the network No., the transmission parameters equations are,

Observation Tab 1c  
(1) For a circuit  $N_a$ ,

	$V_{1a}$	$V_{2a}$	$I_{1a}$ (mA)	$-I_{2a}$
S/C	10.05	5V	5.0	0
O/C	10.05	0	6.4	3.2

(2) For circuit  $N_b$

	$V_{1b}$	$V_{2b}$	$I_{1b}$ (mA)	$I_{2b}$ (mA)
S/C	10.05	0	6.3	3.2
O/C	10.05	5	5.6	0

(3) For a cascade

	$V_1$	$V_2$	$I_1$	$I_2$	$I_3$	$I_4$
S/C	10.05	0	5.6	0.4	0.817	
O/C	10.05	1.432	5.5	0		

CLASSTIME / Page No.  
Date / /

$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

For the cascade connection as shown in the fig  
 $I = I_{1a}, -I_{2a} = I_{1b}, I_2 = I_{2b}, V_1 = V_{1a}, V_2 = V_{2b}$   
 The overall transmission parameters of the combined network  $N_a$  &  $N_b$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$


$$\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

Result

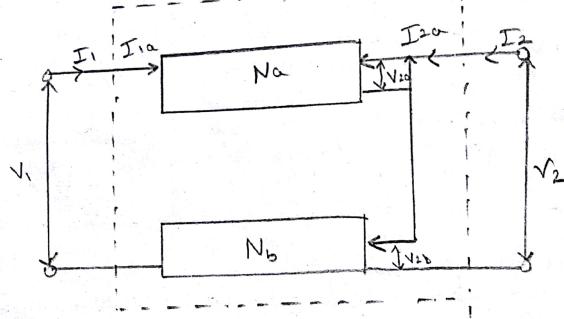The cascade connection parameters have been verified.



For  $N_a = N_b$

	$V_1$	$V_2$	$I_1$	$I_2$
Port 1-1' open	12	5.96	6.4	0
Port 2-2' open	5.98	12	0	6.4

For Series

	$V_1$	$V_2$	$I_1$	$I_2$
Port 1-1' open	12	5.99	2.99	0
Port 2-2' open	6.03	12	0	3.006

CLASSTIME / Page No.  
Date / /

Experiment - 6

- Aim : Determination of  $Z$ -parameters for series-series connection.
- Apparatus : Breadboard, resistance, power supply, multimeter.
- Theory  
A given two port network with some degree of complexity can be built up from simpler two port networks whose ports are inter-connected in certain ways. It's so much easier to design simple blocks & to interconnect them to design a complex network in one piece. They are basically connected in : series-series, series-parallel, parallel-series, parallel-parallel.

$Z$ -parameters for network A

$$\begin{bmatrix} V_1 \\ V_{2a} \end{bmatrix} = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix}$$

$Z$ -parameters for network B

$$\begin{bmatrix} V_{1b} \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

The two networks are in series.

### Calculations

For  $N_a = N_b$

$$Z_{11b} = Z_{11a} = \frac{V_{1a}}{I_{1a}} = 1875$$

$$Z_{12b} = \frac{V_{2a}}{I_{1a}} = 931 \quad I_{2a} = 0$$

$$Z_{22b} = Z_{22a} = \frac{V_{2a}}{I_{2a}} = 1875 \quad I_{1a} = 0$$

$$Z_{21b} = Z_{12a} = \frac{V_{1a}}{I_{2a}} = 934 \quad I_{1a} = 0$$

For  $Z$ -series

$$Z_{11} = V_1/I_1 = \frac{12}{2.992 \times 10^{-3}} = 4010 \quad I_2 = 0$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{5.99}{2.99 \times 10^{-3}} = 2002 \quad I_2 = 0$$

$$Z_{12} = V_1/I_2 = \frac{6.03}{3.006 \times 10^{-3}} = 2005 \quad I_1 = 0$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{12}{3.006 \times 10^{-3}} = 3992 \quad I_1 = 0$$

$I_1 = I_{12} = I_{1b}$ $V_1 = V_{1a} + V_{1b}$ $I_2 = I_{ca} = I_{2b}$ $V_2 = V_{2a} + V_{2b}$	CLASSTIME / Page No. Date / /
--	----------------------------------

Now,  $V_1 = V_{1a} + V_{1b}$   
 $= (Z_{11a} + Z_{11b})I_1 + (Z_{12a} + Z_{12b})I_2$

$\& V_2 = (Z_{21a} + Z_{21b})I_1 + (Z_{22a} + Z_{22b})I_2$

• Procedure

1. Make the circuit acc. to the network ( $N_a = N_b$ )
2. Calculate  $Z$ -param. of block  $N_a$  &  $N_b$ .
3. Connect  $N_a$  &  $N_b$  in series.
4. Find  $Z$  parameters of the series block.

• Result

The theoretical & practical values of  $Z$ -parameters for a series-series connection & hence calculated & verified.

Experiment 17

- Aim : To determine  $\gamma$ -parameters of a given parallel connection.

Apparatus : Breadboard, Power supply ; resistance, multimeter.

Theory  
Parallel Combination

$\gamma$ -parameters equations for network  $N_a$

$$\begin{aligned} I_{1a} &= Y_{11a} V_{1a} + Y_{12a} V_{2a} \\ I_{2a} &= Y_{21a} V_{1a} + Y_{22a} V_{2a} \end{aligned}$$

$\gamma$ -parameter equation for network  $N_b$ ,

$$\begin{aligned} I_{1b} &= Y_{11b} V_{1b} + Y_{12b} V_{2b} \\ I_{2b} &= Y_{21b} V_{1b} + Y_{22b} V_{2b} \end{aligned}$$

for parallel connection

$$V_1 = V_{1a} = V_{1b}$$


$$V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b}$$

$$I_2 = I_{2a} = I_{2b}$$

By combining these equations,

$$I_1 = I_{1a} + I_{1b}$$

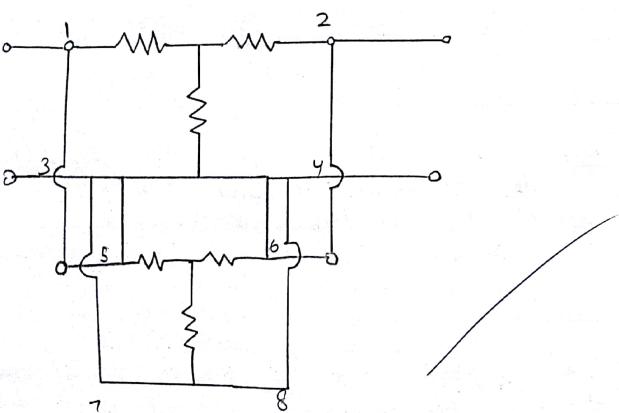

Observation Table

For circuit Na

$V_{1a}$	$V_{2a}$	$I_{1a}$	$I_{2a}$
12	0	8.5	4.2
0	12	4.2	8.5

For circuit Nb

$V_{1b}$	$V_{2b}$	$I_{1b}$	$I_{2b}$
12	0	16.97	8.51
0	12	8.51	16.97

For parallel combination,

$V_1$	$V_2$	$I_1$	$I_2$
0	5.03V	1.608	4.7
5.01V	0	4.7	1.6

Calculations

$$\text{For Na, } Y_{11a} = I_{1a}/V_{1a} \quad [V_{2a}=0]$$

$$Y_{12a} = I_{1a}/V_{2a} \quad [V_{1a}=0]$$

$$Y_{21a} = I_{2a}/V_{1a} \quad [V_{2a}=0]$$

$$Y_{22a} = I_{2a}/V_{2a} \quad [V_{1a}=0]$$

$$\text{For Nb, } Y_{11b} = I_{1b}/V_{1b} \quad [V_{2b}=0]$$

$$Y_{12b} = I_{1b}/V_{2b} \quad [V_{1b}=0]$$

$$Y_{21b} = I_{2b}/V_{1b} \quad [V_{2b}=0]$$

$$Y_{22b} = I_{2b}/V_{2b} \quad [V_{1b}=0]$$

For parallel circuit,

$$Y_{11} = I_1/V_1 \quad [V_2=0]$$

$$Y_{12} = I_1/V_2 \quad [V_1=0]$$

$$Y_{21} = I_2/V_1 \quad [V_2=0]$$

$$Y_{22} = I_2/V_2 \quad [V_1=0]$$

Telco Dt.: Pg.:

$$= (Y_{11a} V_{1a} + Y_{12a} V_{2a}) + (Y_{11b} V_{1b} + Y_{12b} V_{2b})$$

$$= (Y_{11a} + Y_{11b}) V_1 + (Y_{12a} + Y_{12b}) V_2$$

$$\text{And, } I_2 = I_{2a} + I_{2b}$$

$$= (Y_{21a} V_{1a} + Y_{22a} V_{2a}) + (Y_{21b} V_{1b} + Y_{22b} V_{2b})$$

$$= (Y_{21a} + Y_{21b}) V_1 + (Y_{22a} + Y_{22b}) V_2$$

In matrix form,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\text{where, } Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

where result may be generalized for any no. of two port network connected in parallel. Connected two port network is simply the sum of Y-parameters of each individual two port network connected in parallel.

Procedure

1.


Make the circuit according to the network.

2.

Find Y-Parameters of circuit Ne.

*telco*  $\frac{Dt.:}{Pg.:}$

3. Find Y - Parameters of circuit N<sub>b</sub>.
4. Connected the circuit N<sub>a</sub> & N<sub>b</sub> in parallel  
& find Y - parameters for the parallel connection.

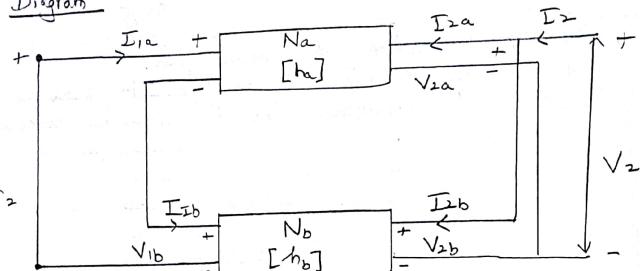Diagram

S - P connection of two port network

Observations

Circuit	$V_1(V_2)$	$V_2(V_1)$	$I_1(mA)$	$I_2(mA)$
$N_a = N_b$	4.93 10	3.0 3.1	0 6.3	4.8 0
Series	10.01	20.1	0	9.6
Parallel	19.7	6.3	6.3	0

Telco Pg. Dr.

Experiment &

Aim: To design series - parallel & determine hybrid parameters for the given two - port network

Equipment: Hybrid parameters kits, multimeters.

Theory: It given two - port network with some degree of complexity can be built up from simpler two - port network whose ports are interconnected in certain way. It is much easier to design a complex network in one piece. They are connected in s - s, s - p, p - s, p - p connection. The s - p connections are used to determine the hybrid parameters. The two port networks are said to be connected in s - p if the input ports are connected in series while the output ports are connected in parallel

$$V_1 = V_{1a} + V_{1b}$$

$$I_1 = I_{1a} + I_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$I_2 = I_{2a} + I_{2b}$$

For network  $N_a$

$$V_{1a} = h_{11} I_{1a} + h_{12} V_{2a}$$

$$I_{2a} = h_{21} I_{1a} + h_{22} V_{2a}$$

### Calculations

For  $N_a = N_b$ ,

$$h_{11} = \frac{V_1}{I_1} = \frac{10}{6.3 \times 10^{-3}} = 1.58 \times 10^{-3} \Omega$$

$$h_{12} = \frac{I_2}{I_1} = \frac{4.93}{3.1} = 0.49$$

$$h_{21} = \frac{V_1}{V_2} = \frac{4.03}{10} = 0.403$$

$$h_{22} = \frac{I_2}{V_2} = \frac{4.8 \times 10^{-3}}{10} = 0.48 \times 10^{-3} \Omega$$

For Series-parallel Connected Network,

$$h_{11} = \frac{V_1}{I_1} = \frac{19.7}{6.93 \times 10^{-3}} = 3.129 \times 10^{-3} \Omega$$

$$h_{12} = \frac{I_2}{I_1} = \frac{10.01 \times 10^{-3}}{6.3 \times 10^{-3}} = 1.25$$

$$h_{21} = \frac{V_1}{V_2} = \frac{10.09}{19.7} = 1.091$$

$$h_{22} = \frac{I_2}{V_2} = \frac{9.6 \times 10^{-3}}{20.1} = 1.12 \times 10^{-3} \Omega$$

telco Dt.: Pg.:

For network  $N_b$ ,

$$V_{1b} = h_{11b} I_{1b} + h_{12b} V_{2b}$$

$$I_{2b} = h_{21b} I_{1b} + h_{22b} V_{2b}$$

As per connection, the final parameters can be evaluated as -

$$h_{11} = h_{11a} + h_{11b}$$

$$h_{12} = h_{12a} + h_{12b}$$

$$h_{21} = h_{21a} + h_{21b}$$

$$h_{22} = h_{22a} + h_{22b}$$

### Procedure

1. Make the circuit according to the network.
2. Calculate "h" parameters using the circuit  $N_a$ .
3. Calculate "h" parameters using the circuit  $N_b$ .
4. Verify the result with the theoretical values.

### Result


Hence, the theoretical & experimental values of "h" parameters are calculated & verified.

14  
14  
14
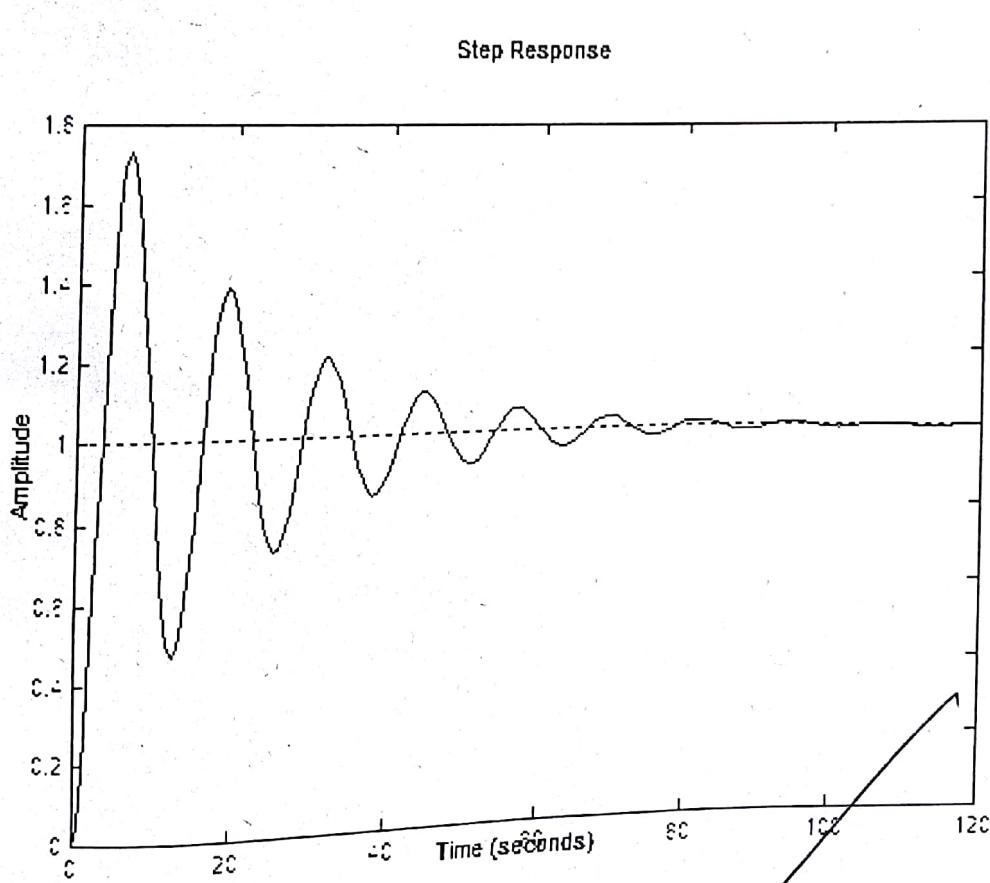
# EXPERIMENT 9

AIM : Transient response of RLC series circuit.

```
>> R=0.1;  
>> R=0.2;  
>> L=2;  
>> C=2;  
>> NEM=[1];  
>> DEN=[L*C,R*C,1];  
>> SYS=tf(NEM,DEN);  
>> step(SYS)
```



RESULT- R, L, C circuit experiment was successfully performed.