

UNIT - INumber System and CodesNUMBER SYSTEMS

Decimal → A decimal code consists of 10 numbers (from 0-9). Each no is represented using these 10 digits.

A decimal no represented as
 $(132)_{10} = (1 \times 10^2) + (3 \times 10^1) + (2 \times 10^0) = 132$

⇒ Numbers used are in decimal code.

Binary → A binary code consists of 2 no. (0 and 1). Each no. is represented using these 2 digits.

A binary number can be represented as

$$(10101)_2 = 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ = 16 + 4 + 1 = 21$$

Decimal to Binary Conversion

- ① Repeatedly divide the no by 2 and write the remi on the right.
- ② start writing the no from bottom to the top including the last quotient.

example

example

$$\begin{array}{r}
 & | 8 \\
 2 | & 10 \\
 & | 5 \\
 2 | & 2 \\
 & | 1
 \end{array}$$

reminders

last quo.

∴ binary no is

$$(21)_{10} = (10101)_2$$

last quo. reminders in reverse order.

Octal → An octal code consists of 8 numbers (0 to 7) which are used to represent another no. in decimal code.

An octal no can be represented as

$$\begin{aligned}
 (327)_8 &= 3 \times 8^2 + 2 \times 8^1 + 7 \times 8^0 \\
 &= 192 + 16 + 7 \\
 &= 215
 \end{aligned}$$

Decimal

Conversion to Octal from Binary.

Divide by 8 instead of 2.

$$\begin{array}{r}
 & | 215 \\
 8 | & 26 \\
 & | 3
 \end{array}$$

7
2

∴ octal no is

$$(215)_{10} = (327)_8$$

Hexadecimal → A hexadecimal code consists of 16 numbers (0 to 15). 0 to 9 are represented by number digits whereas 10 to 15 are represented by alphabets.

0 → 0 A hexadecimal code can be
1 → 1 represented as.

2 → 2

3 → 3

4 → 4

5 → 5

6 → 6

7 → 7

8 → 8

9 → 9

10 → A

11 → B

12 → C

13 → D

14 → E

15 → F

$$(BA3)_{10} = 11 \times 16^2 + 10 \times 16^1 + 3 \times 16^0 \\ = 2816 + 160 + 3 \\ = 2979$$

Decimal

Conversion from binary.

Divide by 16 and follow the same steps.

$$\begin{array}{r} 16 \mid 2979 & \rightarrow \\ 16 \mid 186 & \rightarrow 3 \\ \hline 11 & \end{array}$$

Replace 11 and 10 by their alphabet codes.

$$11 \rightarrow B, 10 \rightarrow A$$

$$\therefore (2979)_{10} = (BA3)_{16}$$

Conversion from Binary to Hexa

01010101

$\downarrow \quad \downarrow$

5 5

- ① Make pairs of 4.
- ② Convert them to decimal
- ③ Write the corresponding hexa decimal codes.

$$(55)_{16} = (01010101)_2$$

For Octa Hexa to Binary, Follow the reverse.

$$(55)_{16} \Rightarrow (01010101)_2$$

\swarrow (0101) \searrow (0101)

* For Binary to Octa
Make pairs of 3.

example

$$(0\underset{5}{|}1\underset{2}{|}0\underset{5}{|}10101)_2 = (525)_{10}$$

For (Octa to Hexa) or (Hexa to Octa),
Direct conversion is not possible.

∴ either Octa \rightarrow Binary \rightarrow Hexa
or Octa \rightarrow Decimal \rightarrow Hexa
is followed.

example $\rightarrow (BA3)_{16} = (?)_8$

$$(BA3)_{16} = (2979)_{10} \quad (\text{solved earlier})$$

$$\begin{array}{r} 8 | 2979 \\ 8 | 372 \quad 3 \\ 8 | 46 \quad 4 \\ 8 | 5 \quad 6 \end{array} = (5643)_8$$

$$\therefore (BA3)_{16} = (5643)_8$$

CODES

BCD code \rightarrow BCD stands for Binary coded decimal.

It is a 4 bit code and each bit is weighed 8, 4, 2, 1 resp.

$$\begin{matrix} & B_4 & B_3 & B_2 & B_1 \\ 8 & \swarrow & \downarrow & \downarrow & \searrow \\ & 1 & 2 & 4 & 8 \end{matrix}$$

Decimal value of $B_4 B_3 B_2 B_1$ is $(B_4 \times 8 + B_3 \times 4 + B_2 \times 2 + B_1 \times 1)$

The code can be written as.

Decimal BCD code.

0 0000

1 0001

2 0010

3 0011

4 0100

5 0101

6 0110

7 0111

8	1000
9	1001

Excess 3-Code → An ~~also~~ Excess 3-Code has no particular weight assignment. It is derived by adding 3 to the B.C.D code.

Decimal	Excess - 3	
0	0011	$(0+3=3)$
1	0100	$(1+3=4)$
2	0101	$(1+3=5)$
3	0110	$(3+3=6)$
4	0111	$(4+3=7)$
5	1000	$(5+3=8)$
6	1001	$(6+3=9)$
7	1010	$(7+3=10)$
8	1011	$(8+3=11)$
9	1100	$(9+3=12)$

Difference in Binary conversion and Binary Codes.

During conversion the no. is directly converted to binary

$(21)_{10} = (10101)_2$ is represented by 5 bits in binary conversion, whereas if we use a code & is converted separately and 1 is done separately resulting in an 8 bit code.

BCD

$$\begin{array}{c} \swarrow \quad \searrow \\ 0010 \quad 0001 \end{array} \rightarrow (0010\ 0001)_{BCD}$$

Excess -3

$$\begin{array}{c} \swarrow \quad \searrow \\ 0101 \quad 0100 \end{array} \rightarrow (0101\ 0100)_{\text{excess-3}}$$

Gray Code → A gray code changes by only one bit from its preceding number. Due to this, it is preferred in cases where analog data is converted into discrete data.

<u>Gray</u>	<u>Decimal</u>
0000	0
0001	1
0011	2
0010	3
0110	4
0111	5
0101	6
0100	7
1100	8
1101	9
1111	10
1110	11
1010	12
1011	13
1001	14
1000	15

Sort of a mirror after every 2ⁿ being the no. of bit

ASCII Code → ASCII code is an alphanumeric code which represents upper/lower case letters, numbers and special characters using a 7-bit code.

ASCII → American Standard Code for Information Interchange

EBCDIC → EBCDIC is an alphanumeric code which represents upper/lower case letters, numbers and special characters using a 8-bit code.

EBCDIC → Extended Binary Coded Decimal (BCD) Interchange Code.

— X — X —

Switching Theory

Postulates of Boolean Algebra (Huntington's Postulates)

① Closure → The end result after any operation belongs to the same set as the operands.

$$a * b = c$$

if $a, b \in B$ then $c \in B$.

here $B = \{0, 1\}$
and * is any binary operation

② Identity → There exists an element which when operated with x , such that $x \in B$, gives x .

$$x \cdot 1 = x \quad \text{and} \quad x + 0 = x$$

③ Distributive →

$$\begin{aligned} x \cdot (y + z) &= x \cdot y + x \cdot z \\ x + yz &= (x + y)(x + z) \end{aligned}$$

④ Commutative →

$$x \cdot y = y \cdot x$$

$$x + y = y + x$$

⑤ Inverse → For every element x there exists an element x' (or \bar{x}) such that $x * x' = e$ where e is the identity element.

$$x \cdot \bar{x} = 0 \quad x + \bar{x} = 1$$

⑥ There exist atleast 2 elements x & y such that $x, y \in B$ and $x \neq y$.

Theorems of Boolean Algebra

I

$$x \cdot x = x$$

$$x + x = x$$

II

$$x \cdot 0 = 0$$

$$x + 1 = 1$$

III

Associative

$$(x \cdot y) \cdot z = x \cdot (y \cdot z)$$

$$(x + y) + z = x + (y + z)$$

IV

Involution

$$(x')' = x$$

V

DeMorgan's Theorem

$$(A + B)' = A'B'$$

$$(AB)' = A'B'$$

Proof.

$$\text{Let } (A + B) = Z$$

$$Z' = (A + B)'$$

$$Z \cdot Z' = 0 \text{ and } Z + Z' = 1$$

$$\text{If } (A + B) \cdot A'B' = 0 \text{ and } (A + B) + A'B' = 1$$

$$\text{Then, } A'B' = (A + B)'$$

$$\begin{aligned} (A + B) \cdot A'B' &= AA'B' + BA'B' \\ &= (AA')B' + A'(BB') \quad (\text{associative}) \\ &= 0 \cdot B' + A' \cdot 0 \quad (x \cdot 0 = 0) \\ &= 0 + 0 \\ &= 0 \end{aligned}$$

$$(A + B) + A'B' = \cancel{(A \cdot A)} \cancel{+ A \cdot B} \cancel{+ A' \cdot B} \cancel{+ A' \cdot A}$$

$$\begin{aligned} &= (A + B)(1) + A'B' \quad [x \cdot 1 = x] \\ &= (A + B)(A' + A) + A'B' \quad [A' + A = 1] \\ &\quad \cancel{(A \cdot A)} \cancel{+ A \cdot B} \cancel{+ A' \cdot B} \cancel{+ A' \cdot A} \end{aligned}$$

$$\begin{aligned} &= A'A + A + A'B + A'B' \\ &= 0 + A + A'(B + B') \quad [x \cdot x' = 0] \\ &= A + A'(1) \quad [B + B' = 1] \\ &= A + A' = 1 \end{aligned}$$

Hence,
 $(A+B)' = A'B'$

Absorption

$$\text{VI} \quad X + XY = X$$

$$X(X+Y) = X$$

$$\text{VII} \quad X + \bar{X}Y = Y + Y$$

Switching Functions

A switching function (boolean function) is formed by boolean variables, parenthesis and boolean operators AND, OR and NOT.

A Boolean function can be represented in an algebraic form and can also be represented using a truth table.

A truth table consists of all the possible inputs/outputs in a function.

example $\rightarrow F = XY + Z'$

all possible inputs
(can only have values 0 or 1)

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Each variable of a Boolean Function is known as a literal.

Switching Functions

Canonical Form

Every term of a canonical form contains all the literals. It is the form which is derived directly from a truth table.

Standard Form

This form consists of the simplified expression and is used to implement circuits of the switching functions.

Canonical Form

Maxterms → All the possible outcomes when the literals are connected using an OR gate are known as maxterms or standard sums.

Min terms → all the possible outcomes when the literals are connected using an AND gate are known as minterms or standard products.

	x	y	z	MAXTERMS	MINTERMS
0	0	0	0	$M_0 = x + y + z$	$m_0 = x'y'z'$
1	0	0	1	$M_1 = x + y + z'$	$m_1 = x'y'z$
2	0	1	0	$M_2 = x + y' + z$	$m_2 = x'y z'$
3	0	1	1	$M_3 = x + y' + z'$	$m_3 = x'y z$
4	1	0	0	$M_4 = x' + y + z$	$m_4 = x y' z'$
5	1	0	1	$M_5 = x' + y + z'$	$m_5 = x y' z$
6	1	1	0	$M_6 = x' + y' + z$	$m_6 = x y z'$
7	1	1	1	$M_7 = x' + y' + z'$	$m_7 = x y z$

* To write maxterms

put x if $x=0$ and x' if $x=1$
and use '+' b/w literals.

* To write minterms

put x' if $x=0$ and x if $x=1$
and use '.' b/w literals.

Canonical POS \rightarrow Product of ~~max~~ maxterm

$$F = \pi(0, 1, 2, 9, 13)$$

$$= M_0 \cdot M_1 \cdot M_2 \cdot M_9 \cdot M_{13}$$

To find Can. POS from Truth table,
write all the maxterms whose
output is 0.

Canonical SOP \rightarrow Sum of minterms

$$F = \Sigma(1, 3, 9, 11) = m_1 + m_3 + m_9 + m_{11}$$

To find Can. SOP write all the minterms with output 1.

example

	X	Y	Z
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	0

$$Z = m_0 + m_2 = x'y' + x'y$$

$$Z = M_1 \cdot M_3 = (x+y)(x'+y')$$

$$Z = \Sigma(0, 2) = \Pi(1, 3)$$

SOP and POS forms are complementary to each other.
i.e. mō present in one are absent in another.

Standard Form

Standard Form can be generated from Cano. form by Simplification
There are 3-methods of Simplification

- (1) ~~Boolean Algebraic~~ (long method but still used in some cases).
- (2) K-Maps (used in most ques)
- (3) Quine Mc-Clusky. (1 mark Ques for sure)

Algebraic \rightarrow Simplification using Theorems.

example

$$\begin{aligned} F &= zxy + x'z'y' + x'zy + z'xy \\ &= xy(z + z') + zx'(y' + y) \\ &= ny + zx' \quad [x + x' = 1] \end{aligned}$$

* Simplification can be done from non-canonical forms to standard forms as well.

example

$$\begin{aligned} F &= xyz + x'y + xy'z' \\ &= ny(z + z') + x'y \quad [n + n' = 1] \\ &= ny \cdot (1) + x'y \\ &= xy + x'y = y(x + x') \quad [x + x' = 1] \\ &= y \end{aligned}$$

K-Map:

A K-Map represents the ~~or~~ function in a combination of squares where each square represents a maxterm/minterm.

SOPs using K-Maps no of sq = a^n
 where n is no of variables.

2 Variable

$$F(A, B) = \Sigma(1, 2, 3)$$

Step I Write the variables in a K-Map.

$F =$	A	B	\bar{B}	1
	\bar{A}			0
	A			1, 2, 3

Step II Put 1 in places of the minterms specified in the ques.

Step III

Make Pairs, Quads or Octants possible. No, no should be left behind. And Octants are first preference followed by Quads followed by pairs.

In the above ques

Pairs (1, 3) and (2, 3)
are possible.

Step IV

For the ans. consider the literals which are similar for a pair/quad/octant and write them with a '+' sign.

(1, 3) have B in common

(2, 3) have A in common

$$\therefore F = B + A$$

example

$$F(x, y) = \Sigma(0, 2, 3)$$

$$F = \begin{array}{c} \bar{x} \\ x \end{array} \boxed{\begin{array}{|c|c|} \hline 1 & 0 \\ \hline 1 & 3 \\ \hline \end{array}}$$

$$F = \bar{y} + x$$

3-variable

$$F(A, B, C) = \Sigma(0, 3, 4, 6, 7)$$

Rest rules are similar just keep in mind the pattern of K-map.

We don't follow rule. We follow rule. i.e. the 4th column's are interchanged.

		BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	A	\bar{A}	10	1	13	2
	A	A	14	5	17	16

$$F = \bar{B}\bar{C} + BC + AB$$

ex $F = \Sigma(0, 1, 2, 4, 6)$

Quadruplets
Octants formed
can be formed
at corners
as shown

		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	A	10	11	3	12
	A	14	5	7	16

Quad (0, 2, 4, 6)
Pair (0, 1)

$$F = \bar{C} + \bar{A}\bar{B}$$

4-variable

$$F = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

Octant (0, 1, 4, 5, 8, 9, 12, 13)

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{x}$	10	1	3	12
$\bar{w}x$	11	1	7	16
$w\bar{x}$	12	1	13	15 14
wx	18	19	11	10

Quad (0, 2, 4, 6)

Quad (4, 6, 12, 14)

$$F = \bar{Y} + \bar{W}\bar{Z} + X\bar{Z}$$

A quad/octant/pair formed should have at least one element which is not a part of any other quad/pair/octant.

5-variable

Draw two 4 variable K-Maps side by side and assume them to be overlapping while considering pairs/quads/octants.

$$F(A, B, C, D, E) = \Sigma (0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 29, 27, 29, 31).$$

	$\bar{D}\bar{E}$	$\bar{D}E$	DE	$D\bar{E}$		$\bar{D}\bar{E}$	$\bar{D}E$	DE	$D\bar{E}$
$\bar{B}\bar{C}$	10	1	3	12	$\bar{B}\bar{C}$	16	17	19	18
$\bar{B}C$	14	5	7	16	$B\bar{C}$	20	21	23	22
$B\bar{C}$	12	13	15	14	BC	28	29	31	30
BC	8	19	11	10	$B\bar{C}$	24	25	27	26

Oct (9, 11, 13, 15, 25, 27, 29, 31)

Quad (0, 2, 4, 6)

Quad (17, 21, 25, 27)

$$F = BE + \bar{B}\bar{E}\bar{A} + A\bar{D}\bar{E}$$

Calculating POS using k-maps

- ① Replace F by F' and plot 0, instead of 1's
 - ② Take complement of the ans.
- example

$$F = \kappa(0, 1, 2, 3, 4, 6, 12) \\ (A, B, C, D)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	0, 1	0, 3	0, 2	0, 5
$\bar{A}B$	0, 4	5	7	6
$A\bar{B}$	0, 12	13	15	14
AB	8	9	11	10

Quad (0, 1, 2, 3); (0, 2, 4, 6)
Pair (4, 12)

$$F' = \bar{A}\bar{B} + \bar{A}\bar{D} + B\bar{C}\bar{D}$$

$$F = (\bar{A}\bar{B} + \bar{A}\bar{D} + B\bar{C}\bar{D})'$$

$$= (\bar{A}\bar{B})' \cdot (\bar{A}\bar{D})' \cdot (B\bar{C}\bar{D})' \quad [De-morgan]$$

$$F = (A+B) \cdot (A+D) \cdot (\bar{B} + C + D)$$

(De moorgans)

Don't Care Elements:

These are the elements which don't have a fixed output in a function. We don't consider this case as its value doesn't effect the output. It can either be 0 or 1.

They are represented by a X in K-map and are only considered if they help reducing the exp. or else are ignored.

example $F(w,yx,y,z) = \sum(1,3,7,11,15) + d(0,2,5)$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz	
$w\bar{x}$	x_0	1	1	1	x_2
wx	4	x_5	1	6	
$w\bar{x}$	12	12	115	14	
wx	8	9	11	10	

Quad (1, 3, 5, 7)

Quad (3, 7, 11, 15)

(only considered 5 ; 0, 2 were not req.)

$$F = YZ + \bar{W}Z$$

~~Imp.~~

Quine - McClusky

Can be used for simplification of func with more than 5-variables

* If the ques asks for Prime implicants / essential Prime implicants always use this method.

Explanation with example

$$F(A, B, C, D) = \Sigma(1, 3, 5, 7, 9, 10, 11)$$

+

$$d \Sigma(12, 13, 14, 15)$$

Step

Write each no in decimal and binary form (include dont-care elements as well).

Decimal	Binary
1	A B C D 0 0 0 1
3	0 0 1 1
5	0 1 0 1
7	0 1 1 1
9	1 0 0 1
10	1 0 1 0
11	1 0 1 1
12	1 1 0 0
13	1 1 0 1
14	1 1 0 0
15	1 1 1 1

Step 2 Make a table acc. to no. of 1s.

no. of 1s	minterms	ABCD
1	1	0001 ✓
2	3 5 9 10 12	0011 ✓ 0101 ✓ 1001 ✓ 1010 ✓ 1100 ✓
3	7 11 13 14	0111 ✓ 1011 ✓ 1101 ✓ 1110 ✓
4	15	1111 ✓

Step 3 Make Pairs by comparing two adjacent rows and replace unlike elements with a -.

no. of 1s	minterm	ABCD
1	1 - 3	00 - 1 ✓
	1 - 5	0 - 01 ✓
	1 - 9	- 001
2	3 - 7	0 - 11 ✓
	3 - 11	- 011 ✓
	5 - 7	0 1 - 1 ✓
	5 - 13	- 101 ✓
	9 - 11	10 - 1 ✓
	9 - 13	1 - 01 ✓
	10 - 11	10 1 - 1 ✓

10-14	1-10 ✓
12-13	110- ~
12-14	11-0 ↗
3	2-15
11-15	-111 ✓
13-15	1-11 ✓
14-15	11-1 ✓
	111- ✕

~~Step 4~~ Compare adjacent rows and make pairs of 4.

no of 1's	minterms	A B C D
1	1-3-5-7	0 - -1] ✓
	1-3-3-7	0 - -1] ✓
	1-3-9-11	-0 - 1] ✓
	1-9-3-11	-0 - 1] ✓
	1-5-9-13	--01] ✓
	1-9-5-13	--01] ✓

2.

3-7-11-15	--11] ✓
3-11-7-15	--11] ✓
5-7-13-15	-1 - 1] ✓
5-13-7-15	-1 - 1] ✓
9-11-13-15	1 - -1] ✓
9-13-11-15	11 - -1]
10-11-14-15	1-1 -]
10-14-11-15	1-1 -]
12-13-14-15	11 - -]
12-14-13-15	11 - -]

* If we get similar pairs,
our ans is correct.

~~Step 5~~: Make further Pairs.

no of 1s.	minterms	A B C D
1	1-3-5-7-9-11-13-15	- - - 1
1	1-3-9-11-5-7-13-15	- - - 1
1	1-5-9-13-3-7-11-15	- - - 1

~~Step 6~~: Note down all the Pairs where further pairing wasn't possible.

minterms	A B C D	Term
10, 11, 14, 15	1 - 1 -	AC
12, 13, 14, 15	1 1 - -	AB
1, 3, 5, 7, 9, 11, 13, 15	- - - 1	D

These are
PIs (Prime Implicants)

Replace
1 by
literal
and 0 by
its complement

~~Step 7~~: Make the PI table.

PI	minterms	1	3	5	7	9	10	11
AC	10, 11, 14, 15						X	X
AB	12, 13, 14, 15							
D	1, 3, 5, 7, 9, 11, 13, 15	X	X	X	X	X		X

(don't write don't care elements)

- ① Put a cross against the min. present.
- ② Circle the X's which are one in the column

- ③ Every PI with a circled x is an essential PI
- ④ Write F as sum of essential PIs.

$$F = AC + D$$

AC and D cover all the minterms, since they don't, we include a PI in the ans. which consists of the remaining minterms



logic gates

AND

$$\begin{array}{c} A \\ \text{---} \\ B \end{array} \rightarrow D \rightarrow \begin{array}{c} A \\ \text{---} \\ B \end{array} \quad F = A \cdot B$$

OR


$$\begin{array}{c} A \\ \text{---} \\ B \end{array} \rightarrow \text{OR gate} \rightarrow F \quad F = A + B$$

NOT

$$A \rightarrow \text{NOT gate} \rightarrow F \quad F = \bar{A}$$

EXOR

$$\begin{array}{c} A \\ \text{---} \\ B \end{array} \rightarrow \text{EXOR gate} \rightarrow F \quad F = A \oplus B \\ = AB + \bar{A}\bar{B}$$

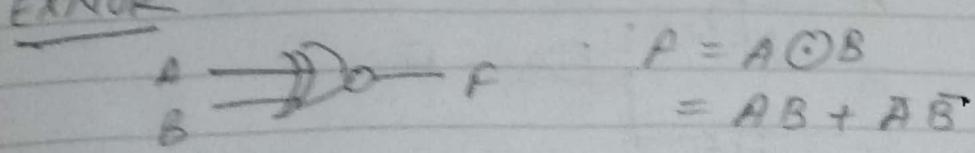
EXNOR

$$P = A \odot B$$


$$= AB + A\bar{B}$$

Universal Gates -

Any logical expression / circuit can be represented only in terms of NAND/NOR gates. Hence, they are known as universal gates.

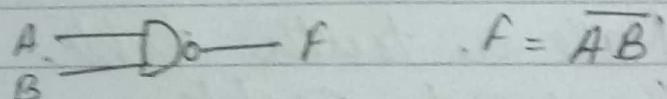NAND

$$F = \overline{AB}$$

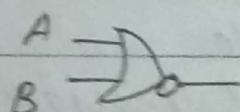NOR

$$F = \overline{A+B}$$

- * To write any exp in form of NAND gates find simplified SOP and then take complement twice
- * For NOR use POS.


Ex

$$F = AB + CD$$

$$F = [(AB + CD)']'$$

$$= [(AB)' \cdot (CD)']' \rightarrow \text{in form of } 3 \text{ nands.}$$
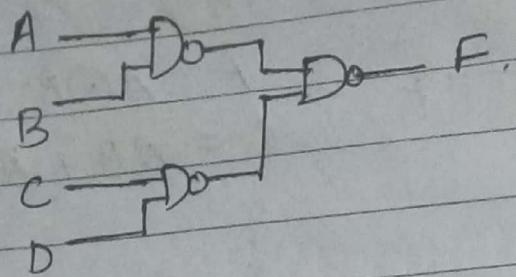
$$= \text{NAND}(\text{NAND}(A,B), \text{NAND}(C,D))$$



Combinational Circuits

It is a logical circuit in which the output is independent of previous output.

Steps to form a Combinational Circuit.

- ① Make a truth table to using the word problem.
- ② Write the expression using the truth table.
- ③ Simplify the expression to form a standard exp.
- ④ Implement it using logic gates.


ADDER

Half Adder \rightarrow adds two 1 bit nos. and return sum and carry.

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = \bar{A}\bar{B} + A\bar{B} = A \oplus B$$

$$\text{Carry} = AB$$

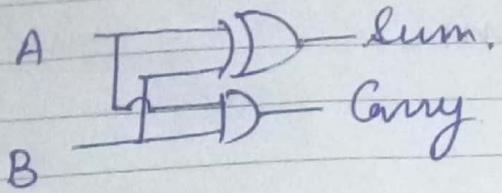

Adder → Adds 3 1bit nos are returns sum and carry.

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$

$$= \bar{A}(B \oplus C) + A(B \odot C)$$

$$= \bar{A}(B \oplus C) + A(B \oplus C)$$

[since
 $A \odot B = \bar{A} \oplus B$]

$$= A \oplus (B \oplus C)$$

$$= A \oplus B \oplus C$$


$$\text{Carry} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$

$$[x+x=x]$$

$$= (\bar{A}+A)BC + (\bar{B}+B)(AC) + (\bar{C}+C)(AB)$$

$$= AB + BC + CA \quad [\bar{x}+x=1]$$

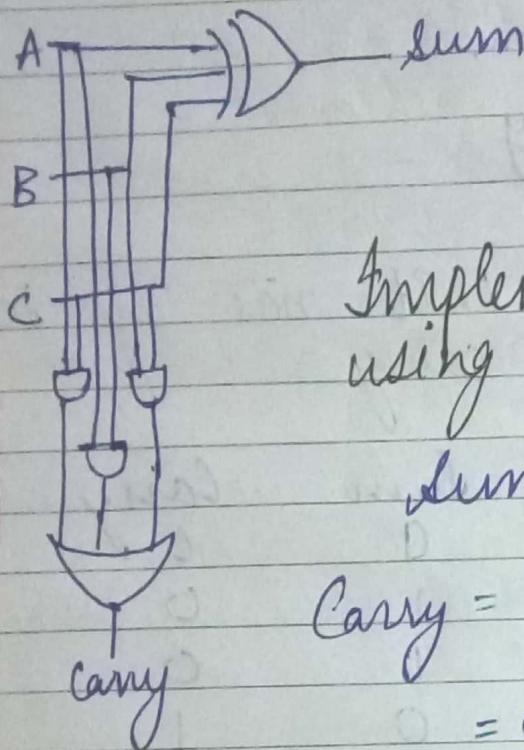


Implementing Full Adder
using 2 Half-Adders

$$\text{sum} = [A \oplus B] \oplus C$$

$$\begin{aligned}\text{Carry} &= \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \\ &= C(\bar{A}B + A\bar{B}) + AB(C + \bar{C}) \\ &= (A \oplus B) \cdot C + AB.\end{aligned}$$

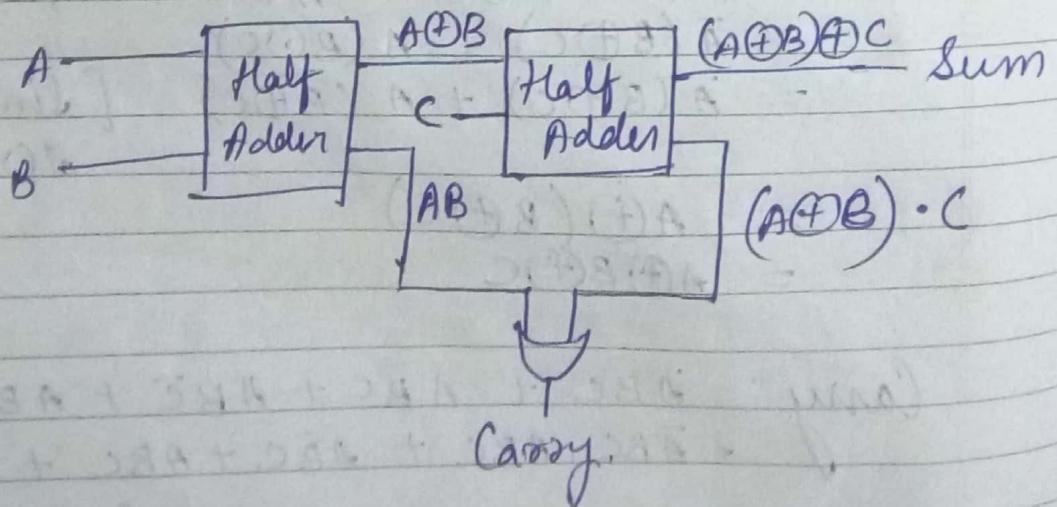Now, $A \oplus B$ is sum of half adder and AB is its carry.




~~SUBTRACTOR~~

Half Sub \rightarrow Subs two one bit nos, and returns diff and borrow.

A	B	Diff	B_o
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Diff} = A\bar{B} + \bar{A}B = A \oplus B$$

$$B_o = \bar{A}B$$

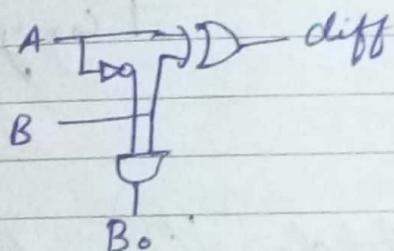


Full Sub \rightarrow Sub three one bit no such as $(A - B) - C$.

A	B	C	Diff	B_o
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Diff} = A \oplus B \oplus C \quad (\text{Same as Added})$$

$$B_o = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$
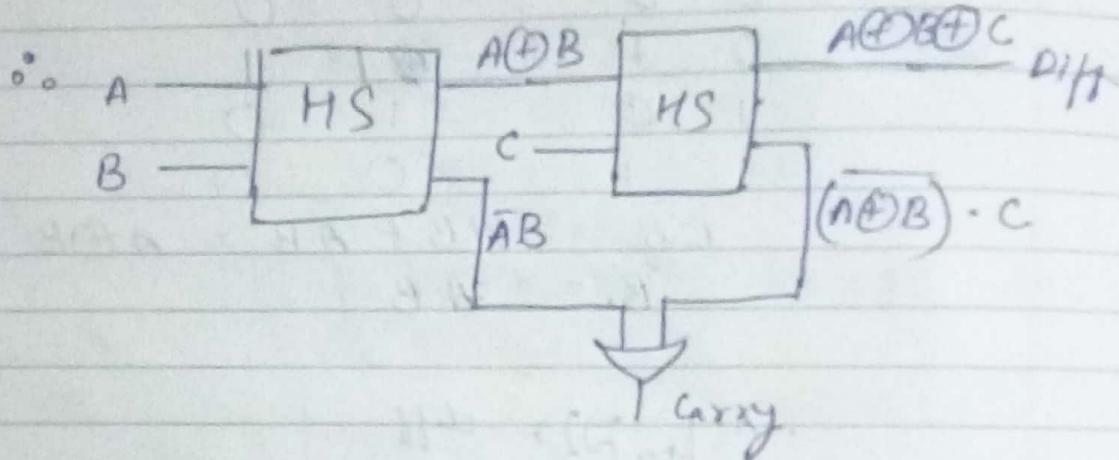
$$\begin{aligned}
 &= \bar{A}B(C + \bar{C}) + C(A\bar{B} + A\bar{B}) \\
 &= \bar{A}B(1) + C(A\bar{B}) \\
 &= \bar{A}B + (\bar{A}\oplus B) \cdot C
 \end{aligned}$$



~~Carry Propagate Adder~~

Parallel Binary Adder / Carry Propagate Adder

Adding 4 bit no:

$$\begin{array}{cccc}
 C_3 & C_2 & C_1 & C_0 = 0 \\
 A_3 & A_2 & A_1 & A_0 \\
 B_3 & B_2 & B_1 & B_0 \\
 \hline
 C_4 & S_3 & S_2 & S_1 & S_0
 \end{array}$$


$C_1 \rightarrow$ carry of $A_0 + B_0$

$C_2 \rightarrow$ carry of $A_1 + B_1$,

$C_3 \rightarrow$ carry of $A_2 + B_2$

$C_4 \rightarrow$ carry of $A_3 + B_3$

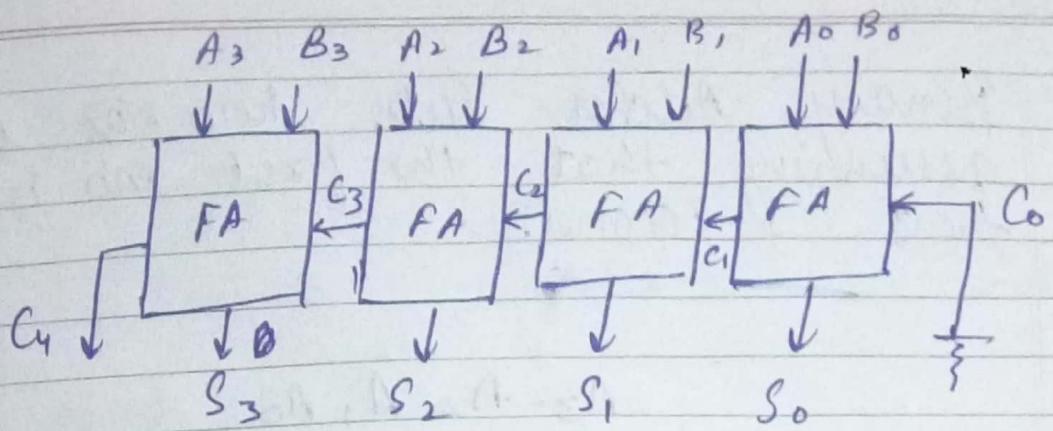8 inputs are given to 2 Adders
and the carry of one is passed
as an input to another.



Binary Subtractor

* Subtraction using 2's Compliment
For $A - B$.

- ① Take 2's compliment of B .
- ② Add A and B .
- ③ If $B < A$; their addition is the final ans just neglect carry.
- ④ If $B \geq A$; take two's compliment of the result and put a -ve sign.

Two's Compliment

- ① Replace 0s by 1s and 1s by 0s.
- ② Add '1' to the outcome.

$$\begin{array}{r} 1010 \\ \leftrightarrow 0101 + 1 \\ = 0110 \end{array}$$

Binary Adder Sub. two no's assuming that the first no is larger than second.

$$\begin{array}{r} A_3 \ A_2 \ A_1 \ A_0 \\ - B_3 \ B_2 \ B_1 \ B_0 \end{array}$$


$$\begin{array}{r} C_3 \ C_2 \ C_1 \ C_0 = 1 \\ A_3 \ A_2 \ A_1 \ A_0 \\ + B_3' \ B_2' \ B_1' \ B_0' \\ \hline C_4 \ S_3 \ S_2 \ S_1 \ S_0 \end{array}$$

diff.

$$\begin{array}{r} 1 \ 0 \ B \oplus 1 \ B \oplus 0 \\ 0 \ 1 \ 0 \ 1 \ 0 \\ 1 \ 1 \ 0 \ 0 \ 1 \end{array}$$

$$\begin{aligned} B \oplus 1 &= B' \\ B \oplus 0 &= B. \end{aligned}$$

∴ A parallel adder/Sub can be made as.

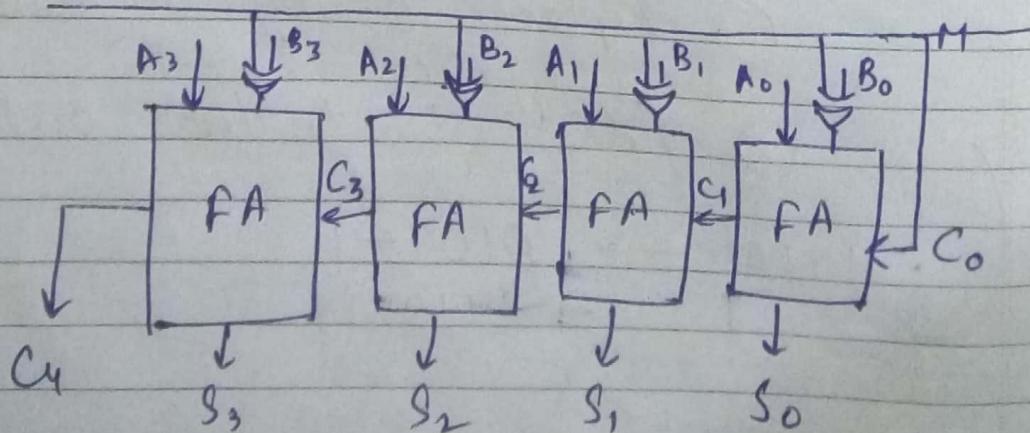

If $M = 0$.

$$C_0 = 0$$

$$\text{and } B \oplus M = B$$

∴ It works as an adder.

If $M = 1$

$$C_0 = 1$$

$$\text{and } B \oplus M = B'$$

∴ It works as a sub.

Carry Look Ahead Adder.

Parallel Adder takes more time as each FA has to wait for the previous FA to complete its process. Thereby increasing time by 4 times.

∴ we use carry look

ahead adder, which calculates carry in advance.

$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = \cancel{A_i \oplus B_i} \quad (A_i \oplus B_i)(\bar{A}_i + A_i B_i)$$

Put $A_i \oplus B_i = P_i$

and $A_i \cdot B_i = G_i$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = P_i C_i + G_i$$

$$C_0 = 0$$

$$\text{For } C_1 = P_0 \cdot C_0 + g_0$$

$$C_1 = g_0 \quad \text{--- (1)}$$

$$C_2 = P_1 \cdot C_1 + g_1$$

$$C_2 = P_1(g_0) + g_1 \quad (\text{from (1)})$$

$$C_2 = P_1 g_0 + g_1 \quad \text{--- (2)}$$


$$C_3 = P_2 C_2 + g_2$$

$$C_3 = P_2(P_1 g_0 + g_1) + g_2$$

$$C_3 = P_2 P_1 g_0 + P_2 g_1 + g_2 \quad \text{--- (3)}$$

$$C_4 = P_3 C_3 + g_3$$
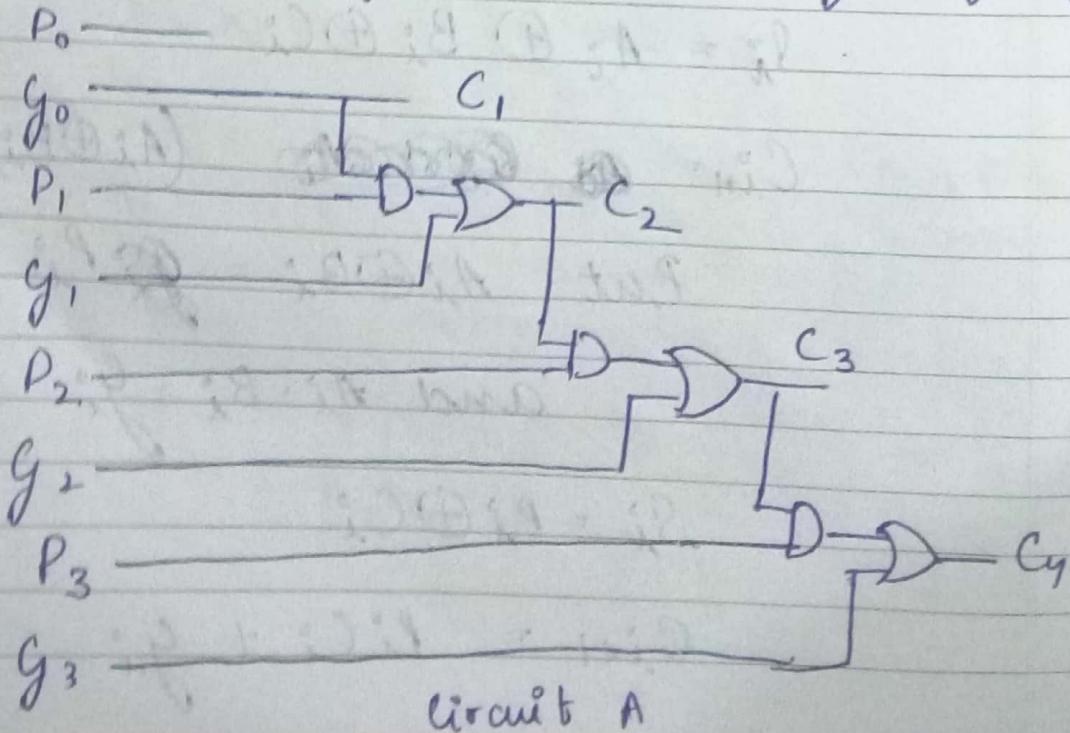
$$C_4 = P_3 P_2 P_1 g_0 + P_3 P_2 g_1 + P_3 g_2 + g_3 \quad \text{--- (4)}$$



For sum.



$$S_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$


$$S_3 = P_3 \oplus C_3$$

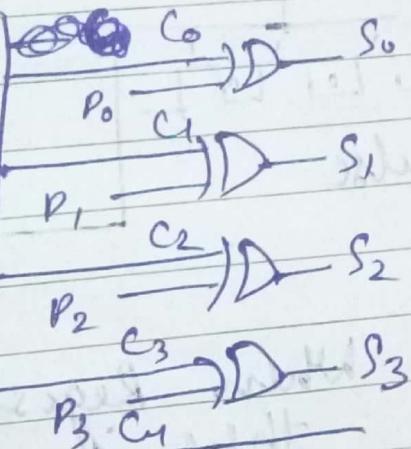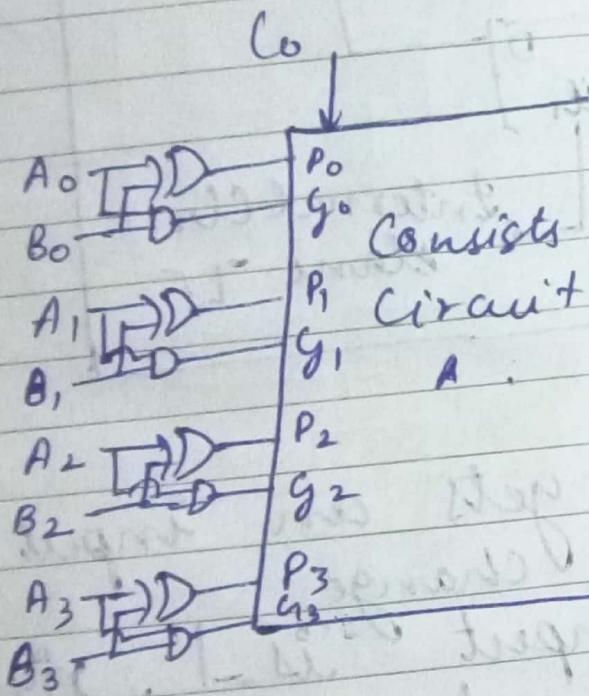∴ Carry Look AHEAD ADDER
can be drawn as.



~~Carry Look Ahead~~
A Carry look Ahead Adder reduces time but increases circuitry.
And that is its drawback.

Serial Adder

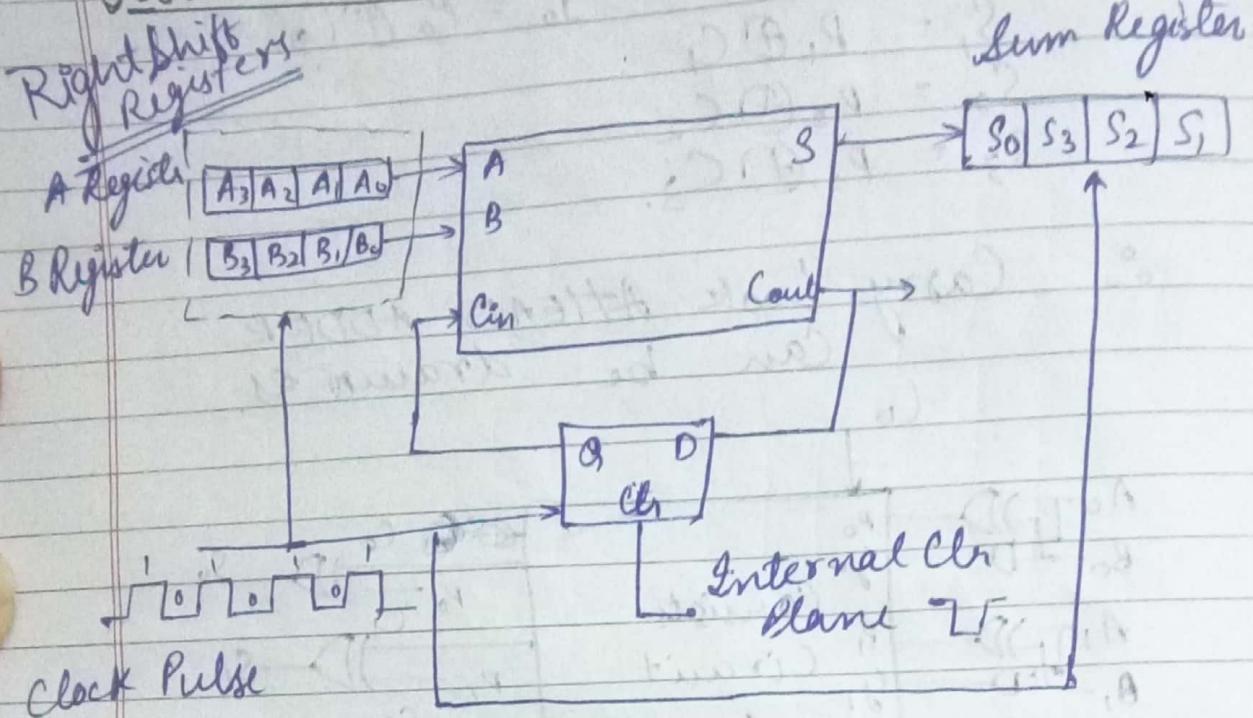

When Register gets an input 0
there is no change,

when input is 1, right shift takes place

when clock is 0

$$A = A_0$$

$$B = B_0$$

$$Cin = 0$$

$$S = A \oplus B \oplus C_{in}$$

$$Cout = \text{Carry}$$

Cout is stored
in memory

when clock is 1
Registers shift.

$$[A_0 | A_3 | A_2 | A_1]$$

$$[B_0 | B_3 | B_2 | B_1]$$

$$[S_1 | S_0 | S_3 | S_2]$$

when clock = 1

$$A = A_3 \ A_2 \ A_1 \ A_0$$

$$B = B_3 \ B_2 \ B_1 \ B_0$$

C_{in} = previous C_{out} .

$$S = A \oplus B \oplus C_{in}$$

$C_{out} = \text{Carry}$

$$S_1 = S_0$$

C_{out} is stored
in memory

And this continues till complete addition occurs.

Final Carry and $S_3 \ S_2 \ S_1 \ S_0$ give us the sum.

Carry Save Adder

Adds more than 2 nos simultaneously.

First 3 no are given as 11 inputs and later new no are introduced on every step.

At the end a 11 adder is added to complete the addition.


Q) 4 No Adder can be constructed with

$$A = A_3 \ A_2 \ A_1 \ A_0$$

$$B = B_3 \ B_2 \ B_1 \ B_0$$


$$C = C_3 \ C_2 \ C_1 \ C_0$$

$$D = D_3 \ D_2 \ D_1 \ D_0$$

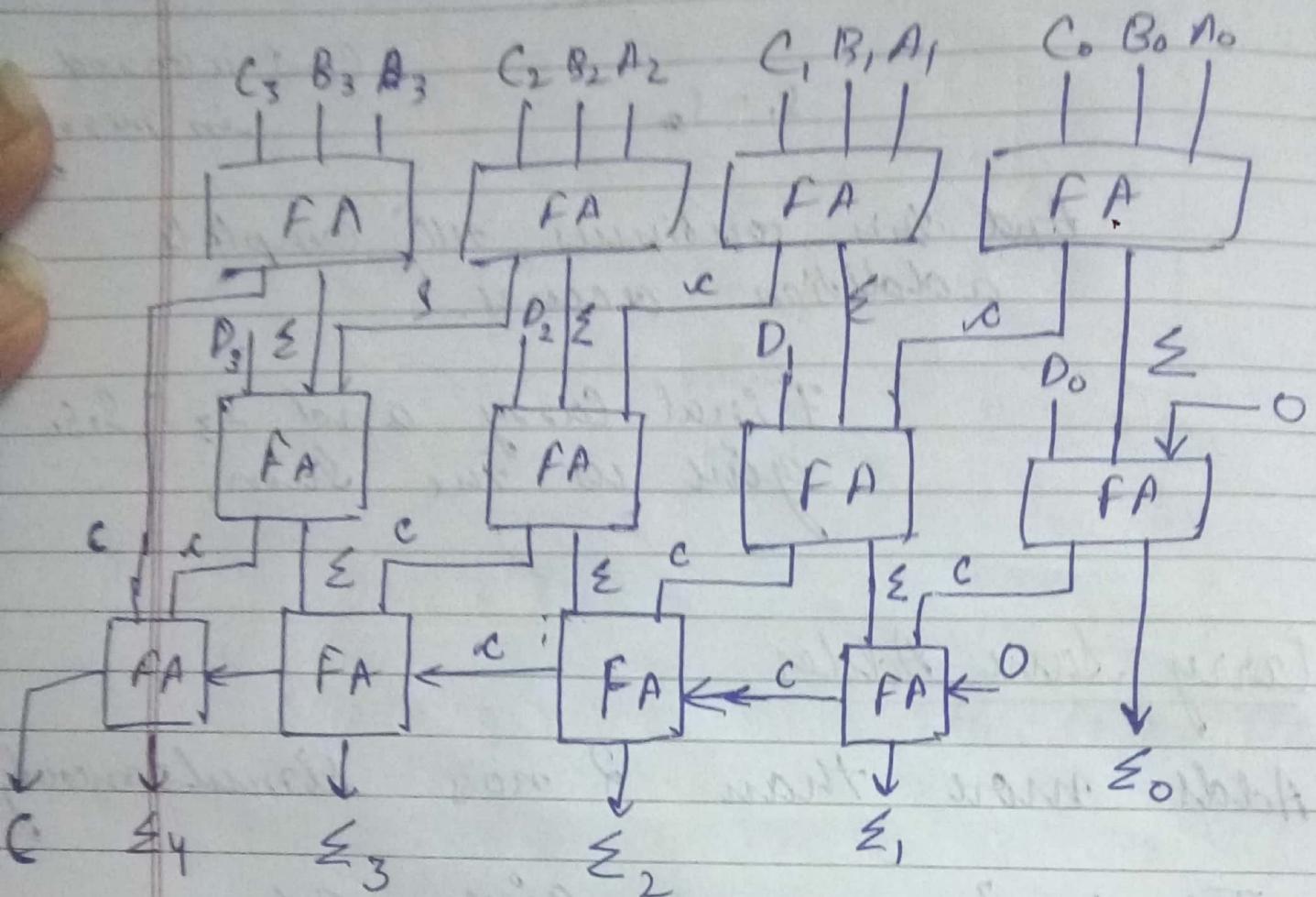

Comparators

1-Bit

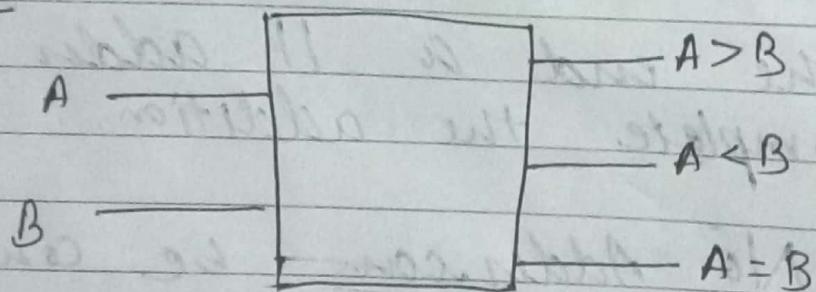

A > B

A	B
0	0
0	1
1	0

$A > B$

0	0
0	1
1	0

$A < B$

0	1
1	0
0	0


$A = B$

1	0
0	1
0	0

$$A > B \Rightarrow A\bar{B}$$

$$A < B \Rightarrow \bar{A}B$$

$$A = B \Rightarrow A \oplus B$$

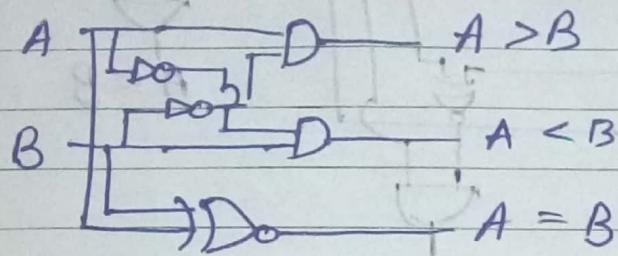

4-Bit Comparator

$$A = A_1 A_0$$

$$B = B_1 B_0$$

$$A_1 > B_1 \rightarrow A > B$$

$$A_1 < B_1 \rightarrow A < B$$

$$A_1 = B_1$$

$$A_0 > B_0 \rightarrow A > B$$


$$A_0 < B_0 \rightarrow A < B$$

$$A_0 = B_0 \rightarrow A = B$$

$$A > B \Rightarrow A_1 \bar{B}_1 + (A_1 \oplus B_1) A_0 \bar{B}_0$$

$$A < B \Rightarrow \bar{A}_1 B_1 + (A_1 \oplus B_1) B_0 \bar{A}_0$$
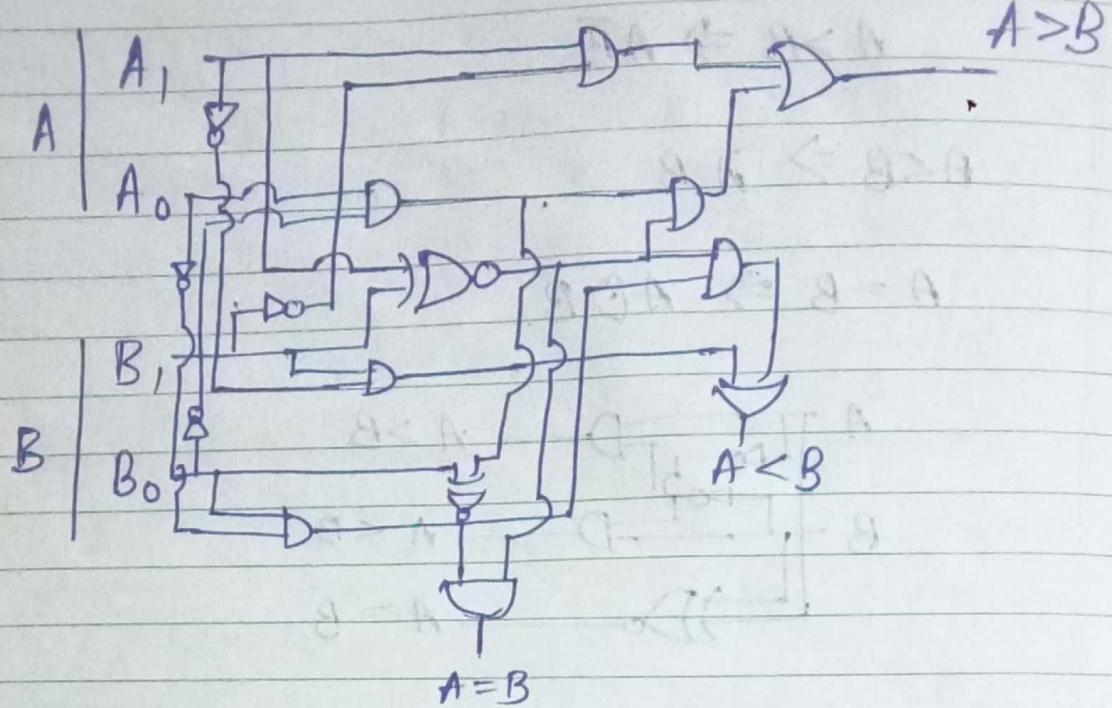
$$A = B \Rightarrow (A_1 \oplus B_1)(A_0 \oplus B_0)$$



Parity Generators

Parity Generators and checkers are used to check if a signal transmitted is same as the signal received.

A parity bit is generated at the transmitting end and is cross-verified at the receiving end.

They are of two types

even bit

parity generator

odd bit

Parity generator


Parity bit added is such that no of ~~bits~~ bits including the parity bit is even.

No. of bits including the parity bit should be odd.

Even Bit.Even


A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = A \oplus B \oplus C$$

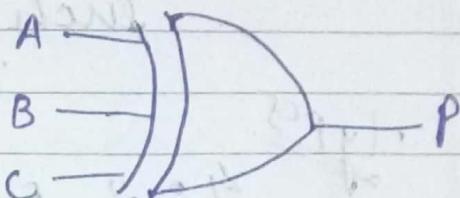Odd Bit

A	B	C	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

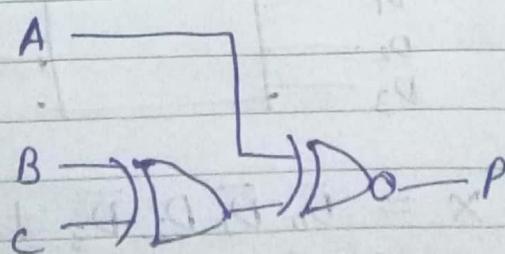$P = \overline{ABC} + \overline{ABC}$
 $+ A\overline{B}C + AB\overline{C}$
 $= \overline{A}(B \cdot C) + A(B \oplus C)$
 $= \overline{A}(B \oplus \overline{C}) + A(B \oplus C)$
 $= A \odot (B \oplus C)$



Encoder →

An encoder codes a message with m input channels into a message with n output channels

such that

$$m \leq 2^n$$

Types


4 : 2 encoder

8 : 3

16 : 4

m


!

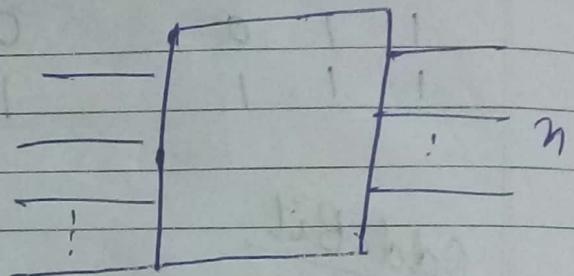

4 → 2 (only one bit can be one at a time)


D_0	D_1	D_2	D_3	1
1	0	0	0	0
0	1	0	0	1
0	0	1	0	0
0	0	0	1	1

X	Y	1	0
00	00	0	1
01	01	1	0
10	10	1	1
11	11	1	1

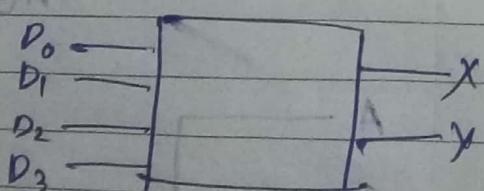

$$\begin{aligned}
 X &= \overline{D_0} \overline{D_1} D_2 \overline{D_3} + \overline{D_0} \overline{D_1} \overline{D_2} D_3 \\
 &= D_2 + D_3 \quad (\text{because when } D_2 \text{ is } 1 \text{ rest are automatically } 0)
 \end{aligned}$$

$$Y = D_0 + D_1$$

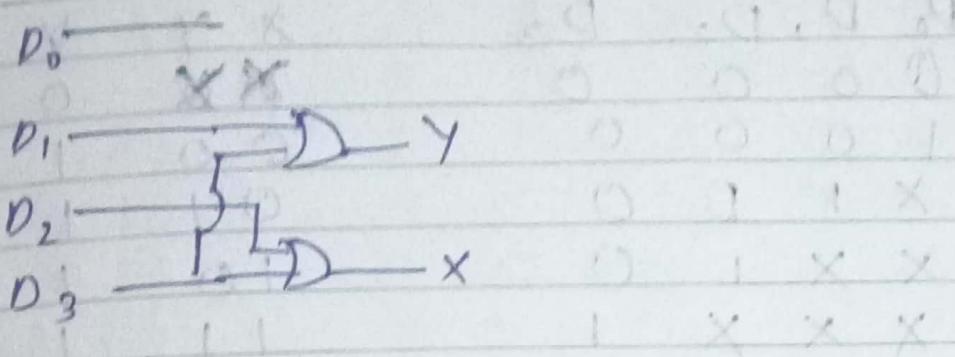

D₀	D₁	D₂	D₃	D₄	D₅	D₆	D₇	X Y Z
1	0	0	0	0	0	0	0	000
0	1	0	0	0	0	0	0	001
0	0	1	0	0	0	0	0	010
0	0	0	1	0	0	0	0	011
0	0	0	0	1	0	0	0	100
0	0	0	0	0	1	0	0	101
0	0	0	0	0	0	1	0	110
0	0	0	0	0	0	0	1	111

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

Limitations

- ① Only one bit can be 1.
- ② 0000 gives the same output as 1000.

Priority Encoder

It eliminates the limitations of encoder by introducing another output V.

When V is 1 \rightarrow Inputs are valid
 V is 0 \rightarrow Incorrect inputs.

D_0	D_1, D_2	D_3	X	Y	V
0	0 0	0	X	X	0
1	0 0	0	0 0	0	1
X	1 0	0	0 1	1	
X	X 1	0	1 0	1	
X	X X	1	1 1	1	

$$X = D_3 + \overline{D}_3 D_2 = D_3 + D_2$$

$$Y = D_3 + \overline{D}_3 \overline{D}_2 D_1$$

$$= D_3 + \overline{D}_2 D_1$$

$$\boxed{X + \overline{X} Y = X + Y}$$

$$N = D_0 + D_1 + D_2 + D_3$$

Decoder A decoder ~~decodes~~ decodes a message with n input lines & m output lines such that


$$m \leq 2^n$$

Types


3: 8

2: 4

4: 16

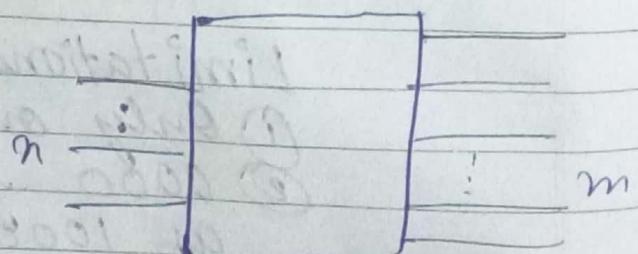

3x8

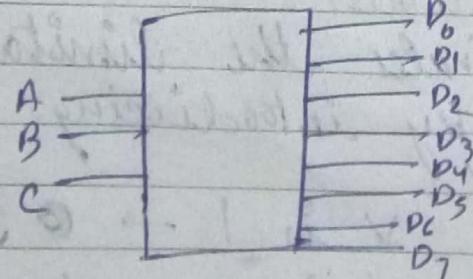

$A \ B \ C$	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
000	1	0	0	0	0	0	0	0
001	0	1	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0
011	0	0	0	0	1	0	0	0
100	0	0	0	0	0	1	0	0
101	0	0	0	0	0	0	1	0
110	0	0	0	0	0	0	0	1
111	0	0	0	0	0	0	0	1

$$D_0 = \bar{A} \bar{B} \bar{C}$$

$$D_4 = A \bar{B} \bar{C}$$

$$D_1 = \bar{A} \bar{B} C$$


$$D_5 = A \bar{B} C$$

$$D_2 = A \bar{B} \bar{C}$$

$$D_6 = A B \bar{C}$$

$$D_3 = \bar{A} B C$$

$$D_7 = A B C.$$

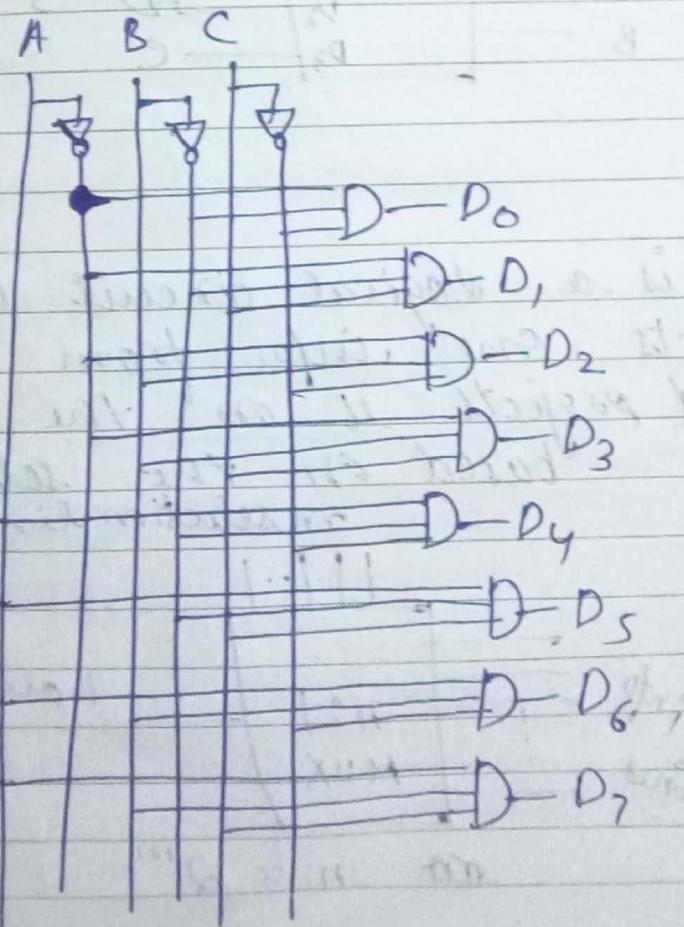


~~Ques.~~ Implement a circuit using Decoder.

- ① Write the function in canonical form.
- ② ~~for~~ OR the outputs corresponding to minterms

Adder using Decoder.


$$S = \bar{A}B + \bar{B}A$$

$$C = AB$$

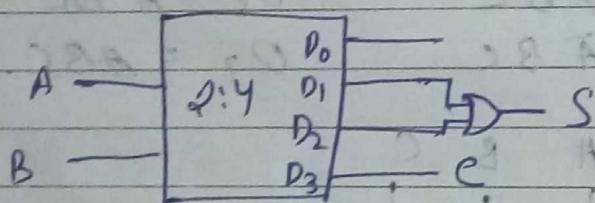

~~MUX~~

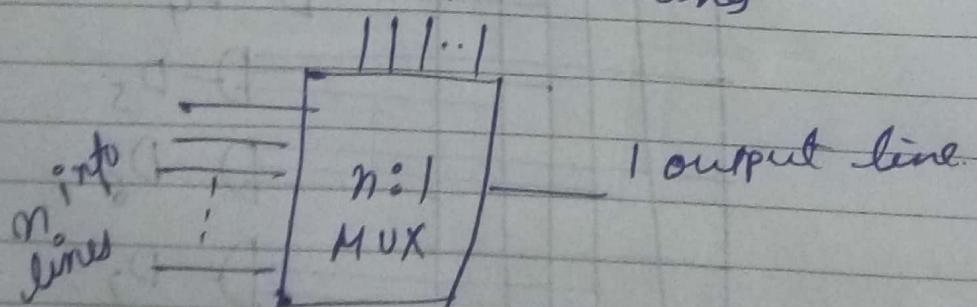It is a logical circuit which selects one info. from the source and projects it on the output line based on the selection lines in selection lines



$$\textcircled{2} \quad n = 2^m$$

Type 4:1


8:1

16:1


⋮

4:1 MUX

A	B	X
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

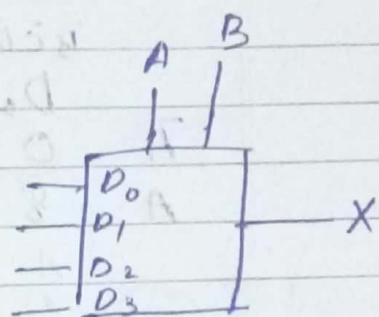
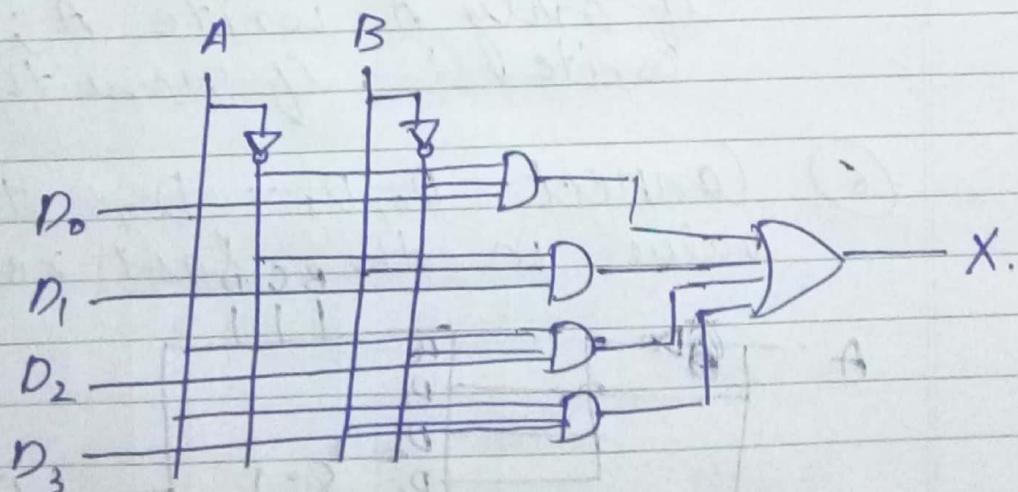
$$X = \bar{A}\bar{B}D_0 + \bar{A}BD_1 + A\bar{B}D_2 + AB\bar{D}_3.$$



Implement a circuit using MUX.
If no of variables = N
So, we use $2^{n-1}:1$ mux.

Explanation with ex.

$$\text{MAP, BCD, DF} = \Sigma (0, 3, 2, 9, 12, 13, 15)$$

① Take BCD as selection lines.


② Draw a table for minterms corresponding to BCD and A.

	$\bar{B}\bar{C}\bar{D}$	$\bar{B}\bar{C}D$	$\bar{B}C\bar{D}$	$\bar{B}CD$	$B\bar{C}\bar{D}$	$B\bar{C}D$	$BC\bar{D}$	BCD
A	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
A	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
A	1	1	1	1	1	1	0	1

③ Circle the minterms present in ques.


④ If only \bar{A} is circled write \bar{A} if only A write A; if both write 1; if none the 0.

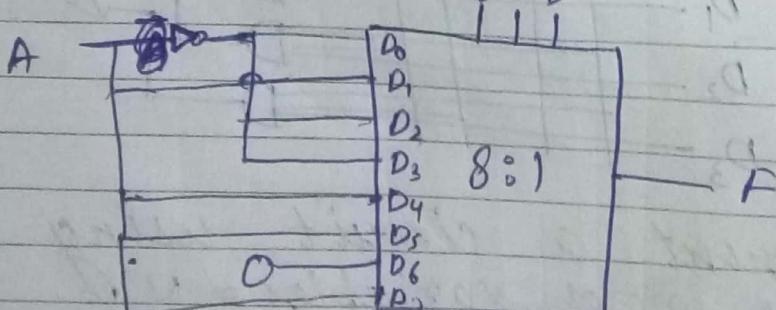⑤ Connect D_0, D_1, \dots, D_7 to the value in the BCD last row.



~~DEMUX~~

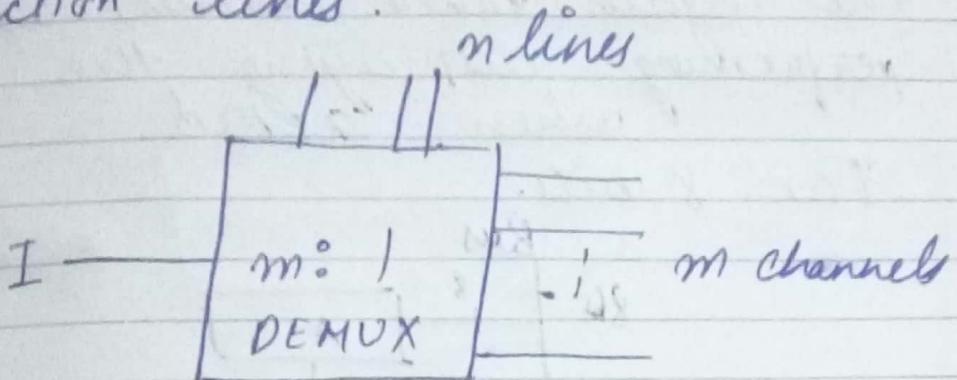~~DEMUX~~ is a logical circuit which projects an information in one of the output channels according to the selection lines.



$$m = 2^n$$


1:4

1:8

1:16

~~1:4~~

A	B	D_0	D_1	D_2	D_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

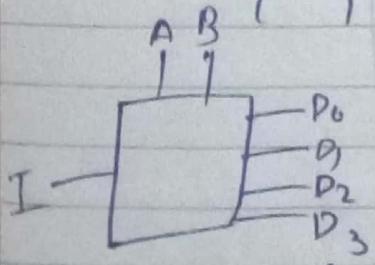


$$D_0 = \overline{A} \overline{B} I$$

$$D_1 = \overline{A} B I$$

$$D_2 = A \overline{B} I$$


$$D_3 = A B I$$

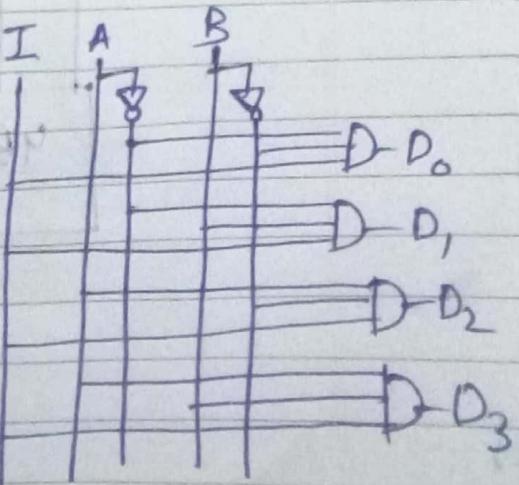

~~ALU~~

ALU performs arithmetic operations (addition/sub in this case) in a computer by taking the no from the registers (saved values) and performing displaying the output when asked.

For 8 bits.

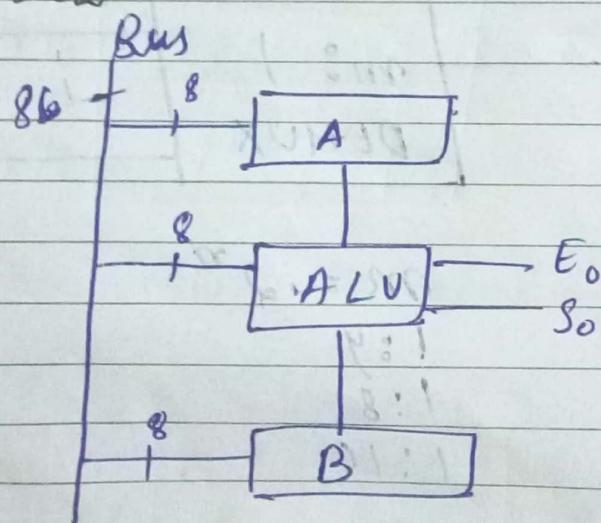


when $E_0 = 1 \rightarrow$ display

when $S_0 = 1 \rightarrow$ Sub

$S_0 = 0 \rightarrow$ add.

Registers

A Register.

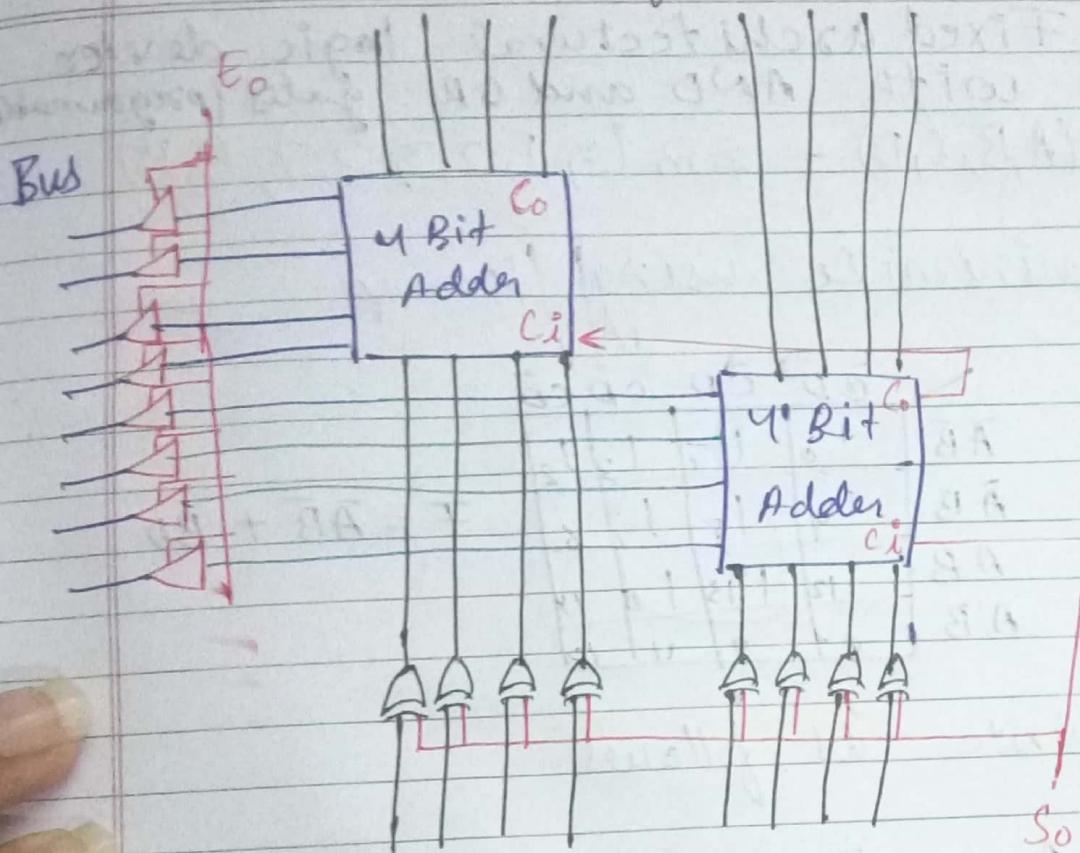

B Register :

~~PLA and
PAL~~

~~PAL~~ → Programmable Array Logics.

~~PLA~~ → Programmable Logic Arrays

- | | |
|---|---|
| <ul style="list-style-type: none"> ① PLA ② Shared Terms ③ Fully Programmable | <ul style="list-style-type: none"> ① PAL ② No Shared terms ③ Not fully programmable. |
|---|---|


~~PLA example~~. Fixed architectural logic devices with AND and OR gates (programmable) $F(A, B, C, D) = \Sigma m(0, 1, 2, 3, 5, 7, 13, 15)$

① minimize using K map

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1 ₀	1 ₁	1 ₂	1 ₂
$\bar{A}B$	1 ₄	1 ₅	1 ₇	1 ₆
$A\bar{B}$	1 ₁₂	1 ₁₃	1 ₁₄	1 ₁₅
AB	1 ₈	1 ₉	1 ₁₁	1 ₁₀

$F = \bar{A}\bar{B} + BD$

② Write as follows.

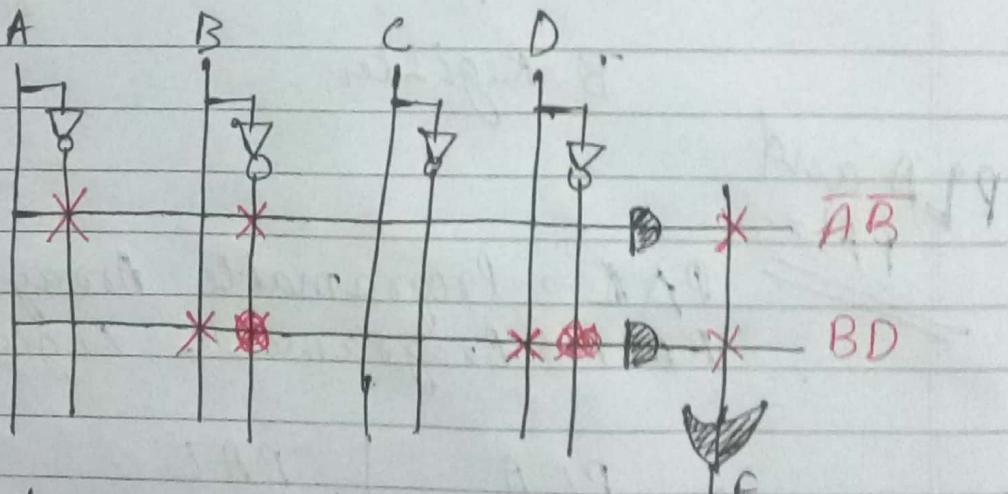


③ We have two terms hence draw two horizontal lines with AND

④ Cut the lines and draw an OR to represent OR in the F.

⑤ Put crosses on the literals used.

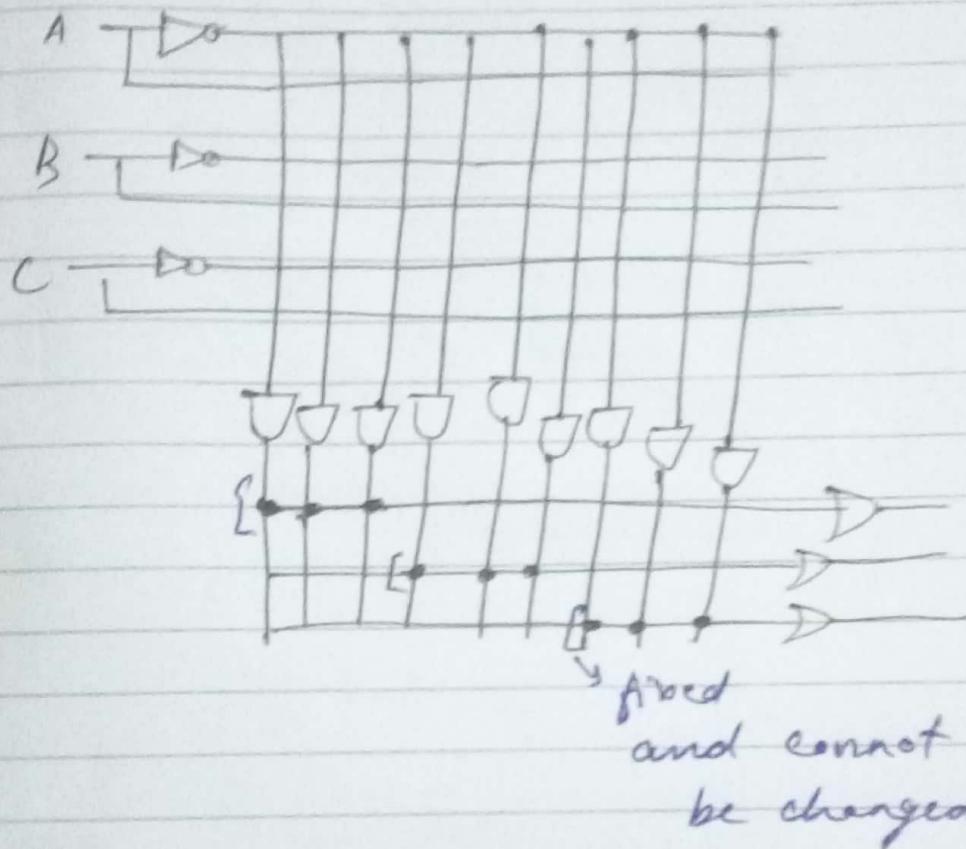PAL, Fixed Architectural logic device with programmable AND and fixed OR gates.



we cannot put crosses
acc to our will!

Rest is same as PLA

Point Conversions

classmate

Date _____

Page _____

Decimal \rightarrow Binary

- (1) Separate the values before and after point.
- (2) For left side convert acc to normal rules (dividing by 2)
- (3) For right side, multiply by 2, on every step note the value of the no. of decimal point.
- (4) Right it from upper to lower.

(ex) \rightarrow 3.75

11 ↘ ↗

$0.75 \times 2 = 1.5$ ↗
 $0.5 \times 2 = 1.0$ ↗

11.11

(ex) \rightarrow 13.25

1101 ↙ ↗

$0.25 \times 2 = 0.5$ ↗
 $0.5 \times 2 = 1.0$ ↗

1101.01

Binary \rightarrow decimal. (-ve powers of 2 for right of point).

$$(1101.01)_2 = (?)_{10}$$

$$(1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) + (0 \times 2^{-1}) + (1 \times 2^{-2}) = 3.25$$

For Octal and Hexa use 8 and 16 resp.