

## Electrical Technology

Ohms law  $V = IR$

$$R = \rho \frac{L}{A}$$

Resistivity

$$\rho_{Ag} = 1.67 \Omega$$

$$\rho = \rho \times \frac{m}{m^2}$$

$$\boxed{\rho = \rho m}$$

$$\rho (10^{-8}) \text{ ohm m}$$


Date: / /  
Page No.: TELCO

Date: / /  
Page No.: TELCO

## Kirchhoff's laws
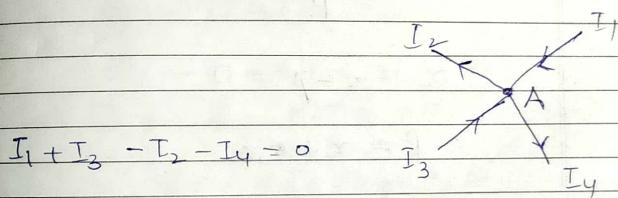
### ① KCL

In any network, sum of the currents meeting at any point of the loop is zero.




$$I_1 + I_3 - I_2 - I_4 = 0$$

$$I_1 + I_3 = I_2 + I_4$$


### ② KVL

The algebraic sum of the product of current & resistances of the electrical components in a loop as well as the emf of that loop is zero.

$$\Sigma IR + \Sigma emf = 0$$

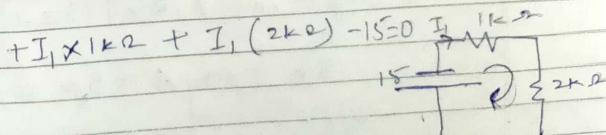

E3.1

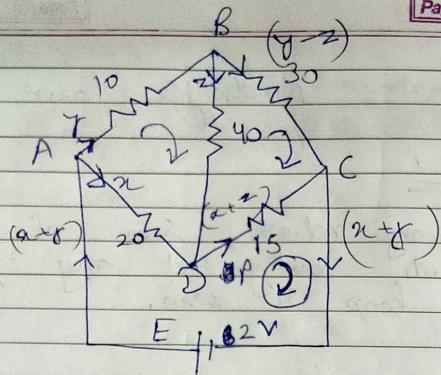

$$x + z - p = 0$$

$$p = x + z$$

In loop ABDA,

$$-10y + 40z + 20x = 0$$

$$20x = y + 4z \quad \textcircled{1}$$

In BCDB,

$$-30(y - z) + 15(x + z) + 40z = 0$$

$$-30y + 30z + 15x + 15z + 40z = 0$$

$$15x - 30y + 85z = 0$$

$$3x - 6y + 17z = 0 \quad \textcircled{2}$$

Date : / /  
Page No.: TELCO

Date : / /  
Page No.: TELCO

In ADCA,

$$-20x - 15(x + z) + 2 = 0$$

$$20x + 15x + 15z - 2 = 0$$

$$35x + 15z - 2 = 0 \quad \textcircled{3}$$

By  $\textcircled{1}$  &  $\textcircled{2}$ ,

$$\begin{aligned} 20x - y - 4z &= 0 && \times 6 \\ 3x - 6y + 17z &= 0 \end{aligned}$$

$$12x - 6y - 24z = 0 \quad \textcircled{4}$$

$$3x - 6y + 17z = 0$$

$$9x - 41z = 0$$




By  $\textcircled{3}$  &  $\textcircled{4}$ ,

$$\begin{aligned} z &= \frac{9}{785} \\ &= 0.01146 \text{ A} \end{aligned}$$

Dir<sup>n</sup> is same as assumed

Date: / /  
Page No.:  
TELCO

Date: / /  
Page No.:  
TELCO

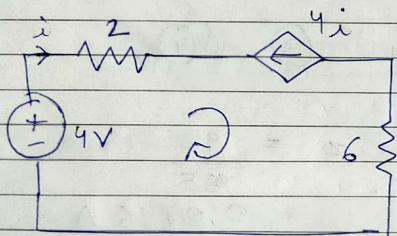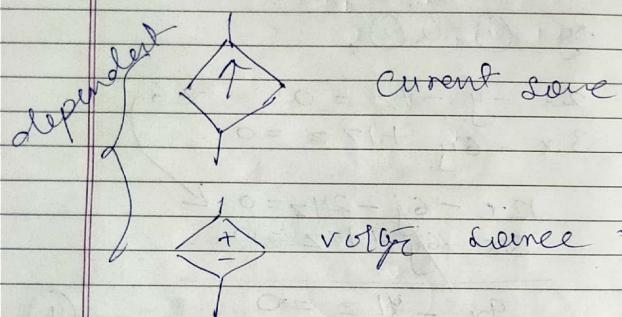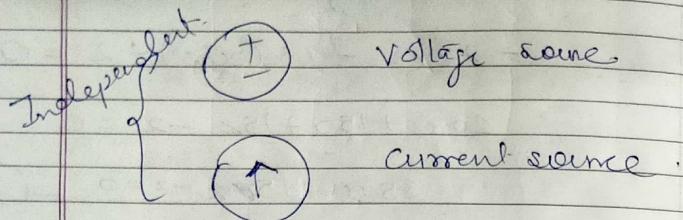


$$-8i + 4i$$

$$-2i + 4i - 6i + 4 = 0$$

$$\text{or } -4i + 4 = 0$$

$$\Rightarrow i = 1 \text{ A}$$

∴ I = 1 A. II is taken.

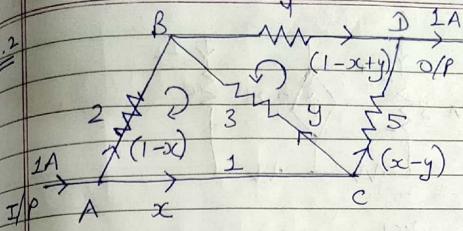

$$-2(1-x) + 3y + x = 0$$

$$\Rightarrow -2 + 2x + 3y + x = 0$$

$$3x + 3y = 2 \quad \textcircled{1}$$

$$4(1-x+y) + 3y - 5(x-y) = 0$$

$$\Rightarrow 4 - 4x + 4y + 3y - 5x + 5y = 0$$

$$\Rightarrow -9x + 12y + 4 = 0$$


$$\text{or } 9x - 12y = 4 \quad \textcircled{2}$$

By ① & ②,

$$\begin{aligned} \textcircled{1} \times 4 &\rightarrow 12x + 12y = 8 \\ \textcircled{2} \rightarrow & 9x - 12y = 4 \\ + & + \\ 21x &= 12 \end{aligned}$$

$$\text{or } x = \frac{12}{21} \Rightarrow x = 0.571 \text{ A}$$
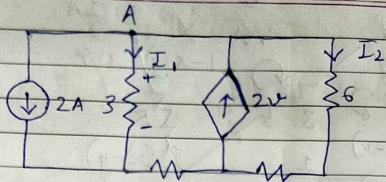
$$\begin{aligned} 3x + 12 &+ 3y = 2 \\ 3y &= 2 - \frac{12}{7} \end{aligned} \quad \text{or } y = 0.0952 \text{ A}$$



Applying KCL,

$$-2 - I_1 + 2v - I_2 = 0$$

$$\Rightarrow 2v = I_1 + I_2 + 2 \quad \textcircled{1}$$

$$v = 3I_1$$

$$\Rightarrow I_1 = \frac{v}{3}$$

&  $v = 6I_2$

or  $I_2 = \frac{v}{6}$

Putting in \textcircled{1},

$$2v = 2v + v + 2$$

$$2v = \frac{3v}{6} + 2$$


$$2v - v = 2$$

$$\frac{3v}{2} = 2 \quad \text{or} \quad v = \frac{4}{3}$$

Date: / /  
Page No.: TELCO

E3.6

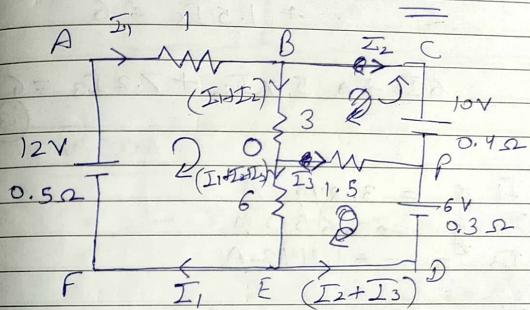$\therefore$  Value of current source will be  $2 \times \frac{4}{3}$   
 $= \frac{8}{3} A$   
 $= 2.66 A$



In loop ABFEA,

$$-0.5I_1 - I_1 - 3(I_1 + I_2) - 6(I_1 + I_2 + I_3) + 12 = 0$$

$$-0.5I_1 - I_1 - 3I_1 - 3I_2 - 6I_1 - 6I_2 - 6I_3 + 12 = 0$$

$$10 - 0.5I_1 + 9I_2 + 12I_3 = 12 \quad \textcircled{1}$$

In loop OBCPD,

$$+0.4I_2 - 1.5I_3 + 3(I_1 + I_2) - 10 = 0$$

$$0.4I_2 - 1.5I_3 + 3I_1 + 3I_2 = 10$$

$$3I_1 + 3.4I_2 - 1.5I_3 = 10 \quad \textcircled{2}$$

Date: / /  
Page No.: TELCO

In OPDEO,

$$-0.3(I_2 + I_3) + 6(I_1 + I_2 + I_3) + 1.5I_3 = 6$$

$$-0.3I_2 - 0.3I_3 + 6I_1 + 6I_2 + 6I_3 + 1.5I_3 = 6$$

$$6I_1 + 5.7I_2 + 7.2I_3 = 6$$

$$\begin{aligned} I_1 &= 3.349 \text{ A} \\ I_2 &= 0.650 \text{ A} \\ I_3 &= 1.442 \text{ A} \end{aligned}$$

The dir<sup>n</sup> of  $I_2$  &  $I_3$  is opposite.

~~XX~~

$$-4I_1 - 20I_1 + I_2 = 0$$

$$24I_1 = 12$$

$$I_1 = 0.5 \text{ A}$$

Current in 6 $\Omega$  node,

$$9I_1 = 4.5 \text{ A}$$


$$R = 6 \Omega$$

$$\checkmark = 4.5 \times 6$$

$$\checkmark = 27 \text{ V}$$

Date: / /  
Page No.: TELCO

Maxwell's Current Loop Method

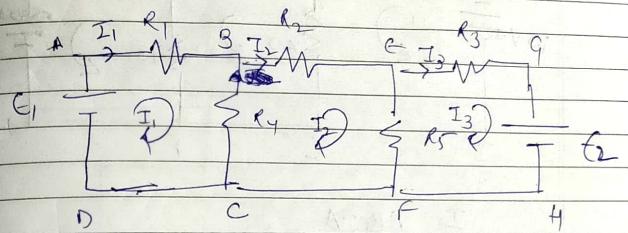

ABCDA

$$-I_1R_1 - (I_1 - I_2)R_4 + E_1 = 0$$

$$I_1R_1 + (I_1 - I_2)R_4 = E_1$$


In BEFCB,

$$-I_2R_2 - (I_2 - I_3)R_5 - (I_2 - I_1)R_4 = 0$$

In EGHFE,

$$-(I_3 - I_2)R_5 - I_3R_3 - E_2 = 0$$

3.9

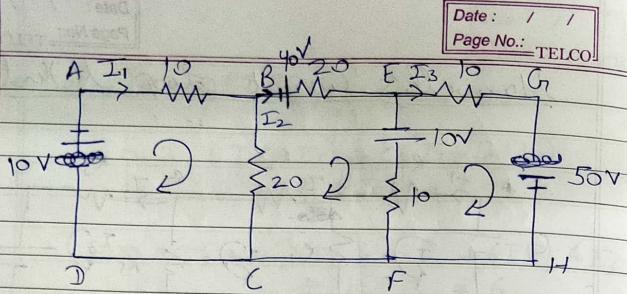

In ABCDA,

$$-10I_1 - (I_1 - I_2)_{20} + 10 = 0$$

$$\Rightarrow 10I_1 + 20I_1 - 20I_2 + 10 = 0 \quad (1)$$

In BEFCB,

$$+40 - 20I_2 + 10 - 10(I_2 - I_3) - 20(I_2 - I_1) = 0$$

$$-20I_2 - 10I_2 + 10I_3 - 20I_2 + 50 = 0$$

$$20I_1 - 50I_2 + 10I_3 = -50 \quad (2)$$

In EGHFE,

$$-10I_3 - 10(I_3 - I_2) = 50$$


$$10I_2 - 20I_3 = -40 \quad (3)$$

$$I_1 = 1A$$


$$I_2 = 2A$$

$$I_3 = 3A$$


### Source Conversion

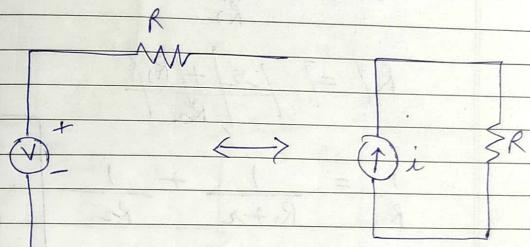

### Thermin's Theorem

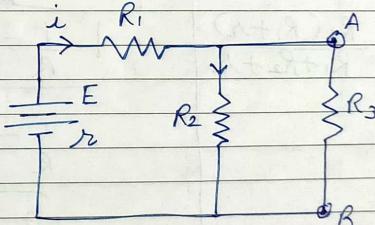

Step 1

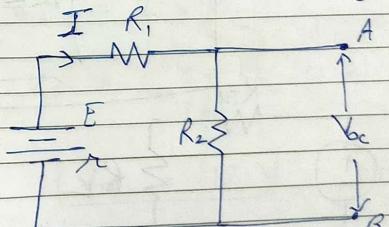


$$V_{oc} = \text{V across } R_2 = IR_2$$

$$V_{oc} = V_m = \frac{E}{R_1 + R_2} \cdot R_2$$

Date: / /  
Page No.: TELCO

Date: / /  
Page No.: TELCO

Step II - Finding  $R_{Th}$

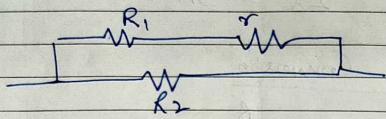

$$R_1 = \frac{1}{r} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1 + r} + \frac{1}{R_2}$$


$$\frac{1}{R} = \frac{R_1 + R_2 + r}{R_2(R_1 + r)}$$

$$R_{Th} = \frac{R_2(R_1 + r)}{R_1 + R_2 + r}$$

$$\frac{1}{R} = \frac{R_1 + R_2}{R_1 R_2}$$



$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

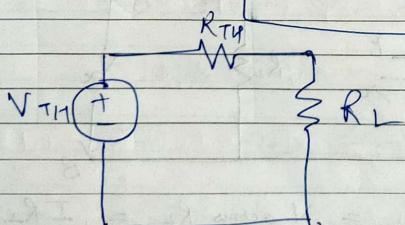

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

E3.12

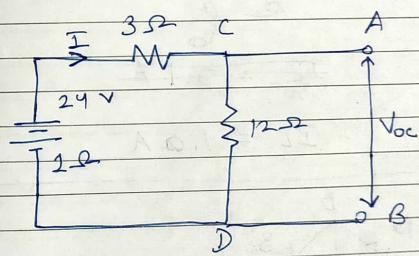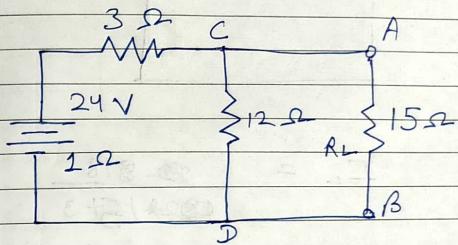

$$V_{Th} = I \times 12$$


$$V_{Th} = \frac{24}{16} \times 12$$

$$V_{Th} = 18 \text{ V}$$

$$R_{Th} = \frac{12(16)}{164}$$


$$R_{Th} = 3 \Omega$$



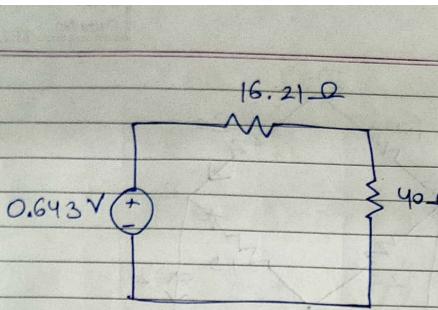

$$I_L = \frac{0.643}{16.21 + 40}$$

$$I_L = 0.0114 \text{ A}$$

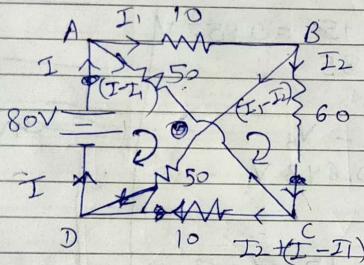

In BDCB,

$$-I_2 \times 60 - 10[I_2 + I - I_1]$$

$$+50(I_1 - I_2) = 0$$

$$-60I_2 - 10I_2 - 10I + 10I_1 + 50I_1 - 50I_2 = 0$$

Date: / /  
Page No.: TELCO

$$\begin{aligned} 50I_1 - 120I_2 &= 0 \\ \Rightarrow 5I_1 - 12I_2 &= 0 \quad (1) \\ \text{In ACDA,} \\ -50(I - I_1) - 10(I_2 + I - I_1) \\ + 80 &= 0 \end{aligned}$$

$$\begin{aligned} \Rightarrow 50I - 50I_1 + 10I_2 + 10I - 10I_1 &= 80 \\ 50I - 40I_1 + 10I_2 &= 80 \quad (2) \\ \text{In ABDA,} \\ +50(I_1 - I_2) - 50I_1 + 80 &= 0 \\ -10I_1 - 50(I - I_2) + 80 &= 0 \end{aligned}$$

$$\begin{aligned} +10I_1 + 50I - 50I_2 &= 80 \quad (3) \\ I_1 + 5I - 5I_2 &= 80 \\ \text{In ABCA,} \\ -10I_1 - 60I_2 - 50(I - I_1) &= 0 \\ +10I_1 + 60I_2 + 50I - 50I_1 &= 0 \\ 50I - 40I_1 + 60I_2 &= 0 \quad (4) \\ 5I - 4I_1 + 6I_2 &= 0 \end{aligned}$$

$$5I_1 - 12I_2 = 0$$

$$3I - 4I_1 + I_2 = 8$$

$$I_1 + 5I - 5I_2 = 8$$

$$5I - 4I + 6I_2 = 0$$


$$(1) - (2)$$

$$5I_2 = -8$$

$$I_2 = \frac{8}{5}$$

$$I_2 = 1.6 \text{ A}$$

Finding Thevenin's Voltage

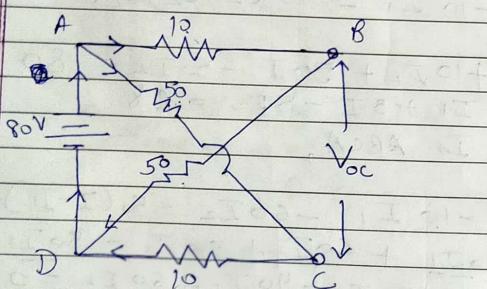

In loop ABDA,

$$V_{\text{at } B} = 80 \times \frac{50}{50+10}$$

(Using Voltage Divider formula)

$$V_B = 80 \times \frac{50}{60}$$

$$V_B = \frac{60}{66.66} \text{ V}$$

In ACDA,


$$V_C = 80 \times \frac{10}{60}$$

$$V_C = 13.33 \text{ V}$$

V Across B & C,

$$V_{Th} = V_B - V_C = 53.33 \text{ V}$$

Step II

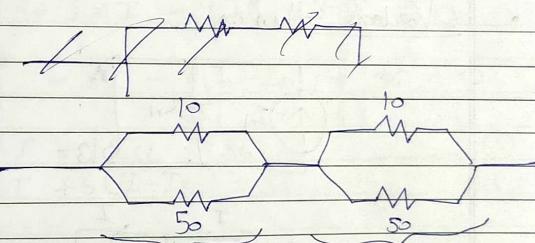


$$\left[ \frac{1}{R_1} = \frac{1}{10} + \frac{1}{50} \right] + \left[ \frac{1}{R_2} = \frac{1}{10} + \frac{1}{50} \right]$$

$$\Rightarrow \frac{1}{\left( \frac{60}{500} + \frac{60}{500} \right)}$$

~~R<sub>Th</sub> = 0.25 Ω~~




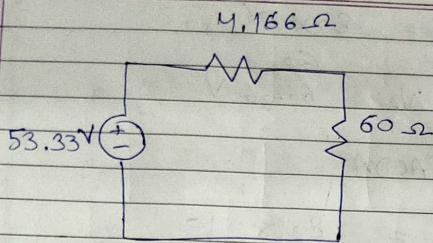
$$R_{Th} = 4.166 \Omega = \frac{25}{6} \Omega$$



$$I_L = \frac{53.33}{60 + 4.166}$$

$$I_L = 0.83 A$$

### Norton's Theorem

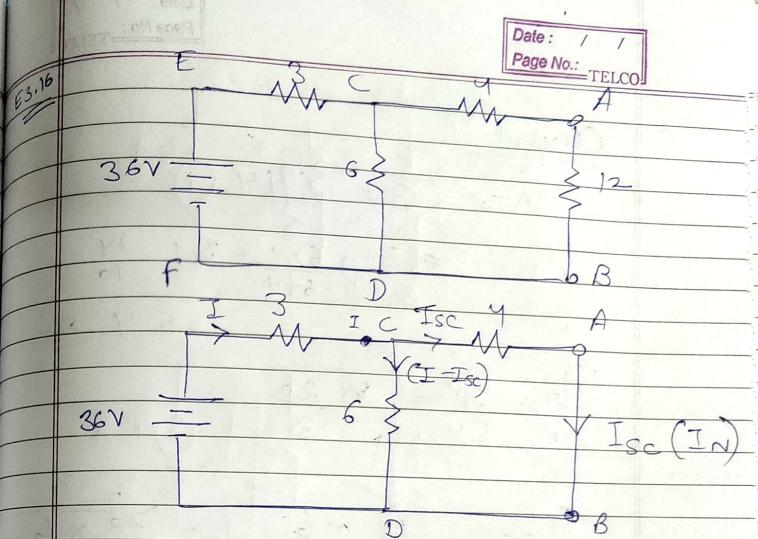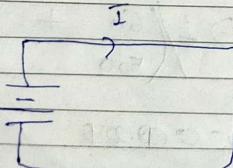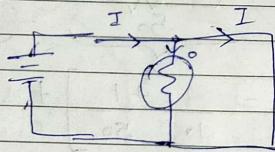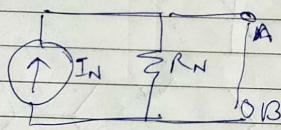

$$I = -3I - 4I_{SC} + 36 = 0$$

$$-3I - 6(I - I_{SC}) + 36 = 0$$

$$3I + 4I_{SC} = 36 \quad (1)$$

$$3I + 6(I - I_{SC}) = 36 \quad (2)$$

$$\begin{aligned} (2) - (1) \\ 6(I - I_{SC}) - 4I_{SC} = 0 \\ 6I - 6I_{SC} - 4I_{SC} = 0 \end{aligned}$$

$$\begin{aligned} 6I &= 10I_{SC} \\ 3I &= 5I_{SC} \end{aligned} \quad (3)$$

$$-4I_{SC} + 6(I - I_{SC}) = 0$$

$$6I - 6I_{SC} - 4I_{SC} = 0$$

$$8I = 10I_{SC}$$

Current

$$R_{TOT} = 3 + 6 \parallel 4$$


$$= 3 + \frac{6 \times 4}{6+4} = 3 + \frac{24}{10} = 5.4 \Omega$$

$$I = \frac{36}{5.4} = 6.67 A$$

$$I_{SC(4\Omega)} = \frac{6}{6+4} = \frac{6}{10} = 0.6 A$$

$$I_{SC(6\Omega)} = I \times \frac{4}{6+4} = 6.67 \times \frac{4}{10} = 2.67 A$$


$$I_{SC} = 0.6 + 2.67 = 3.27 A$$

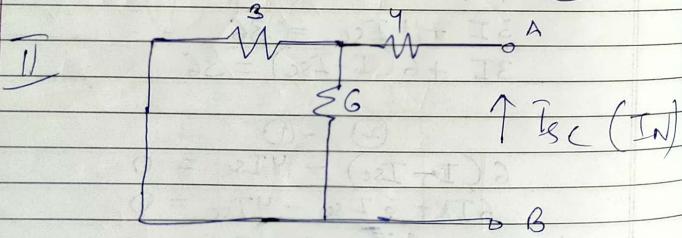

GEF 81K4

$$4 + 3 \parallel 6$$


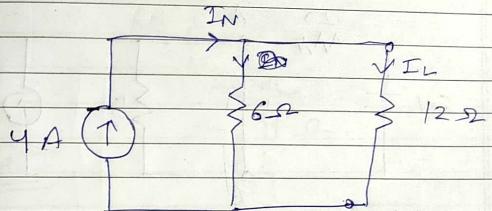
$$= 4 + \frac{3 \times 6}{3+6} = 4 + \frac{18}{9} = 6.67 A$$



$$IL = \frac{4 \times 6}{6+12}$$

$$= 4 \times \frac{6}{18} = 1.33 A$$

$$= 1.33 A$$

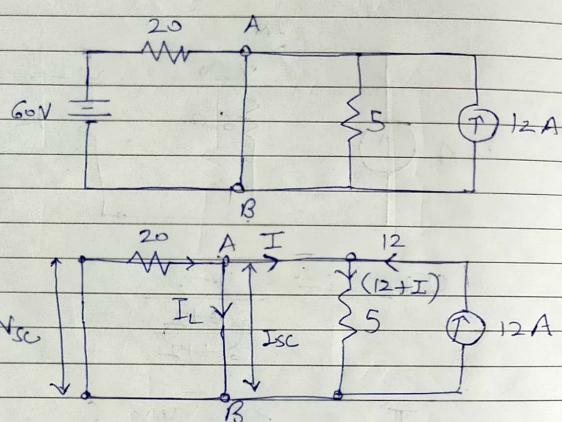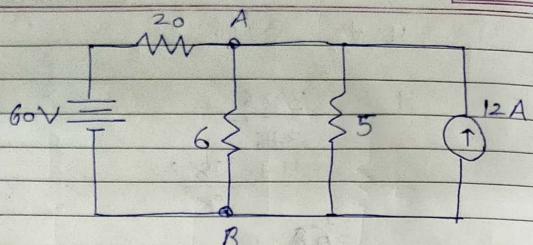


$$\text{Step I} \quad \underline{\underline{I_{SC} =}} \quad I_L = \frac{\sqrt{sc}}{R}$$

$$I_L = \frac{64}{12} 3$$


$$I_L = 3A$$
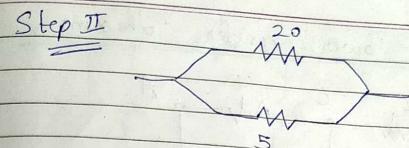
$$\therefore I_{Sc} = I_L + I_2 = 3 + 12 \\ = 15 \text{ A}$$






$$R_{SC} = \frac{20 \times 5}{245} = \underline{\underline{60}} \\ \underline{\underline{17}}$$

$$R_{SC} = \frac{0.520}{0.25} = 2.08$$

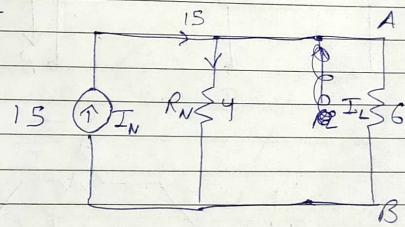

$$I_L = \frac{15 \times 4}{4+6} = 6 A$$


### Maximum Power Transfer Theorem

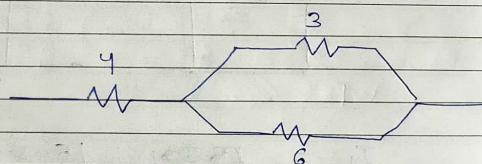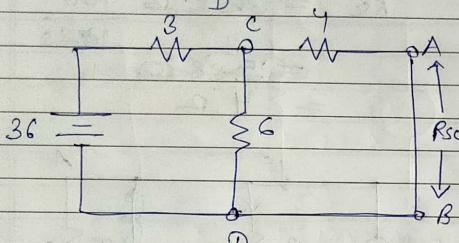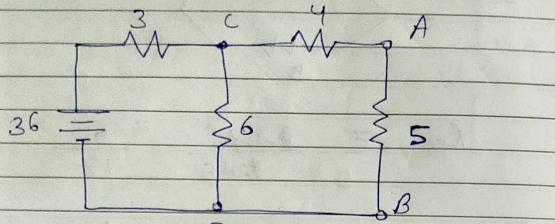




$$R_{eqL} = 4 + \frac{3 \times 6}{3+6}$$

$$= 4 + \frac{18}{9}$$

$$= 6 \Omega$$

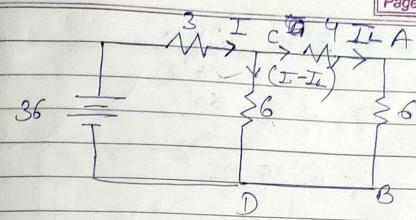

$$\frac{36}{3}$$

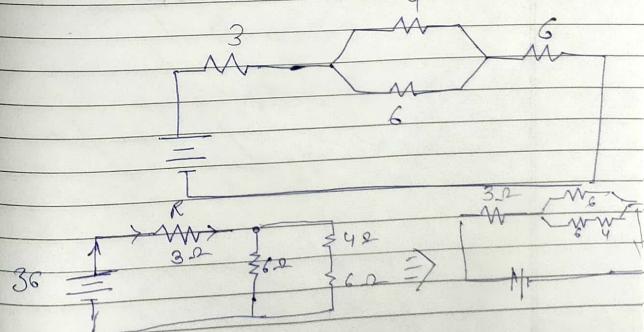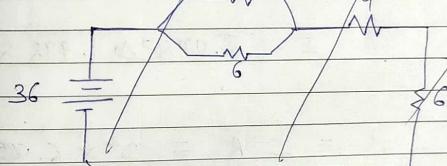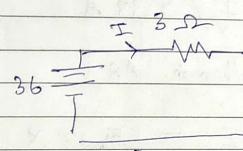

$$R = 3 + \frac{6 \times 10}{6+10}$$

$$= 3 + \frac{60}{16}$$

$$= 6.75 \Omega$$

$$I = \frac{36}{6.75}$$

$$I = 5.33 A$$

$\therefore$  Through AB,

$$I = 5.33 \times \frac{6}{10+6}$$



$$I = 1.998 \approx 2 A$$

$$P = I^2 R = 2^2 \times 6.75$$



$$= 27 W$$

Date: / /  
Page No.: TELCO

Date: / /  
Page No.: TELCO

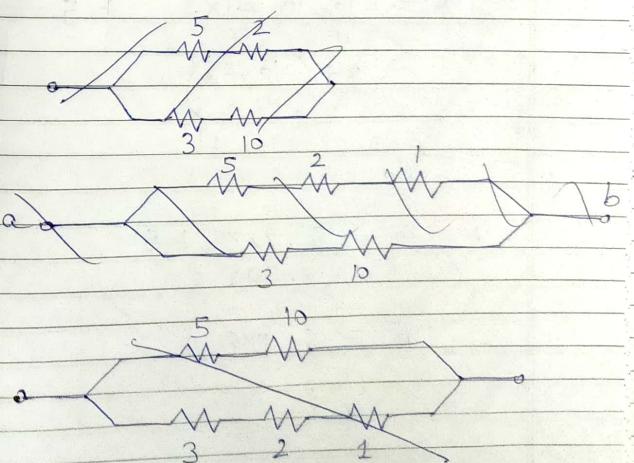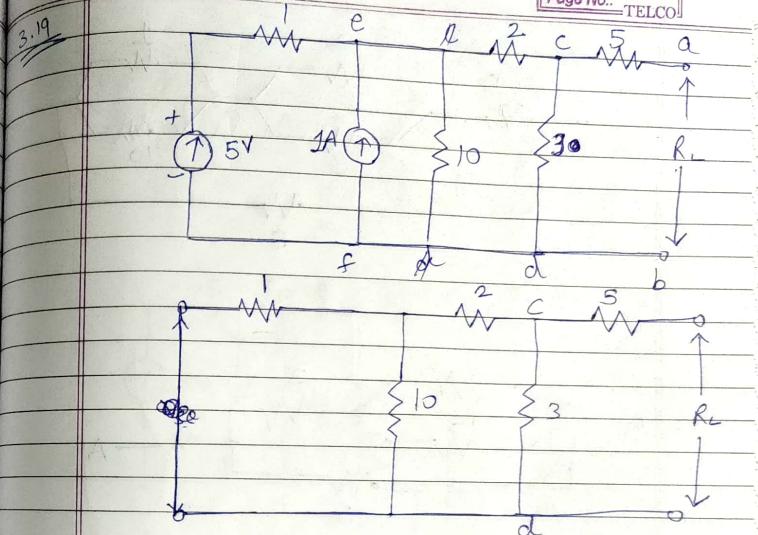

Date : / /  
Page No.: TELCO



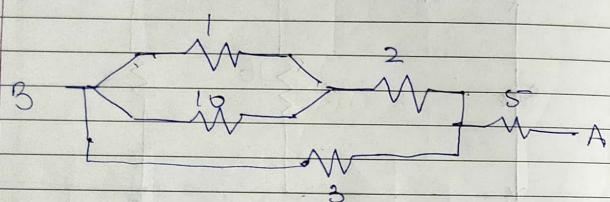
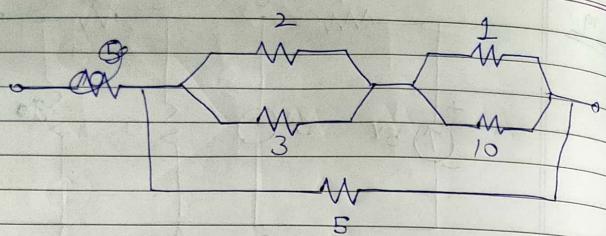



$$R = \frac{\left(\frac{10}{11} + 2\right) \times 3}{3 + \left(\frac{10}{11} + 2\right)} + 5$$

$$R = \frac{8.727}{5.909} + 5$$


$$R = 6.476 \Omega$$

Date : / /  
Page No.: TELCO

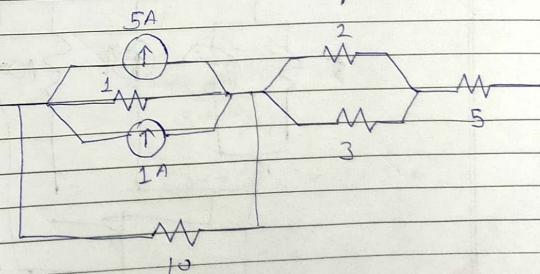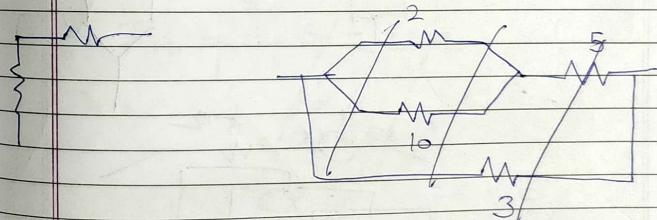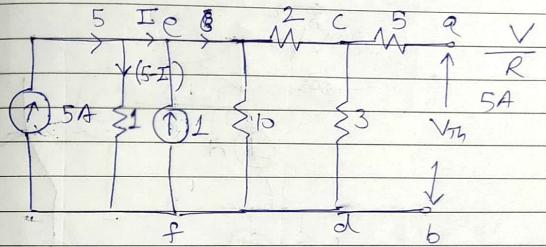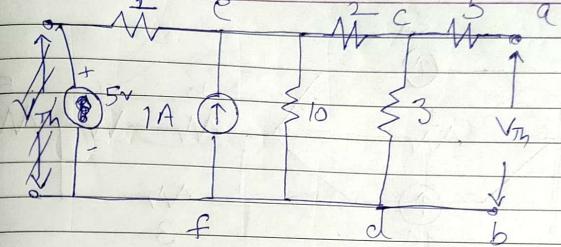

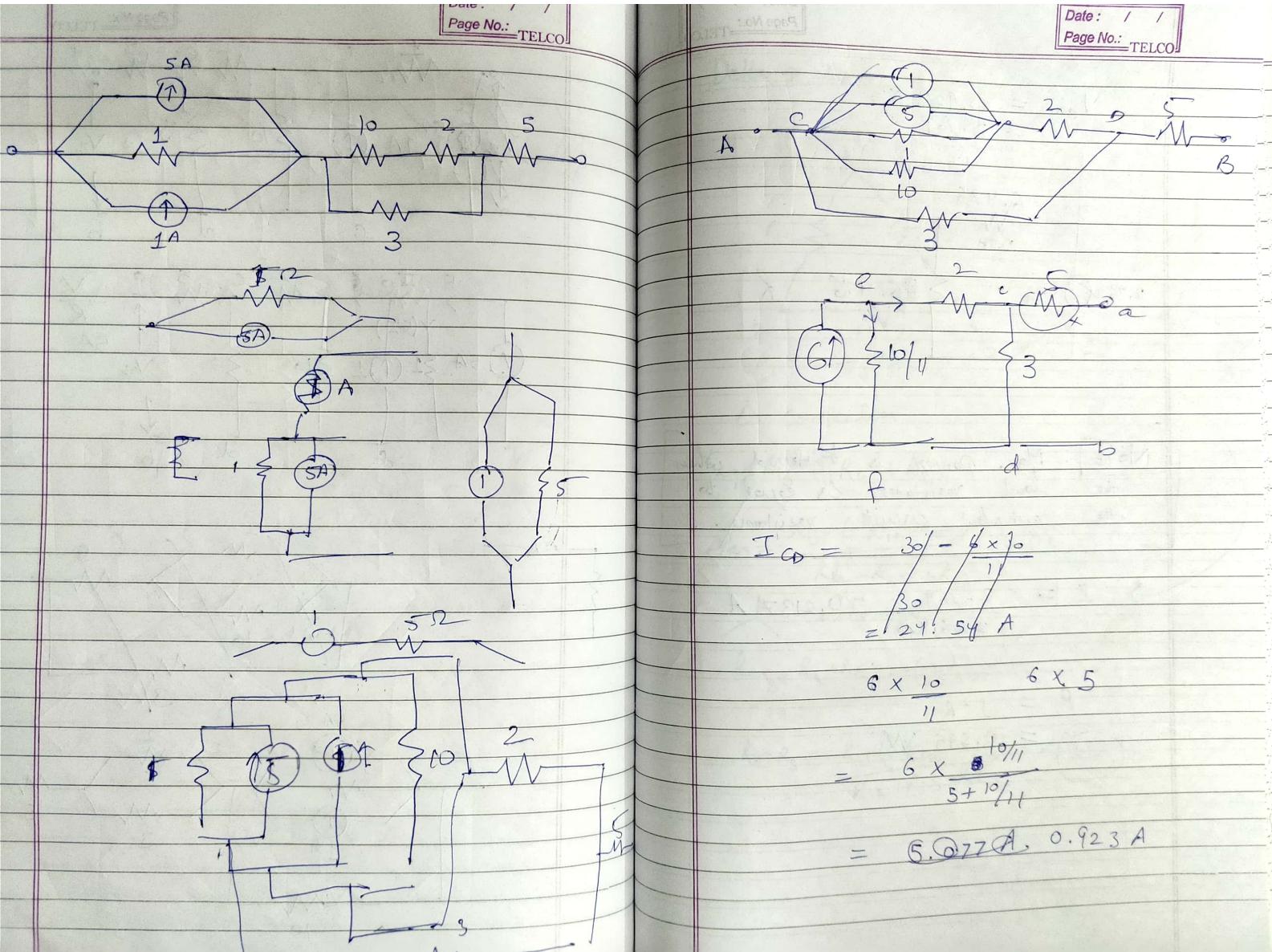

$$V_{CD} = 0.923 \times 3 \\ = 2.769$$

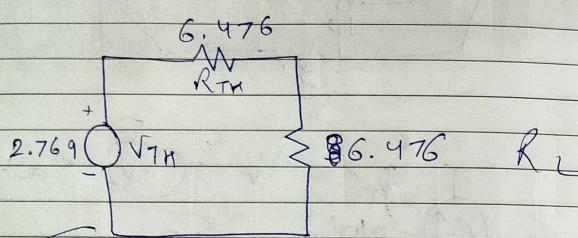


**NOTE:** Max. power is transferred when the load resistance is equal to the equivalent circuit resistance.

$$I = \frac{2.769}{2 \times 6.476} = 0.2137 A$$

$$P = I^2 R \\ = 0.295 W$$

10/9/17 Delta  $\rightarrow$  Star

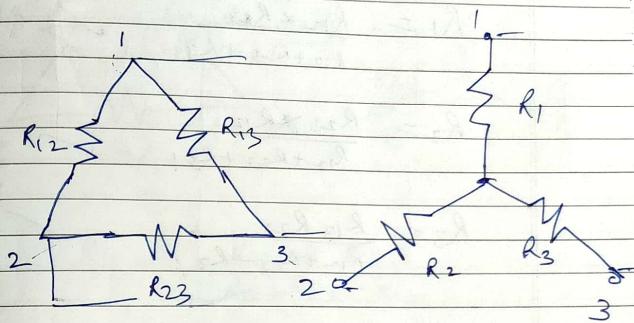

$\Delta$  Connection

$$R_{eq} = R_{13} \parallel (R_{12} + R_{23})$$

$$R_{eq} = \frac{R_{13} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{13}} \quad \text{--- (1)}$$

$\star$  Connection

$$R_{eq} = R_1 + R_3 \quad \text{--- (2)}$$


$$R_1 + R_3 = \frac{R_{13} (R_{12} + R_{23})}{R_{12} + R_{13} + R_{23}} \quad \text{--- (1)}$$

$$R_1 = \frac{R_{12} \times R_{13}}{R_{12} + R_{13} + R_{23}}$$

$$R_2 = \frac{R_{23} \times R_{12}}{R_{12} + R_{23} + R_{13}}$$

$$R_3 = \frac{R_{13} \times R_{23}}{R_{13} + R_{23} + R_{12}}$$


Star - Delta

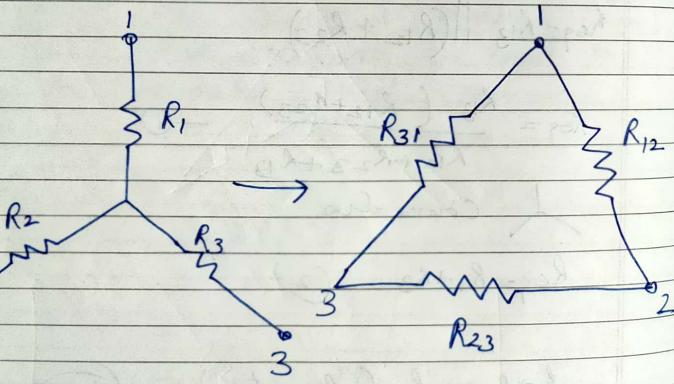

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$
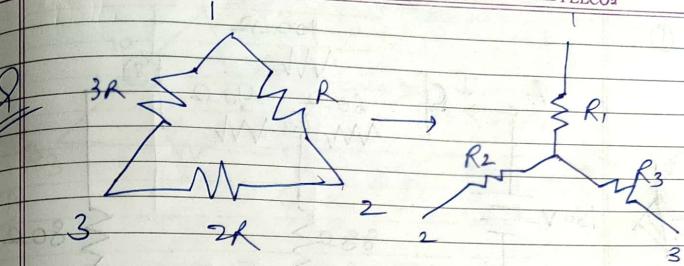
$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$



$$R_1 = \frac{R_{12} \times R_{13}}{R_{12} + R_{13} + R_{23}}$$


$$= \frac{R \times 3R}{R+2R+3R} = \frac{3R^2}{6R} = \frac{R}{2}$$

$$R_2 = \frac{R_{12} \times R_{23}}{R_{12} + R_{23} + R_{13}}$$

$$= \frac{R \times 2R}{R+2R+3R} = \frac{2R^2}{6R} = \frac{1}{3} R$$




$$R_3 = \frac{R_{23} \times R_{13}}{R_{12} + R_{23} + R_{13}} = \frac{2R \cdot 3R}{R+2R+3R} = \frac{6R^2}{6R} = R$$

∴ Equivalent Star connection:

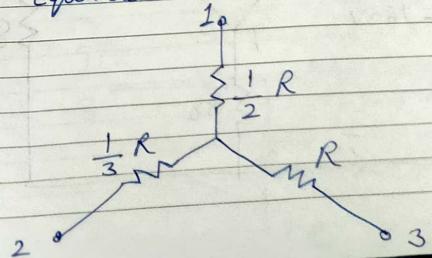


Date: / /  
Page No.: TELCO

Q.

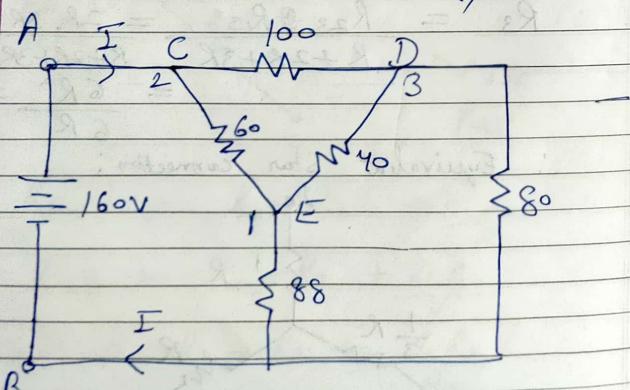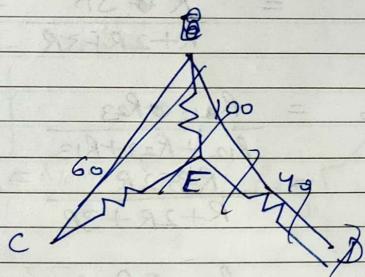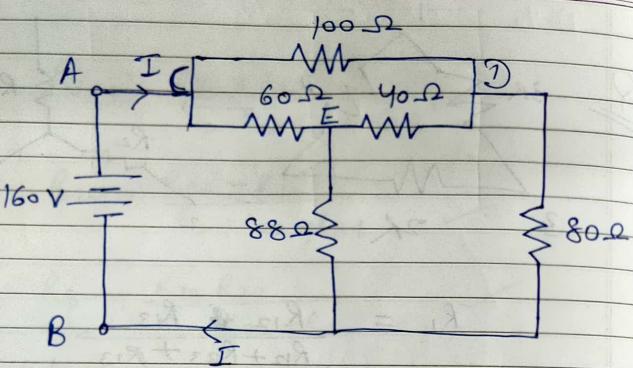

Date: / /  
Page No.: TELCO

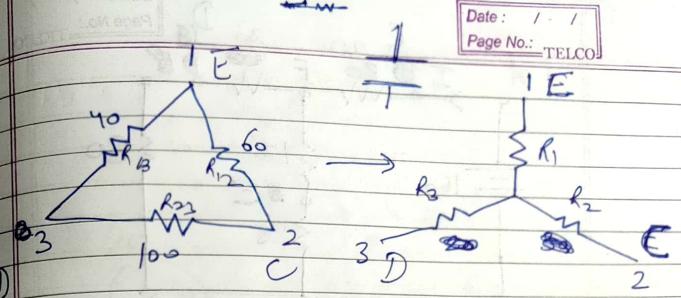

$$R_{1E} = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{23} + R_{31}} = \frac{60 \cdot 40}{60 + 40 + 100}$$


$$= \frac{2400}{200} = 12 \Omega$$


$$R_{2E} = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{60 \cdot 100}{200}$$

$$= \frac{6000}{200} = 30 \Omega$$




$$R_{3E} = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{40 \cdot 100}{200}$$

$$= \frac{4000}{200} = 20 \Omega$$

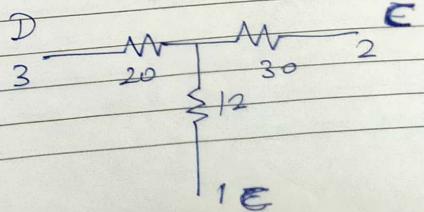

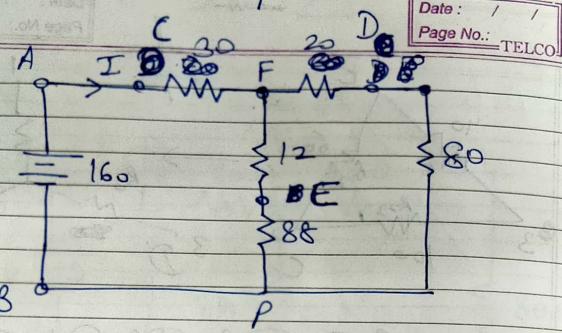
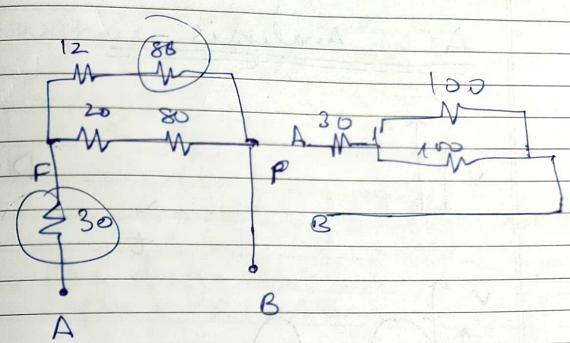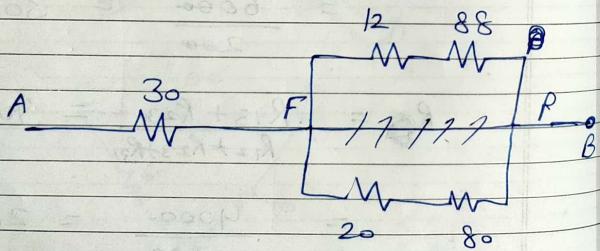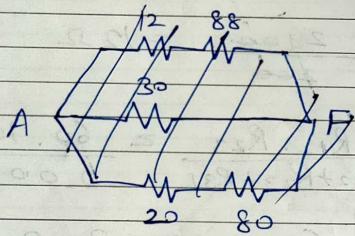
$$\Rightarrow \frac{30}{(30+20)} \parallel \frac{12}{(12+88)} \parallel \frac{80}{(20+80)}$$



$$30 + \frac{(20+80)}{(20+80) + (12+88)}$$

$$= 30 + \frac{100 \times 100}{100 + 100}$$

$$= 30 + \frac{10000}{200}$$

$$= 80 \Omega$$

$$I = \frac{160}{80} = 2A$$