

7/3/17

UNIT - 3


DATE _____
PAGE _____

TRANSISTORS

B J T

Bipolar
(both holes &
electrons)


Junction Transistor
(Resistance)

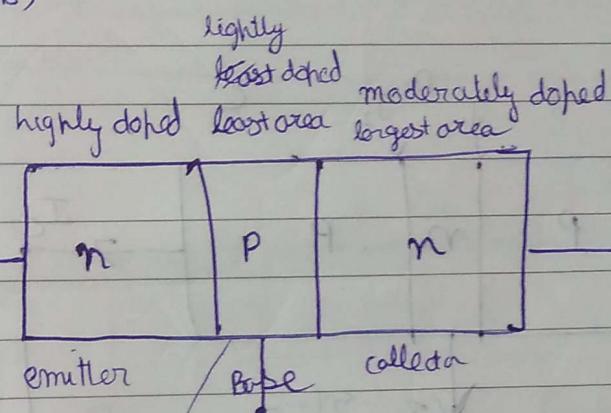

least area & hole bcoz it offers high resistance.


Collector - largest area for heat dissipation

Diagram

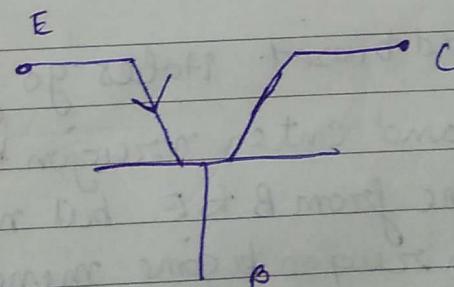

Pointing on

PnP

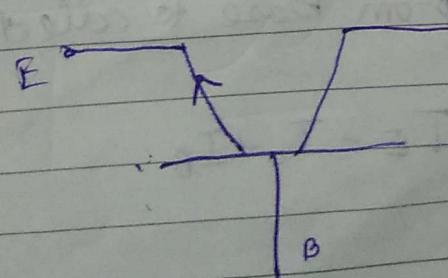


not pointing in

npn

Biasing is done to obtain the operating point of a device.

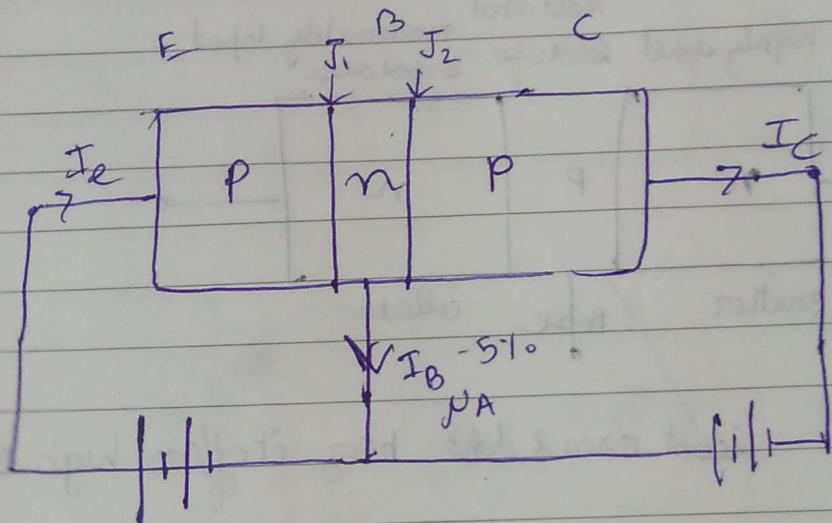Always Emitter base junction is forward biased and CB junction is reverse biased
 collector base



V_{EB}
or
 V_{EE}

$$I_B = 5 \text{ mA}$$

95% transferred

E B is forward biased. Holes go from P to n or

E to B and enter n region by crossing J_1 .
 I^e also come from B to E but negligible. Now
 holes of p region become minority of n region.
 So J_2 is reverse biased hence minority carriers
 (holes) go from base to collector.

$$I_E = I_B + I_B$$

Amplifier


$$V_o = I_c \times 100 \text{ k}\Omega$$

(2000 V)

$$I_E = I_C = 20 \text{ mA}$$

$$R_{\text{output}} = 100 \text{ k}\Omega \text{ by } R_E$$

If $I_B = 0$, $R_E = 10 \Omega$ (small)

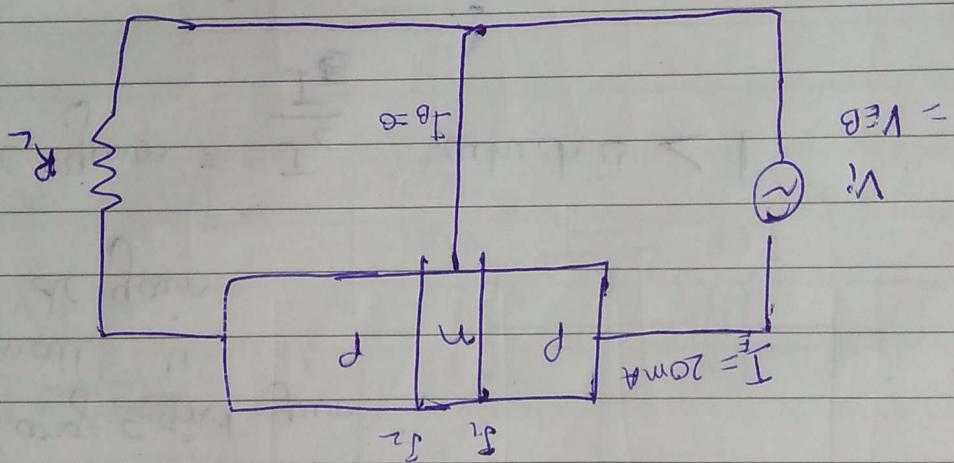

~~q13) 17~~

$$I_C = I_{C(\text{magenta})} + I_{C(\text{O})}$$

when E.B is not biased and C.B is grounded biased
numerically sum of flows called $I_{C(\text{O})}$.

(grounded)

components of I_C



Transistor current Equation

$$I_c = \alpha I_e + I_{c0}$$

in active region

α = current gain

↓
3 types
↓

- ① Large Signal gain
- ② Small " "
- ③ dc gain

$$\text{dc gain} = \frac{I_c}{I_E} \quad \text{which is } < 1$$

($b \log I_E \approx I_C$)
always

$$\text{Large Signal gain} - \alpha = \frac{I_c - I_{c0}}{I_E - 0}$$

~~or~~ ratio of gain in I_c when I_E is changed


$$\alpha_{\text{small}} \text{ or } \alpha_{\text{ac}} = \frac{\Delta I_c}{\Delta I_E}$$

Configurations

The side which is common is grounded

CB


- Common Base

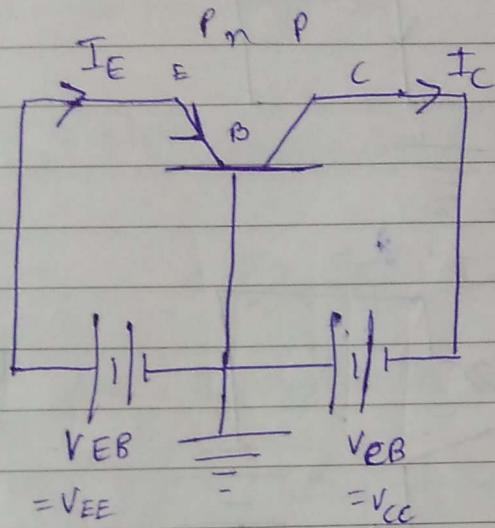Input characteristic
 I_E & V_{EB}

Output char

 I_C & V_{CB}


$$0.9 < \alpha < 0.99$$


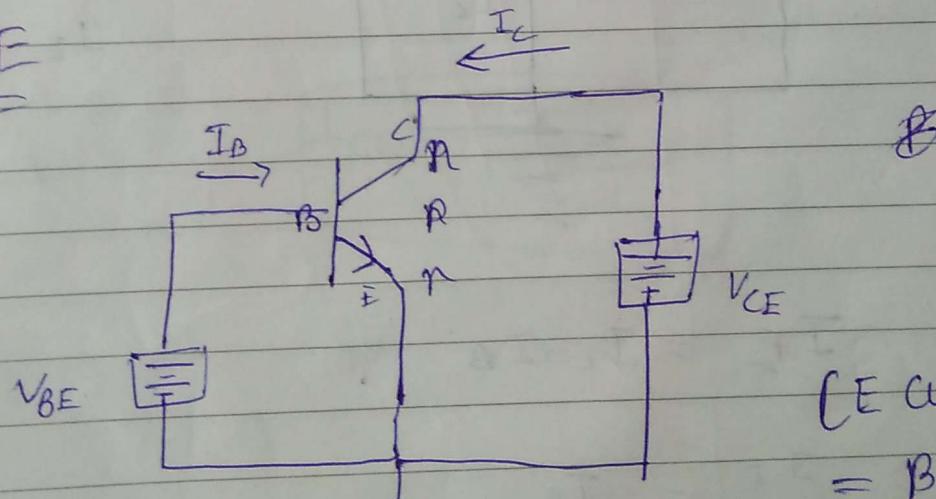
CE

CE current gain

$$\beta = \frac{I_C}{I_B} \gg 1$$

$$50 < \beta < 100$$

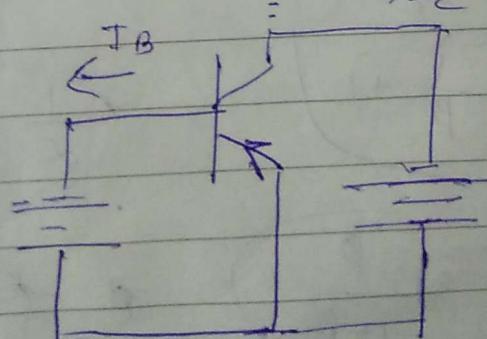

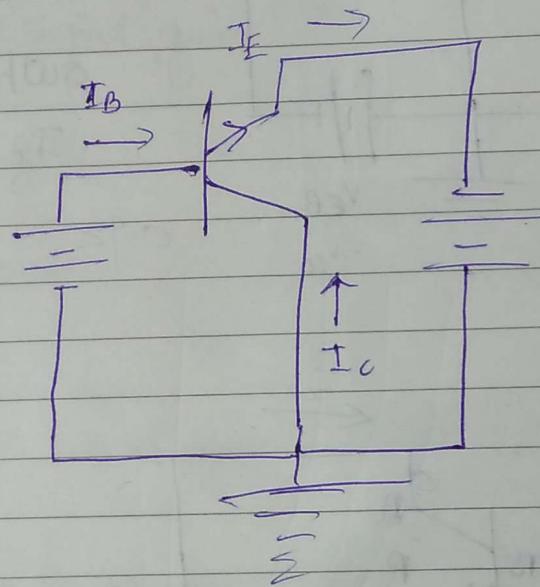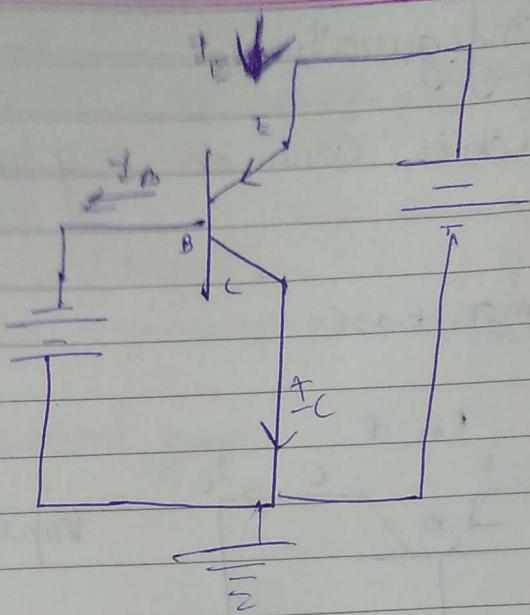

Input

I_B, V_{CB}

Output

I_E, V_{CE}

$$I_E = I_C + I_B$$

$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$$

$$\frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\frac{1}{\alpha} = \frac{1 + \beta}{\beta}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

use this

$$\beta = \frac{\alpha}{1 - \alpha}$$

Current equation

$$\left. \begin{array}{ll} CB & I_C = \alpha I_E + I_{CBO} \\ CE & I_C = \beta I_B + I_{CEO} \end{array} \right\} \begin{array}{l} \text{(Common Base are reverse} \\ \text{saturation current)} \\ \text{when Emitter is open} \\ \text{Open:} \end{array}$$

(1) (2)

\rightarrow putting value of I_E in (1)

Common emitter reverse
saturation current
when Base is open

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$(1-\alpha) I_C = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1-\alpha} I_B + \overbrace{I_{CBO}}^{1-\alpha}$$

Comparing with (2)

$$I_{CEO} = \frac{I_{CBO}}{1-\alpha}$$

10/31/17



DATE _____
PAGE _____

Characteristics

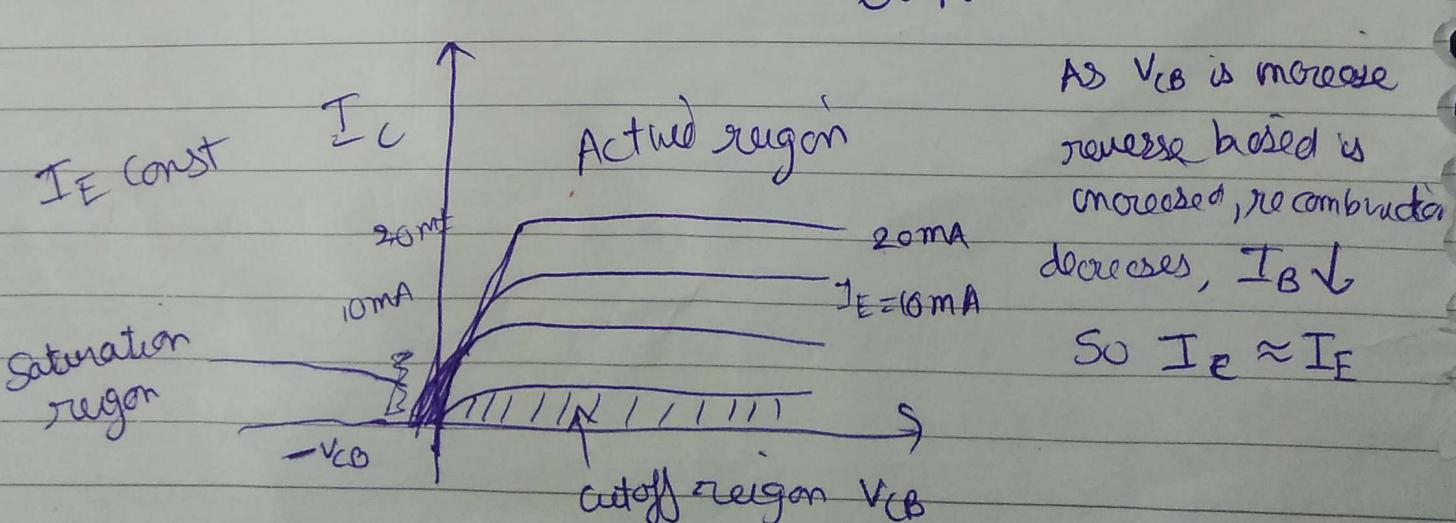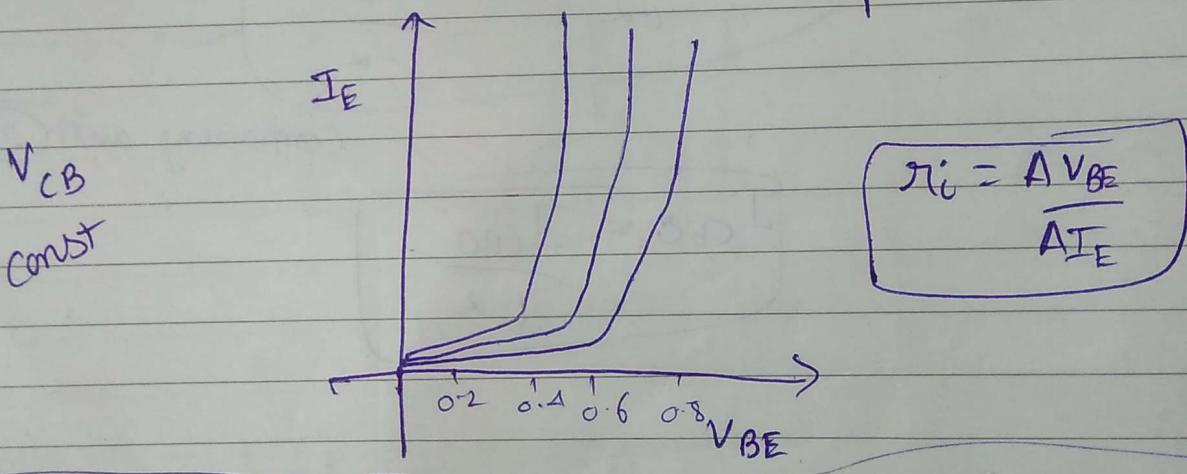- 1.) Input or Driving point char - x axis pe
input voltage, y axis pe input current
(when output voltage is constant)
- 2.) Output or collector char - output voltage on
x axis, current on y axis (when input
current is constant)

Common Base

AS V_{CB} is increased, R_B increases
recombination less, resistance less
 I_E increases & becomes steeper as V_{BE} increases
Input



With Active region - EB is FB
CB is RB



Cutoff EB & CB are RB

Saturation EB & CB both FB

DATE _____
PAGE _____

For very small, sufficient FB in CB & EB, I_C changes fast & is independent of I_E .


Common-emitter

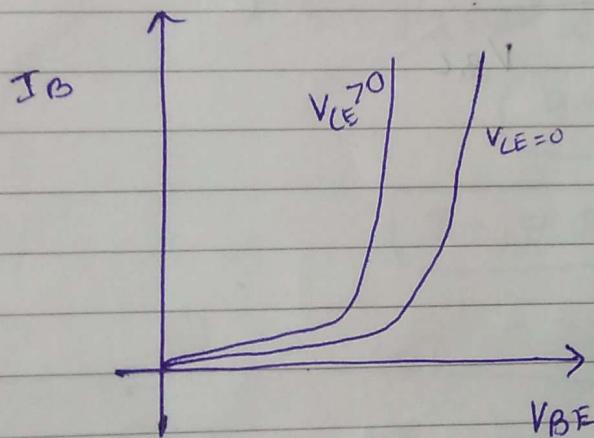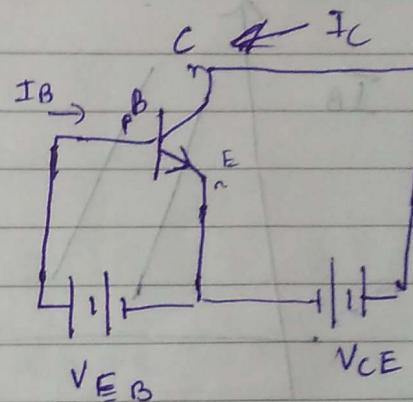

$$V_{EB} = -V_E \\ \text{so } V_{BE} = +V_E$$

$V_{CE} = +V_E$
Same as CB or FB diod

Saturation



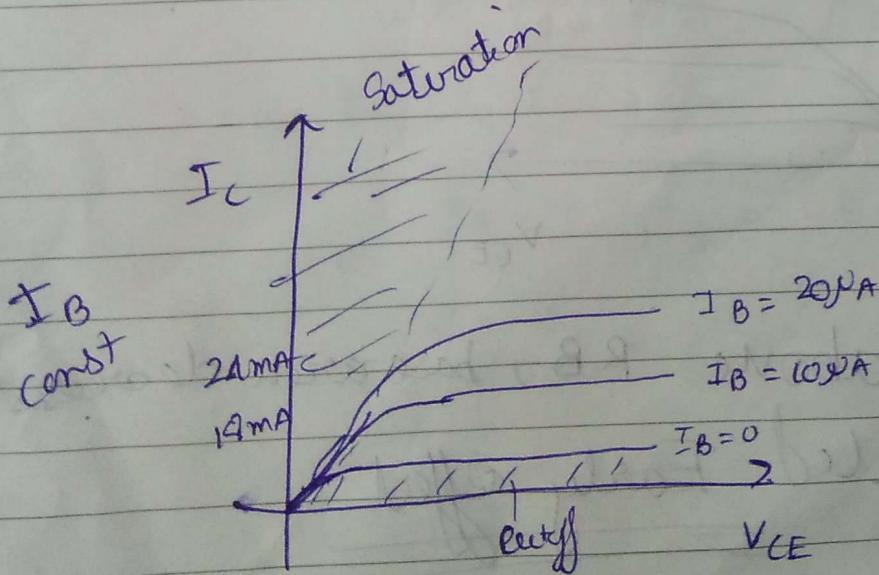


As $\Delta I_B \uparrow$, $R_B \uparrow$
depletion region \uparrow recombination region

so $I_B \downarrow$
(from)

$$I_C \propto I_E$$

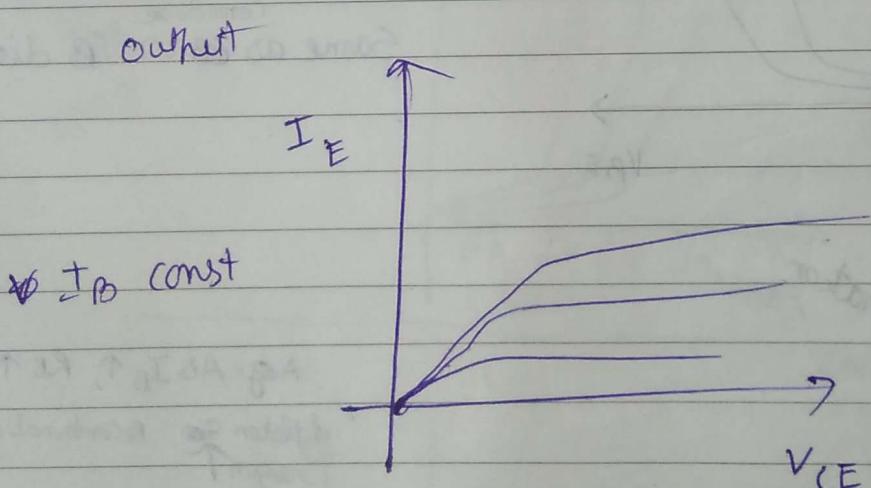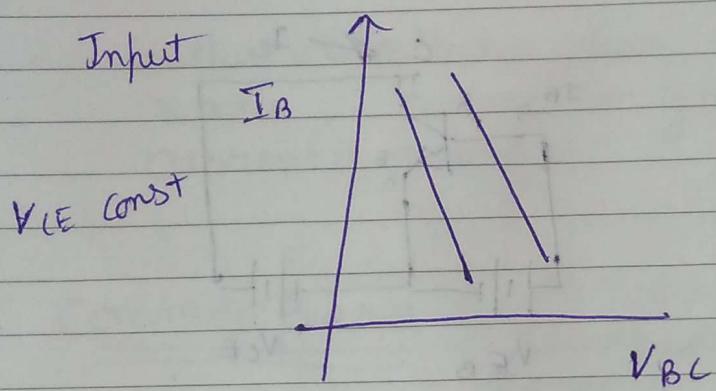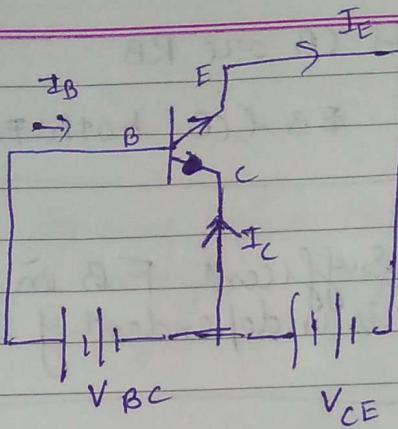Saturation region
At a very small value
 I_C will change fast
& become independent of
 I_B .



All the above RB, base area decreases
shit is called Early effect

14/3/17

$$\beta = \frac{\alpha}{1-\alpha} \quad I_E = I_C + I_B \quad \alpha = \frac{I_C}{I_E} \quad \beta = \frac{I_C}{I_B}$$
$$I_C = \alpha I_E + I_{CBO} \quad I_L = \beta I_B + I_{CEO}$$

DATE _____
PAGE _____

FORMULAS

Ques

$$I_E = 10mA \quad \alpha = 0.98$$

$$I_B + \beta$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\beta = \frac{0.98}{1-0.98} = 49$$

$$\alpha = \frac{I_C}{I_E}$$

$$\alpha I_E = I_C$$

$$10 \times 0.98 \times 0.98$$

$$9.8mA = I_C$$

$$I_B = 0.2mA$$

J2

pnp

$$I_B = 45\mu A \quad I_C = 5.45mA$$

$$\frac{5.45}{0.045} = 121.11$$

α, β, I_E

$$I_E = I_C + I_B = 50.45\mu A + 0.045mA$$
$$I_E = 5.495mA$$

$$\alpha = \frac{I_C}{I_E} = \frac{5.45}{50.45} = \frac{5.45}{5.495} = 0.991$$

$$\beta = \frac{I_C}{I_B} = 121.11$$



Fund I_B for $I_C = 10 \text{ mA}$

at B_{sat} remanence

$$\beta = \frac{I_C}{I_B} = 121.11$$

$$I_B = \frac{10 \times 10^{-3}}{121.11} = \frac{1}{121.11}$$

$$82.56 \mu\text{A}$$

Ques 3 n P n transistor $\alpha = 0.98$, $CBmB$

$$I_E = 3 \text{ mA} \quad I_{CBO} = 10 \mu\text{A}$$

Fund I_B & I_C

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = 0.98 \times 3 + \frac{1}{100}$$
$$= 2.94 + 0.01$$

$$I_C = 2.95 \text{ mA}$$

$$I_B = I_E - I_C$$

$$= 3 - 2.95 = 0.05 \text{ mA}$$

Ques BDATE _____
PAGE _____

$$\beta = \frac{I_C}{I_B}$$

$$I_{CBO} = 12.5 \mu A \quad I_E = 2 \text{ mA} \quad I_C = 1.97 \text{ mA}$$

 $\alpha, \beta \text{ & } I_B$

$$I_B = I_E - I_C = 0.03 \text{ mA}$$

$$\alpha = \frac{I_C}{I_E} =$$

* 1) Whenever Reverse saturation current is given

you cannot use $\alpha = \frac{I_C}{I_E} \text{ & } \beta = \frac{I_C}{I_B} \times$

You can only use equation of reverse saturation

2) β_{DC} or α_{DC}

is direct formula

$$\frac{I_C}{I_B} \text{ & } \frac{I_C}{I_E}$$

But β_{AC} is calculated
using formula
of reverse saturation

$$I_C = \alpha I_E + I_{CBO}$$

$$1.97 = 0.0125 \times 2 \text{ mA} + 0.0125 = \alpha$$

$$\alpha = 0.978$$

$$\beta = \frac{0.978}{1 - 0.978} = 44.45$$

resistance

Ques B

input

output

 V_{BE}

V

Com B

$$R_{in} = \frac{im/p V}{un/p I} = \frac{\Delta V_{BE}}{\Delta I_E}$$

$$R_{out} = \frac{\Delta V_{CB}}{\Delta I_C}$$

Com E

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_B}$$

$$R_{out} = \frac{\Delta V_{CE}}{\Delta I_C}$$

 $\rho \leq$

Com B

$$\Delta V_{BE} = 200 \text{ mV}$$

$$\Delta I_E = 5 \text{ mA}$$

when ~~Base~~ V_{CB} is fixed

$$R_{in} = \frac{200}{5} = 40 \Omega$$

 $\rho \leq$

Com E

$$\Delta V_{BE} = 250 \text{ mV}$$

$$\Delta I_B = 1 \text{ mA}$$

$$R_{in} = 250 \Omega$$

5, we have
its wavele
or a sys
for this
m. mecha
es. It sh
tation is s
elocities
this co
e-Brogl
there s
but of
wave

6.1

The w
the wave
transverse disp
genetic waves,
of the wave fun
be interpreted
probability o
suggested that
near that po
will be found n
connection
ot where
all value

than or equal
consider

$\phi-7$ ΔV_{CE} from 5 to 10V $\Delta I_C = 5 \text{ mA to } 5.8 \text{ mA}$

$$R_{out} = \frac{5}{0.8 \times 10^{-3}} = 6.25 \times 10^3 = 6.25 \text{ k}\Omega$$

 $\phi-8$

$I_E = 5 \text{ mA}$

$I_C = 4.95 \text{ mA}$

$I_B = 0.05 \text{ mA}$

$I_{CEO} = 200 \mu\text{A}$

 β_{dc} , & leakage current I_{CBO}

$I_C = \beta I_B + I_{CEO}$

~~$4.95 - 0.2$~~
 ~~0.05~~

 $\beta_{dc} = 50$ direct formula

$$= \frac{I_C}{I_B} = \frac{4.95}{0.05} = 99$$

$$\alpha = \frac{\beta}{1+\beta} = 0.99$$

$I_{CBO} = (\alpha) I_{CEO}$

$I_{CBO} = 0.001 \times 200 \mu\text{A}$

$(2 \mu\text{A})$

Q-9

Following OBS are data

If emitter open

$$V_{CB} = 10V$$

$$I_{CBO} = 0.25 \mu A$$

Base open

$$V_{CE} = 10V$$

$$I_{CEO} = 25 \mu A$$

$I_E, I_B \neq \alpha$ when $I_c = 1.2mA$

$$I_{CEO} = I_{CBO}$$

$$1 - \alpha = \frac{0.25}{25}$$

$$1 - \alpha = 0.01$$

$$\boxed{\alpha = 0.99}$$

$$I_c = \alpha I_E + I_{CBO}$$

$$-0.0025 + 1.2 = 0.99 I_E$$


$$\boxed{I_E = 1.211 \text{ mA}}$$

$$I_B = I_E - I_c = \boxed{0.011 \text{ mA}}$$


16/31/17


DATE _____
PAGE _____

In h topic missed

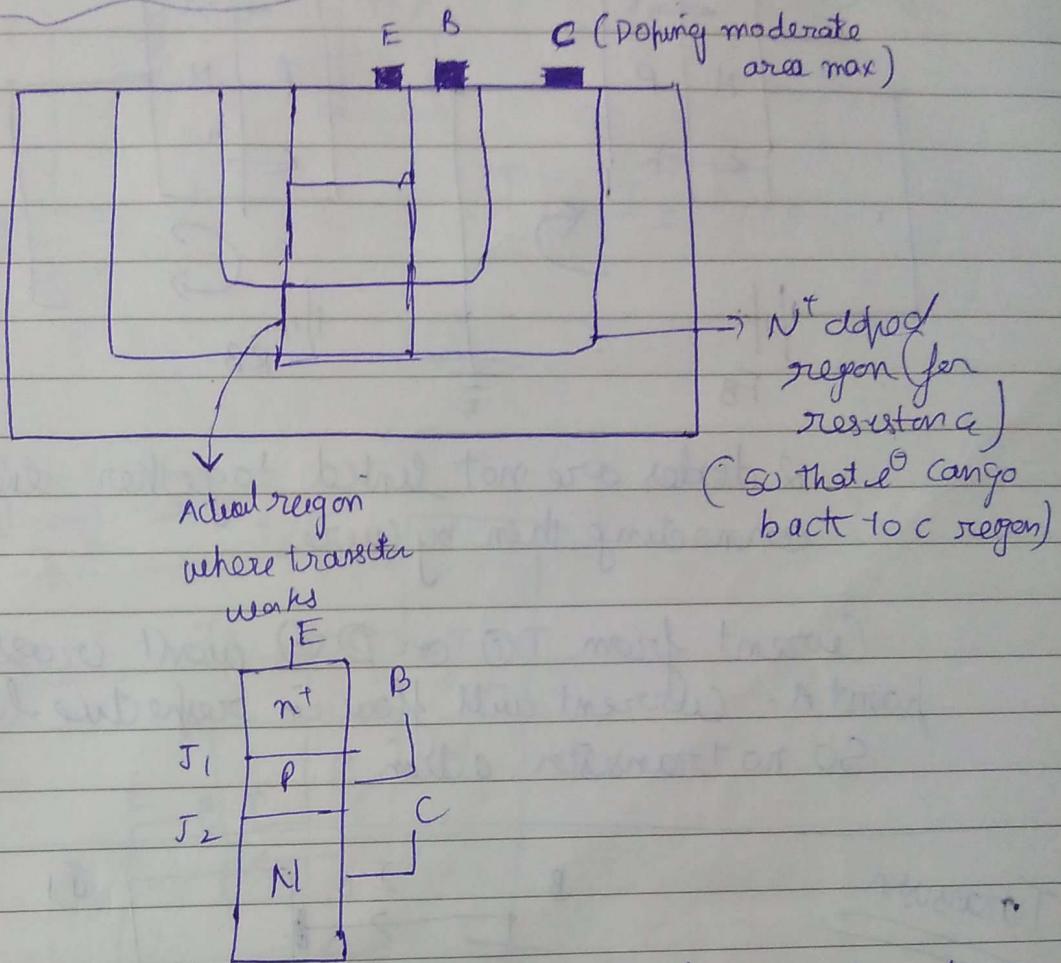

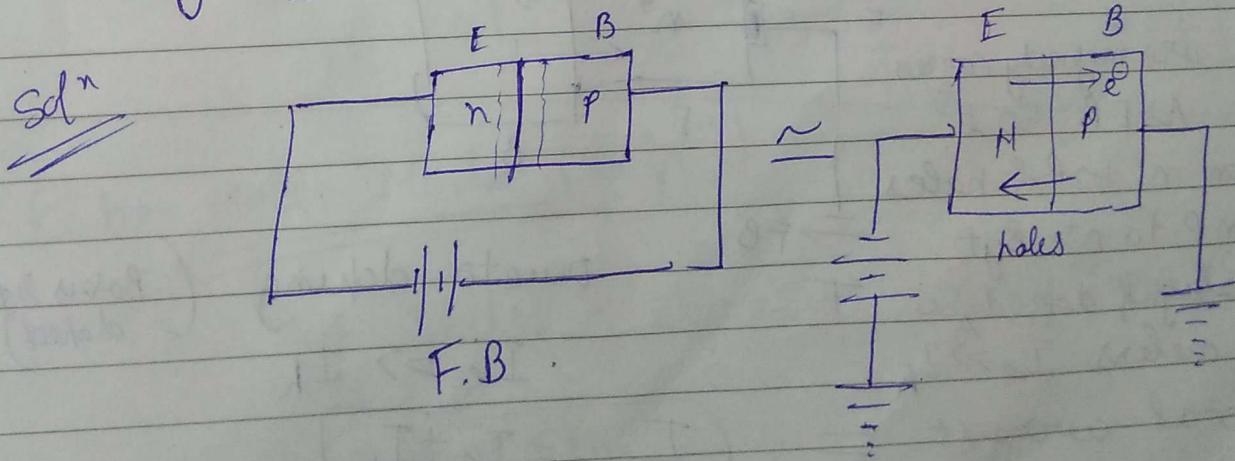* If 2 diodes are connected back to back will it work as transistor ??




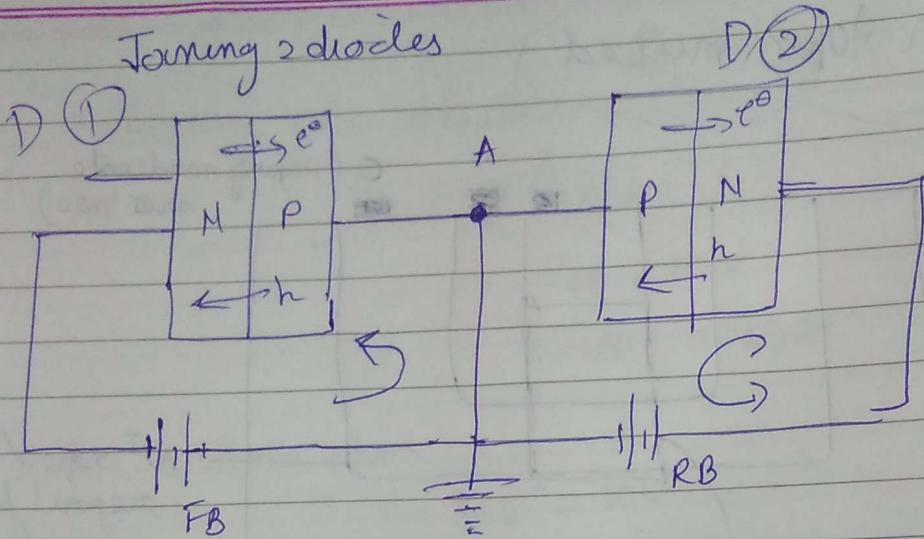

2 diodes are not linked together even by connecting them by wire.

Current from D(1) or D(2) won't cross the point A. Current will flow in respective loops only
So no transistor action.

Transistor

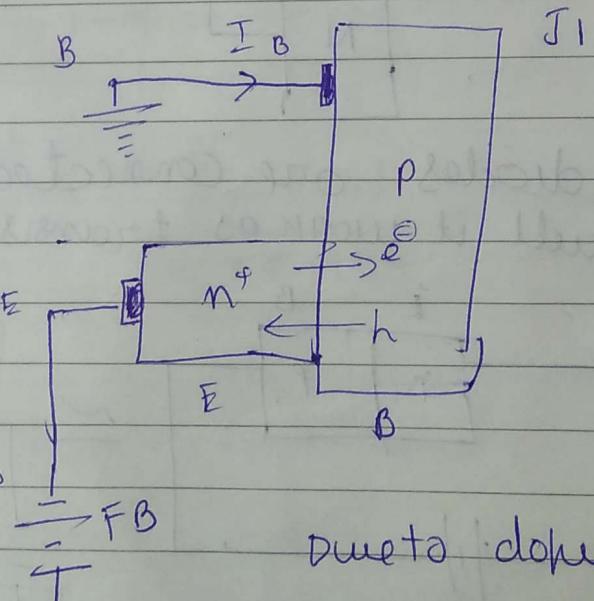

e^- are majority carriers in n^+ . As FB, so e^- go from n^+ to P & holes


from P to n^+ . But Base is lightly doped, so holes are less, $I_e \gg I_h$

Total current =

$$I_T = I_e + I_h$$


Due to doping (Base is lightly doped)

$$I_e \gg I_h$$

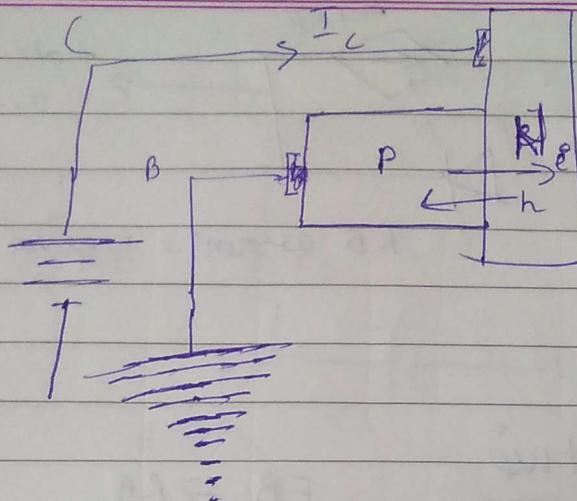

$$I_2 = I_e + I_h$$

After fusing

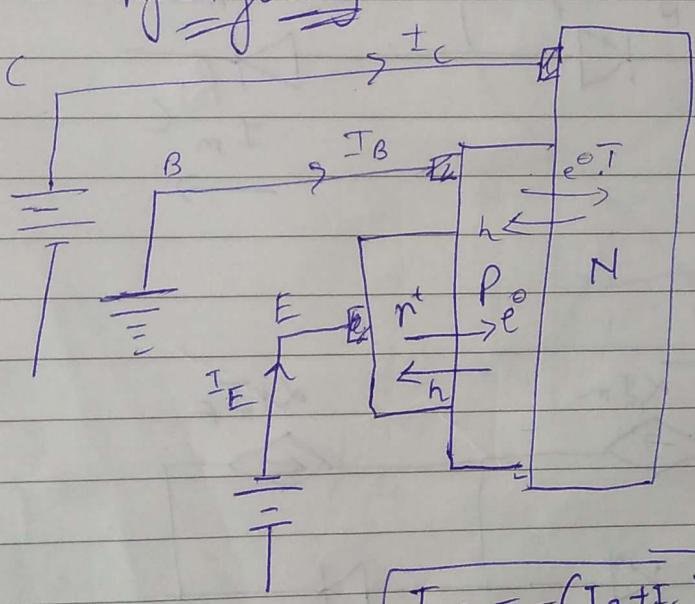


$$I_E = -(I_B + I_C)$$

Fedorov's Model (mhp)

4 states of transistor using 1 model

- Active
- Inverse active
- Saturation
- cutoff

① Active

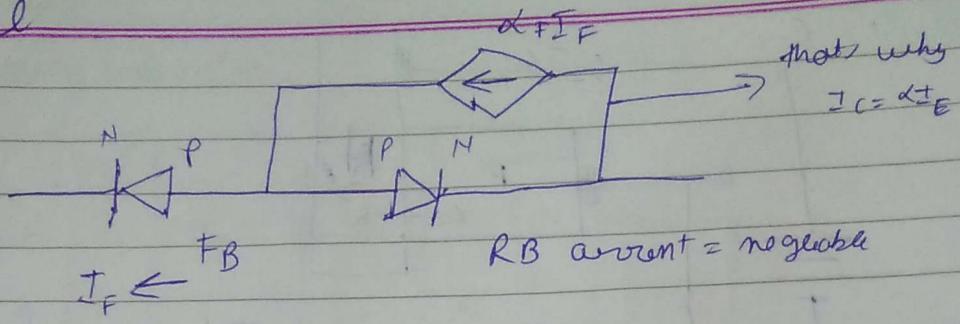


②

Inverse Active


$EB \rightarrow RB$

$B-C \rightarrow FB$

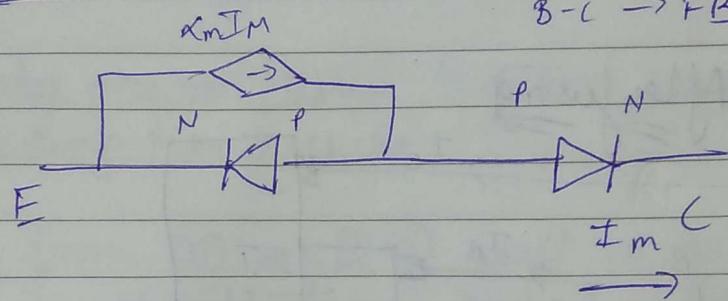


③

Saturated

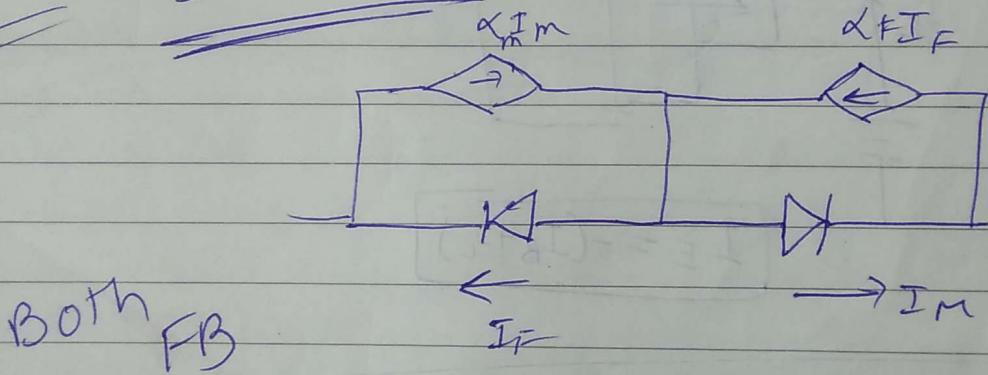

④

~~cutoff~~

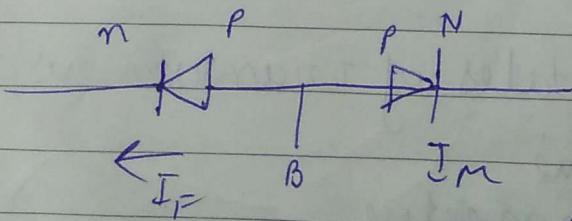

17/3/17


-DC

Common Emitter (emitter is grounded)

PAGE _____

FIXED BIAS

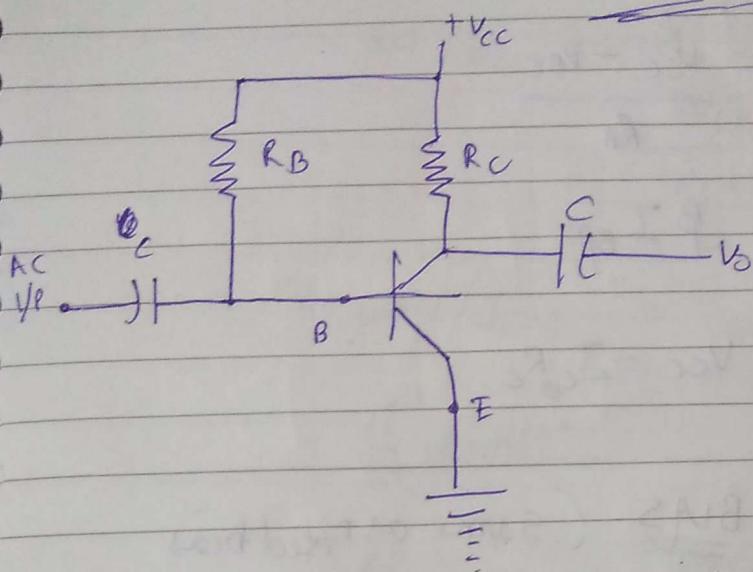
resistor C
resistor B (Identify)
resistor E



(Remove the unnecessary capacitors)

Load line

(All operating points lie on this load line for dc
if for AC it will move near load line)

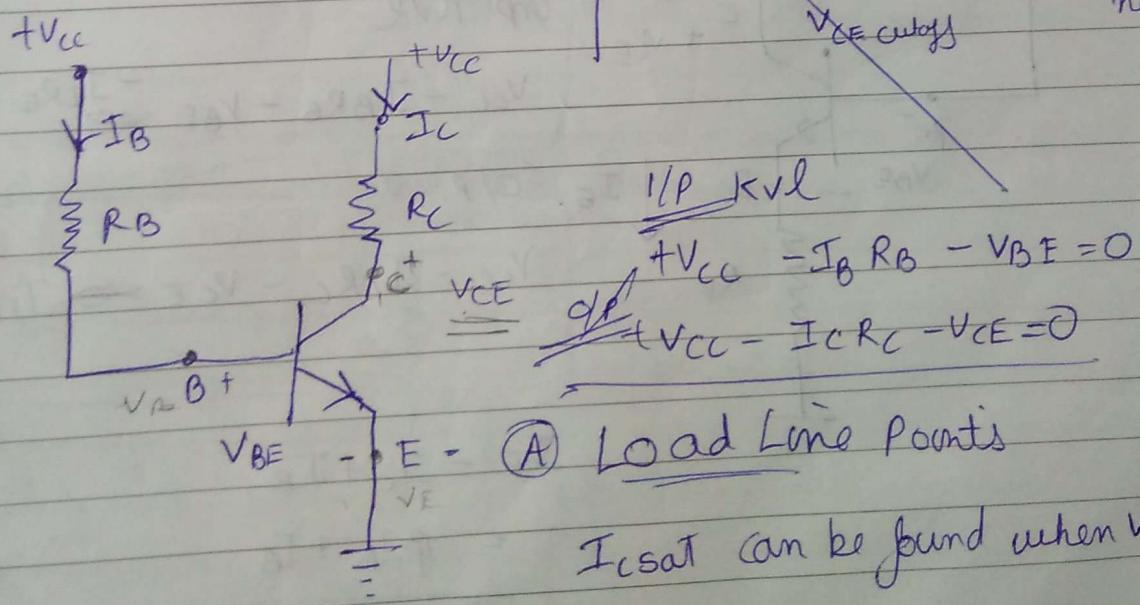I/P KVL

$$\begin{aligned} &+V_{CC} - I_B R_B - V_{BE} = 0 \\ &+V_{CC} - I_C R_C - V_{CE} = 0 \end{aligned}$$

(A) Load Line PointsI_{Csat} can be found when V_{CE} = 0

$$V_{BE} = V_B - V_E$$

$$\left. \frac{I_{C\text{sat}}}{V_{CE=0}} \right| = \frac{V_{CC}}{R_C} \Rightarrow \text{saturation pt}$$

$$\left. \frac{V_{CE\text{cutoff}}}{I_{C=0}} \right| = V_{CC}$$


(B)

$$\textcircled{1} \quad I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\textcircled{2} \quad I_{CQ} = \beta I_{BQ}$$

$$\textcircled{3} \quad V_{CEQ} = V_{CC} - I_{CQ} R_C$$

(better than fixed)

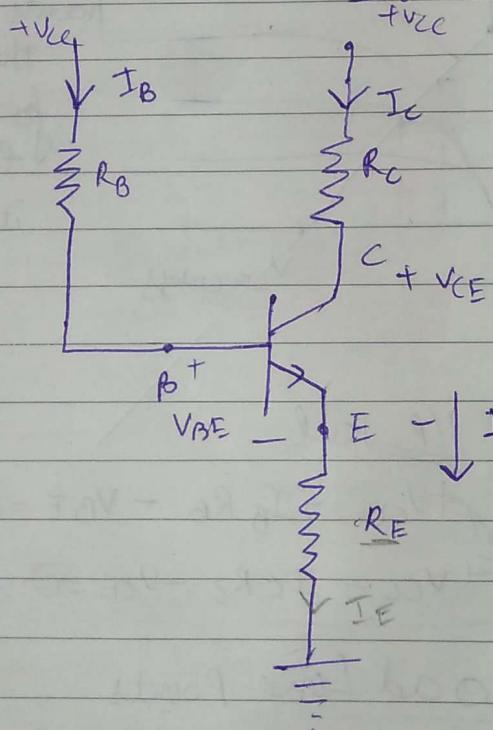EMITTER BIASSELF BIAS(same as fixed bias
just RE added)

Fixed bias is unstable

A resistor is added to
make stable

Q/P KVL

$$V_{CC} - I_{B} R_B - V_{BE} - I_{E} R_E = 0$$

Q/P KVL

$$V_{CC} - I_{C} R_C - V_{CE} - I_{E} R_E = 0$$

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B$$

$$\boxed{I_E = (1 + \beta) I_B}$$

Replace I_E in above equation (Q/P only)

$$V_{CC} - I_{B} R_B - V_{BE} - (1 + \beta) R_E = 0$$

$$V_{CC} - I_C R_C - V_{CE} \rightarrow (1 + \beta) R_E = 0$$

o/p wali mean $I_E = (1+\beta) I_B$

O/P wali eqn men $I_C \approx I_E$

DATE _____
PAGE _____

$$I_{C\text{sat}} /_{V_{CE}=0} = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE\text{cutoff}} /_{I_C=0} = \frac{V_{CC}}{R_C + R_E}$$


Q point

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B + R_E (1+\beta)}$$

$$I_{CQ} = \beta I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_C (R_C + R_E)$$

voltage Divider

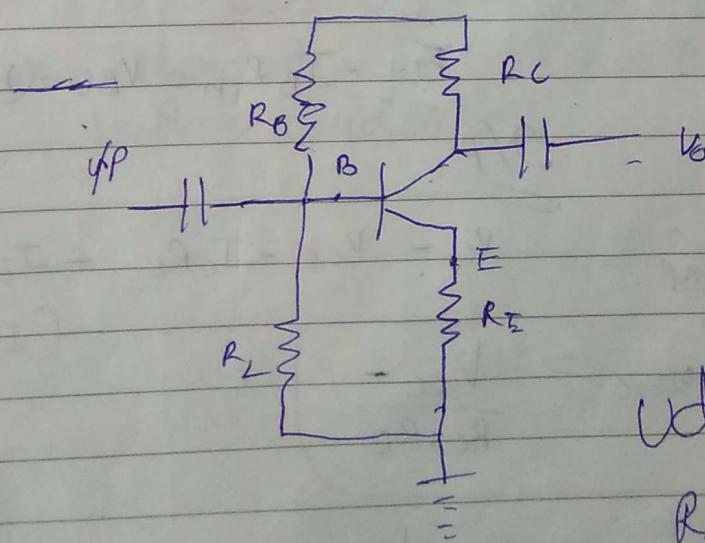

uda do
Raddi

$$\frac{V_{CE(\text{diff})}}{I_C} = V_{CC}$$

$$(I_C = I_E)$$

$$V_{CC} - V_{CE} - I_C R_C - I_E R_E = 0$$


$$\frac{I_{CSat}}{V_{CE=0}} = \frac{R_C + R_E}{V_{CC}}$$

~~Load Line~~

~~Eff~~

$$I_B R_{TH} - V_{BE} - (1+\beta) R_E = 0$$

$$I_B R_{TH} - V_{BE} - I_E R_E = 0$$

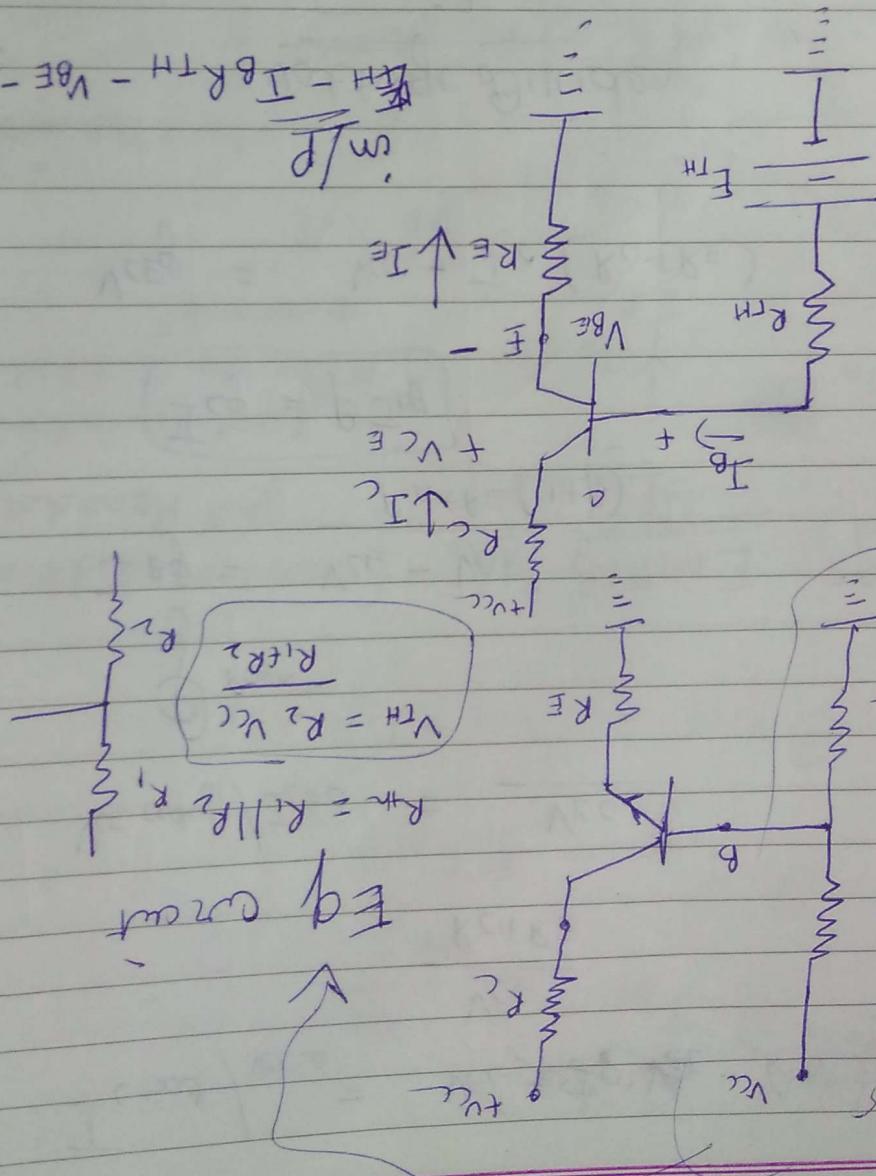

Q Points

$$I_{BQ} = \frac{E_{TH} - V_{BE}}{R_{TH} + R_E(1+\beta)}$$

$$I_{CQ} = \beta I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_C (R_C + R_E)$$

Stability Comparison

- ① Fixed Bias circuit is not properly stable.
- ② Emitter resistance is added to Fixed Bias to stabilize it. (called Emitter Bias or self Bias)

Problem with Emitter Bias

- ③ not stable bcoz values of I_{BQ} & I_{CQ} depend on β . β is highly sensitive to Temp specially for Si transistors
- ④ It is desirable to develop a bias circuit which is less dependent on β . Such a Bias circuit is called Voltage Divider.

21/3/17

DATE _____

PAGE _____

Numericals - 2~~Q-1~~

Q-1 Fixed Bias


$$R_B = 240 \text{ k}\Omega$$

$$V_{CC} = 12 \text{ V}$$

$$R_C = 200 + 2.2 \text{ k}\Omega$$

Find $I_{B\phi}$, $I_{C\phi}$, $V_{CE\phi}$
 V_B , V_{C1} , V_E , V_{B2}

$$\beta = 50$$

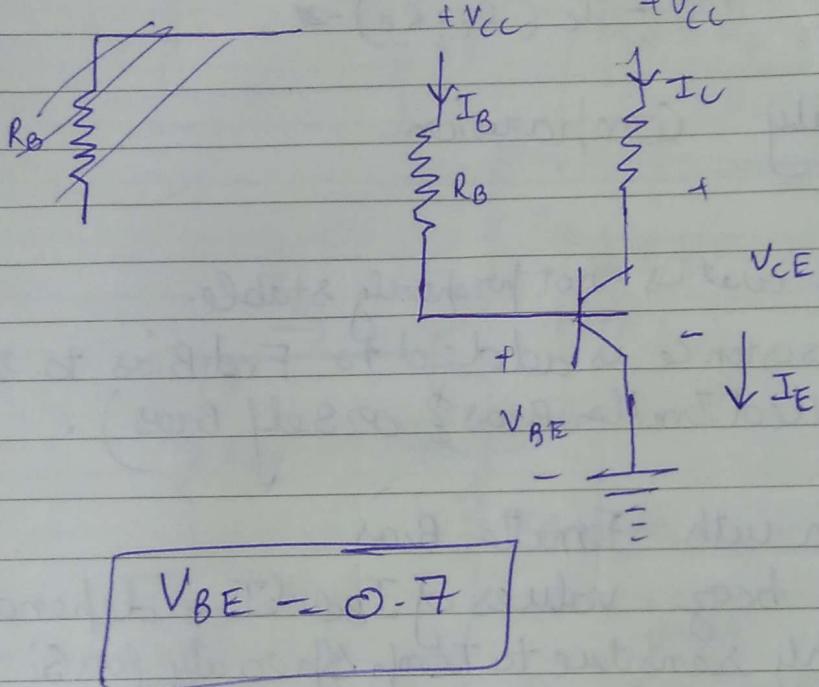

$$I_{B\phi} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{240 \times 10^3}$$

$$= 0.47 \times 10^{-3}$$

$$0.47 \text{ mA}$$

$$I_{C\phi} = \beta I_{B\phi} = 50 \times 0.047 = 2.35 \text{ mA}$$

$$\begin{aligned} V_{CE\phi} &= V_{CC} - I_{C\phi} R_C \\ &= 12 - 2.35 \times 2.2 \\ V_{CE\phi} &= 6.83 \text{ V} \end{aligned}$$

we can consider $V_{CE\phi}$ for v_t

DATE _____
PAGE _____

$$V_{BE} = 0.7$$

$$V_B - V_E = 0.7$$


$$V_B = 0.7$$

$V_E = 0$ = grounded

$$V_{CE\phi} = V_C - V_E = 6.83$$

$$V_C = 6.83$$
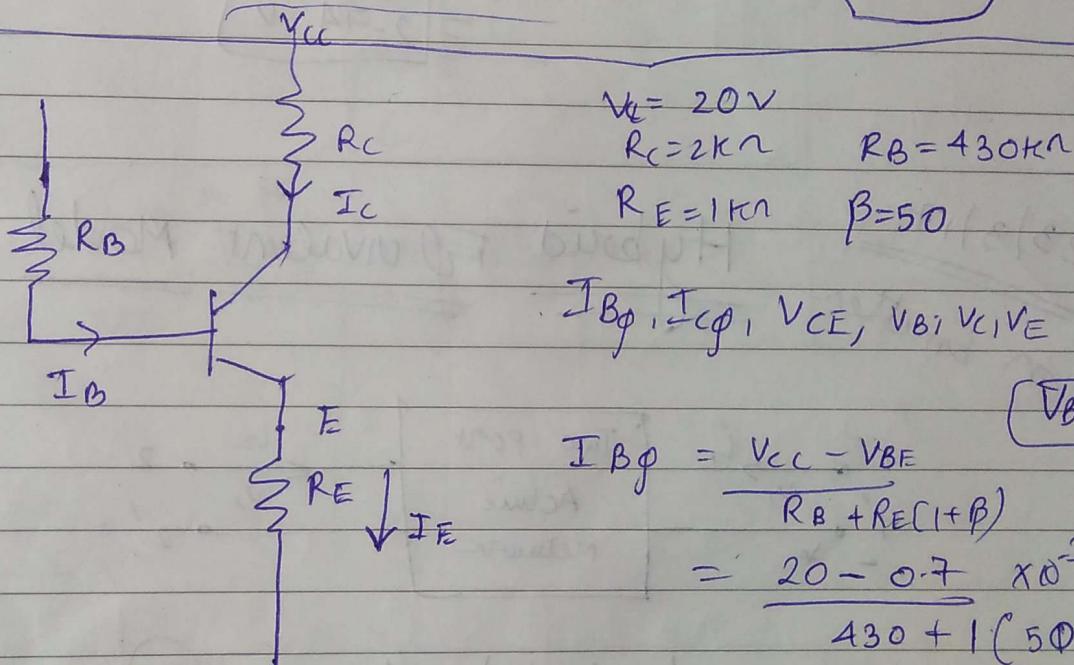
$$V_{BC} = V_B - V_C = 0.7 - 6.83 = -6.13$$



$$\begin{aligned} I_{B\phi} &= \frac{V_{CC} - V_{BE}}{R_B + R_E(1+\beta)} \\ &= \frac{20 - 0.7 \times 10^3}{430 + 1(50+1)} \\ &= 0.041mA \end{aligned}$$

$$I_{C\phi} = \beta I_{B\phi} = 50 \times 0.041 \\ = 2.00 \text{ mA}$$

$$\begin{aligned} V_{CE\phi} &= V_{CC} - I_C (R_C + R_E) \\ &= 20 - 2 \times 10^{-3} (430 + 1) \times 10^3 \\ &= 14V \end{aligned}$$

$$\begin{aligned} V_{CE\phi} &= V_C - V_E = 14 - 0 = 14V \\ V_{BE} &= 0.7 \\ V_B &= 0.7 \\ V_E &= 0 \end{aligned}$$

$$V_{BE} = 0.7$$

$$V_B - V_E = 0.7$$

$$V_B - I_E R_E = 0.7$$

$$V_B - (1 + \beta) I_B R_E = 0.7$$

$$V_B - (51) 0.04 \times 1 = 0.7$$


$$I_E = (1 + \beta) I_B$$

$$V_B = 0.7 + 2.04$$

$$= 2.74 \text{ V}$$

23/3/17

Common Emitter Hybrid Equivalent Model

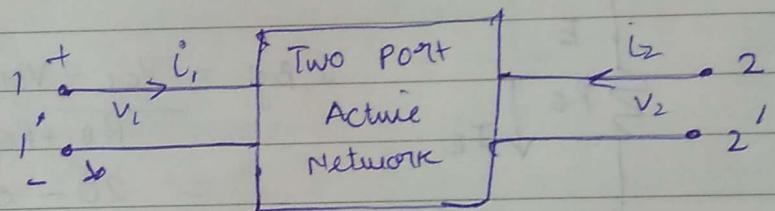

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$\textcircled{1} \quad i_2 = h_{21} i_1 + h_{22} V_2 \quad \textcircled{2}$$

This means i_1 & V_2 are independent variables

Now

What
shot circuit

$$N_2 = 0$$

$$\text{So } h_{11} = \frac{V_1}{i_1} = \text{input impedance} = Z_{i_1} = h_i$$



$$h_{21} = \frac{i_2}{i_1} = h_f, \text{ current gain found}$$

i/p
o/c

so $i_1 = 0$

$$h_{12} = \frac{V_1}{V_2} \quad \text{* } h_{12}, \text{ reverse voltage gain}$$
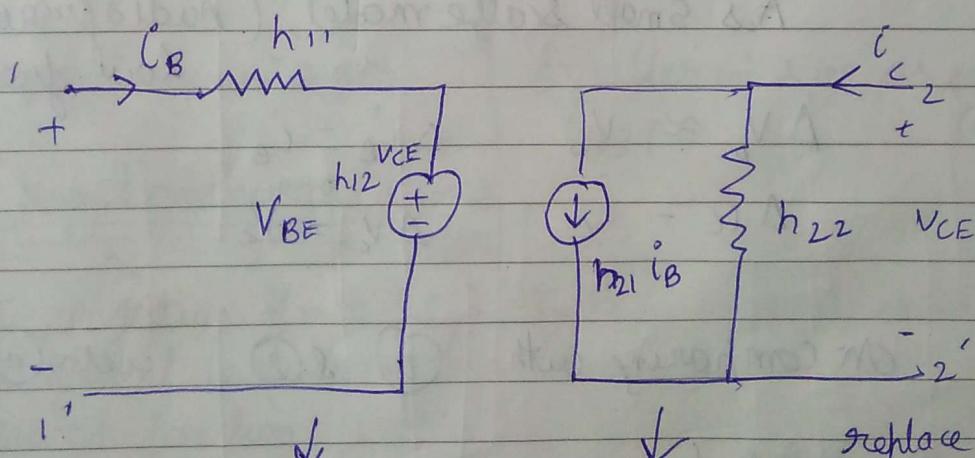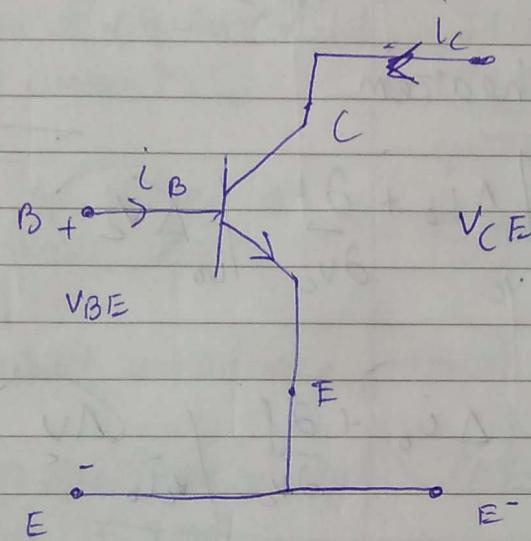
$$h_{22} = \frac{i_2}{V_2} \quad Y_0 \text{ or } h_0 = \text{Admittance}$$



So this is a
Thevenin equivalent
circuit

↓
This is a Norton
equivalent circuit.
replace i_2 with i_C
 $i_1 = i_B$
 $V_1 = V_{BE}$
 $V_2 = V_{CE}$

That's why hybrid

50 → 150



DATE _____

PAGE _____

Derivation

$$V_{BE} = V_B$$

$$V_b = f(i_b, v_c)$$

(representing earlier equation in function form)

$$i_c = f(\cancel{V_b})(i_b, v_c)$$

using Taylor's theorem

$$\Delta V_b = \frac{\partial f}{\partial i_b} \Big|_{V_c} (i_b + \frac{\partial f}{\partial v_c} \Big|_{i_b} \Delta v_c) \quad @$$

$$\Delta i_c = \frac{\partial f}{\partial i_b} \Big|_{V_c} (\Delta i_b + \frac{\partial f}{\partial v_c} \Big|_{i_b} \Delta v_c) \quad b$$

As small scale model, (Audio frequency)
low freauency

$$\Delta V_b \approx V_b \quad \Delta i_b = i_b$$

$$\Delta i_c = i_c \quad \Delta v_c = V_c$$

On comparing with ① & ② with ③ ④

$$h_{11} = \frac{\partial f}{\partial i_b} \Big|_{V_c}$$

$$h_{12} = \frac{\partial f}{\partial v_c} \Big|_{i_b}$$

$$h_{21} = \frac{\partial f}{\partial i_b} \Big|_{V_c}$$

$$\frac{\partial f}{\partial i_b} \Big|_{i_b}$$

28/3/17

DATE _____

PAGE _____

JFET

Junction Field Effect Transistor

~~min~~

~~sure~~

Differences b/w BJT & JFET

1) BJT is a ^{current} control device whereas FET is a voltage control device.

BJT

2) Both e⁻ & holes contribute to output current I_o

3) BJT has AC Voltage is higher than JFET

4) Less input impedance

BJT

5) Transistors are more sensitive to changes in temp

6) ~~same~~ larger in size

JFET

- It is a unipolar device. Either e⁻ or holes contribute to output current

less than BJT

High input impedance



JFET are more temp stable

smaller in size as compared to BJT

7) O/P based on charge carriers


In BJT, injection of minority carriers takes place across
Forward Biased junction

In FET, majority charge carriers conduct

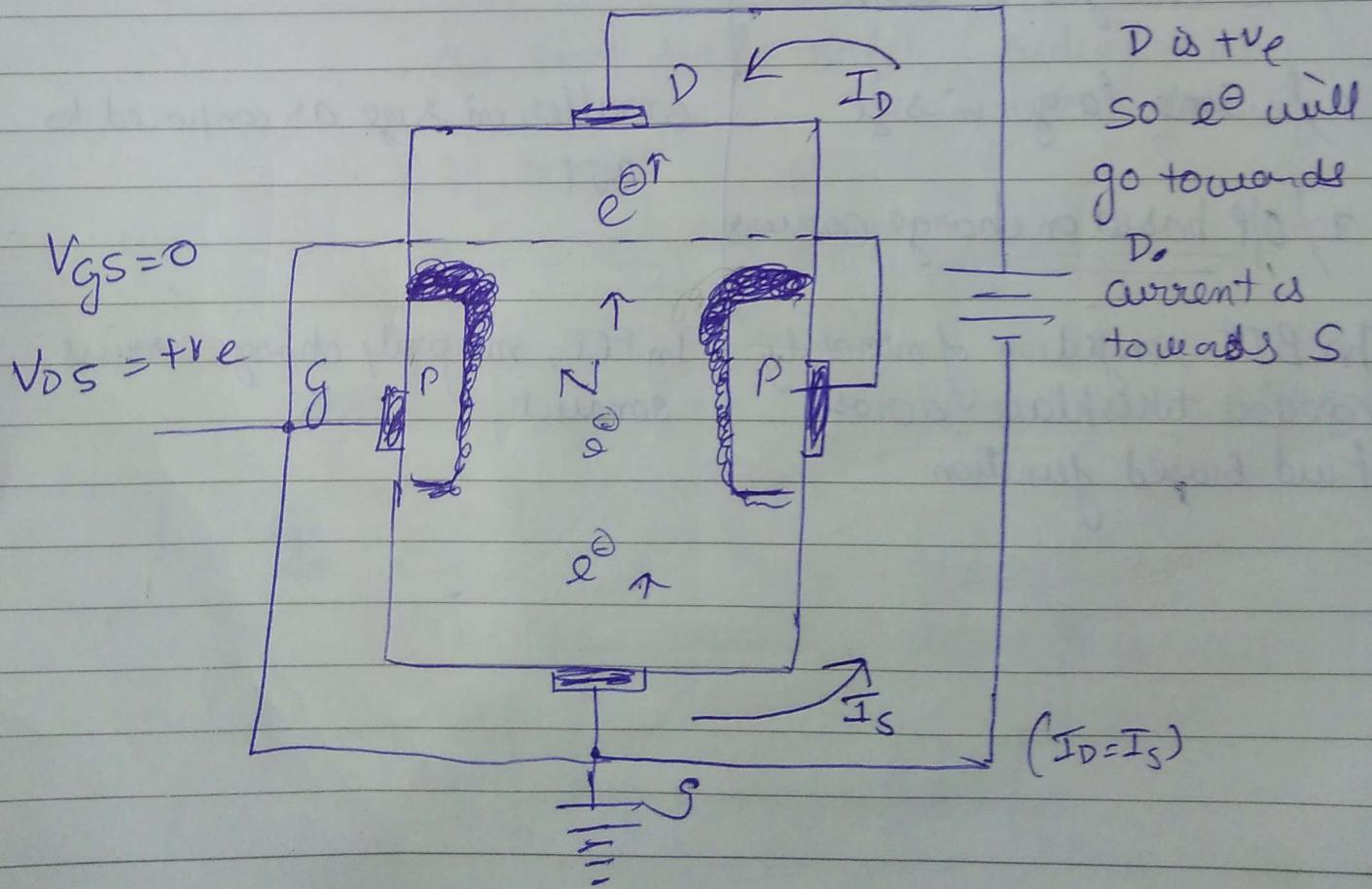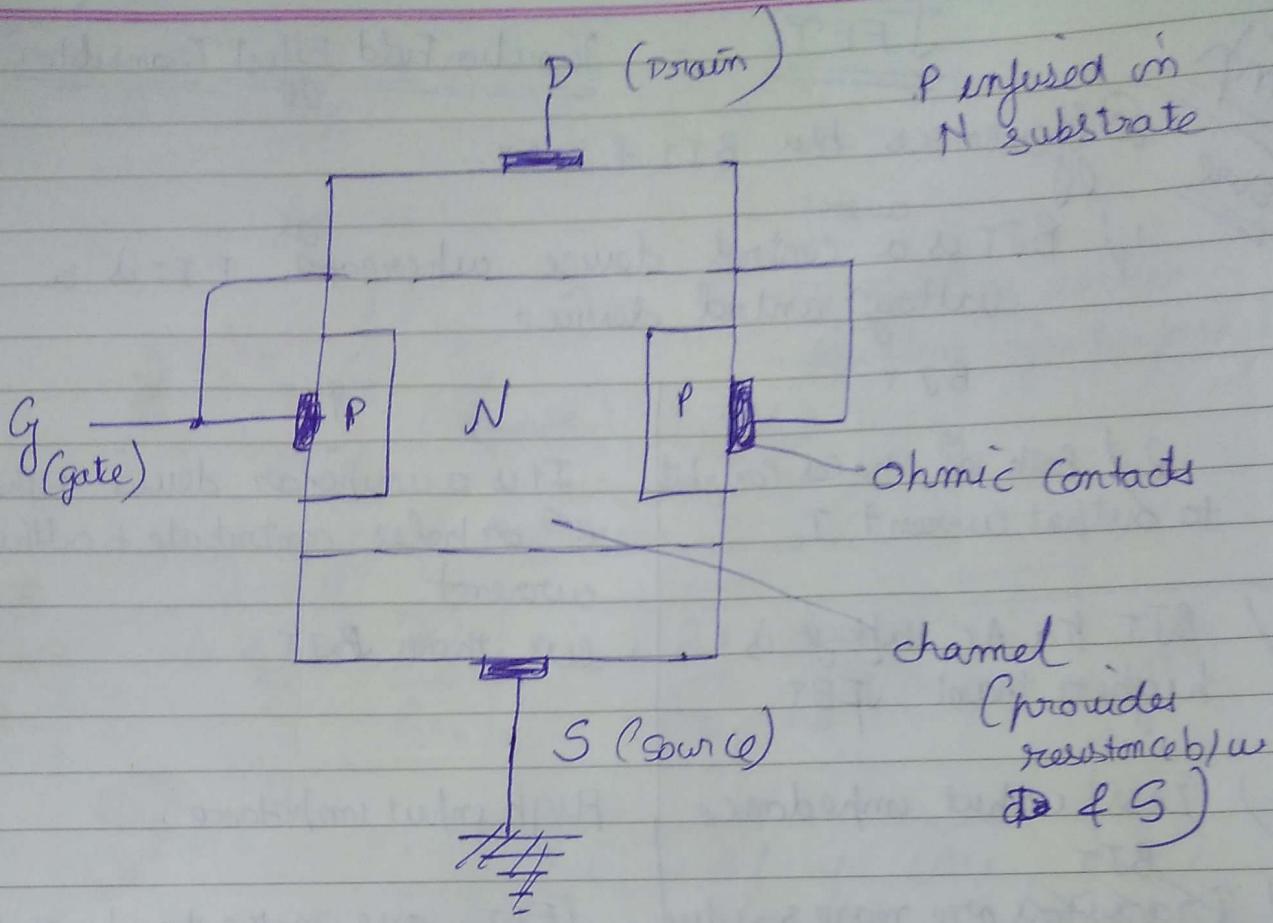

Scanned by CamScanner

As we increase V_{DS} , more e^- will be attracted so current will go increasing. But also R_B is increasing, so depletion is increasing. At some voltage, the depletion region will become so large that both depletion region will start touching each other and no e^- will not be able to pass easily. This is the saturation level and current is called I_{DSS} (saturation drain current) and the voltage is called punchoff voltage.

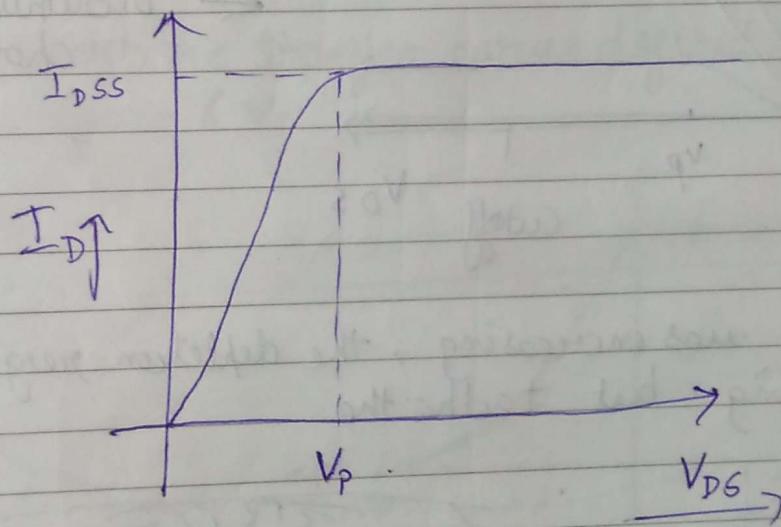



Now instead of taking $V_{GS} = 0$, V_{GS} is now equal to -2° . So now the depletion region are already close to each other as R_B is high.

That's why, V_p will be less, I_{DSS} will be less and saturation will come earlier. (common sense)



This means V_{GS} controls the current.

As V_{GS} becomes more $-V_L$, saturation, V_p, I_{DSS} will start decreasing.

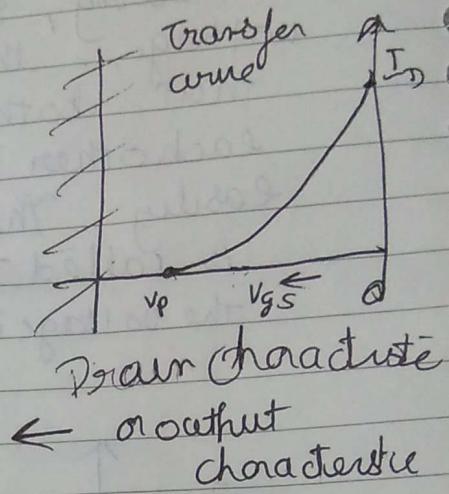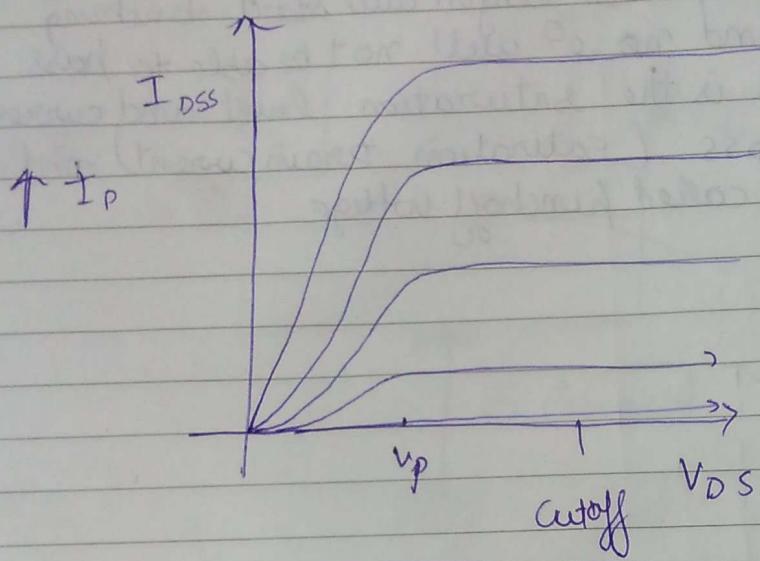So when $V_{GS} = -V_P$, at this voltage no current will start flowing. This is the cutoff voltage.



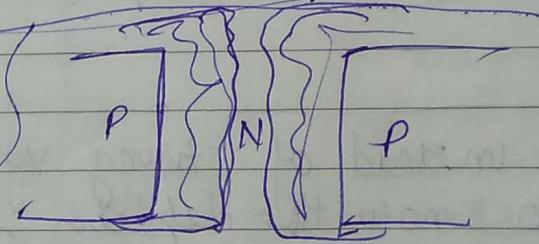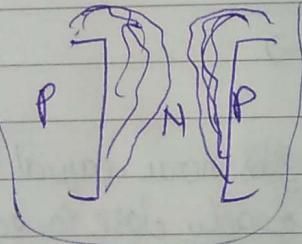- * When V_{DS} was increasing, the depletion regions were closing but before the



but when V_{GS} becomes $-V_P$, the channel closes properly

30/3/17


DATE _____
PAGE _____

Analogous to BJT
Gate - Base
Drain - collector
Source - Emitter

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{- Tells operation of JFET}$$

For a particular value of V_{GS} , V_P and I_{DSS} are constant

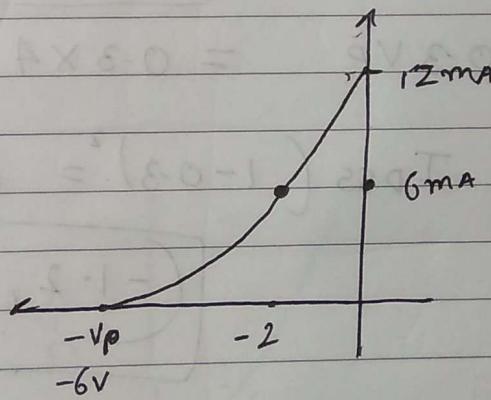Ques Sketch the transfer curve defined by $I_{DSS} = 12\text{mA}$
 $V_P = -6\text{V}$.



No manufacturing points

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{when } V_{GS} = 0.3V_P$$

$$I_D = I_{DSS} \left(1 - \frac{0.3V_P}{V_P} \right)^2 = (0.7)^2 I_{DSS} \times 12$$

$$I_D = 0.5 \times 12 = 6$$

$$\& V_{GS} = 0.3V_P = 0.3 \times 6 = -2$$

Now when $V_{GS} = 0.5V_P$

$$(1 - 0.3) V_P \rightarrow 0.7 V_P \rightarrow 0.7 \text{ mA}$$

$$I_{DSS} = 12 \text{ mA}$$

$$V_P = -4$$

$$V_{GS} = 0.5 V_P$$

$$V_{GS} = -2$$

$$I_D = I_{DSS} \left(1 - 0.5 \right)^2 = 0.25 I_{DSS} = 3 \text{ mA}$$

$(-2, 3)$

$$V_{GS} = 0.4 V_P = 0.4 \times -4 = -0.4$$


$$\Rightarrow I_D = I_{DSS} \left(1 - 0.1 \right)^2 = 0.81 \times 12 = 9.72$$

$(-0.4, 9.72)$

$$V_{GS} = -0.3 V_P = 0.3 \times 4 = 1.2$$

$$I_{DSS} \left(1 - 0.3 \right)^2 = 0.49 \times 12 = 5.88$$

$(-1.2, 5.88)$

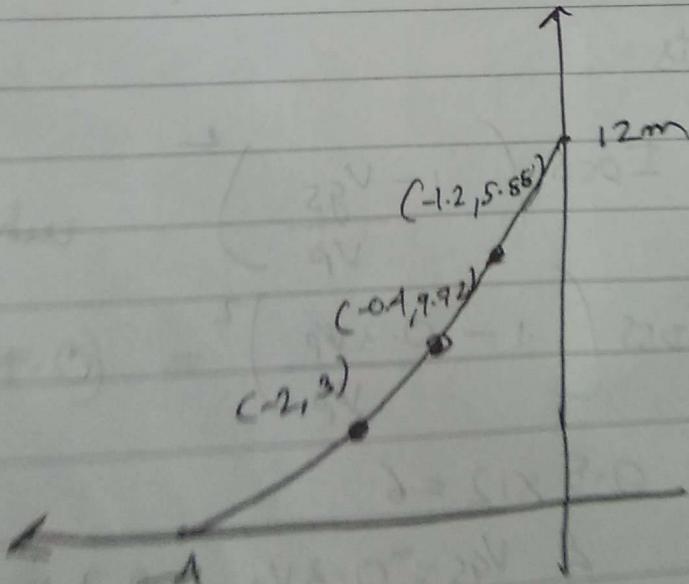

How to use Eber's equations.

Doubt

Pg 183 - Eber's equation

Are they sufficient to explain?

