

Unit 2 Laplace Transform of Signals

→ Double sided

• Bilateral Laplace Transform is used to find system characteristics.

E.g. Causality, frequency response, stability.

• Unilateral Laplace is used for solving the differential eqns when the initial conditions are known.

Laplace

$$H(s) = \int_{-\infty}^{\infty} h(t) \cdot e^{-st} dt$$

Inverse Laplace


$$h(t) = \frac{1}{2\pi j} \int_{-\infty}^{\infty} H(s) \cdot e^{st} dt$$

S-Plane — Real (s) \rightarrow
Imag (s) $\downarrow j\omega$

$$s = \sigma + j\omega$$

$j\omega$ \rightarrow Poles

$\sigma \rightarrow$ holes/2

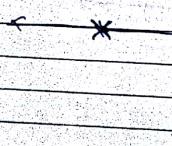


$$H(s) \leftrightarrow \frac{1}{s+2}$$

$$e^{-2t} \leftrightarrow \frac{1}{s+2}$$

$$X(s) = \frac{s+2}{(s+3)(s+4)}$$

$$s = 2 + 3j \rightarrow \text{Zero}$$

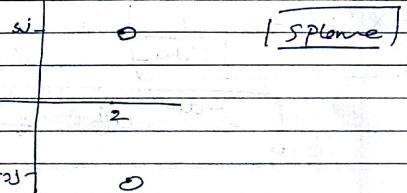Roots of Numerator - Zeros / poles = 0
Roots of Denominator - Poles - X



Q. Find the Laplace transform of $x(t) = e^{-at} \cdot u(t)$

$$X(s) = \int_{-\infty}^{\infty} x(t) \cdot e^{-st} dt$$

$$= \int_0^{\infty} e^{-at} \cdot e^{-st} \cdot u(t) dt$$

$$= \int_{-\infty}^{\infty} u(t) \cdot e^{-at} \cdot e^{-st} dt + \leftarrow X(0) \text{ zero.}$$

$$+ \int_0^{\infty} u(t) \cdot e^{-at} \cdot e^{-st} dt$$

$$\therefore X(s) = \int_0^{\infty} e^{-at} \cdot e^{-st} dt$$

$$\begin{aligned}
 &= \int_0^\infty e^{-(s+a)t} dt \\
 &= \left[-\frac{1}{s+a} e^{-(s+a)t} \right]_0^\infty \\
 &= \frac{1}{s+a} \left[1 - e^{-\infty} \right] \\
 &= \frac{1}{s+a} [0 - 1] \\
 &= -\frac{1}{s+a}
 \end{aligned}$$

$$X(s) = \frac{1}{s+a}$$

$$\boxed{\int e^{-at} \cdot u(t) \leftrightarrow \frac{1}{s+a}}$$

$$\begin{aligned}
 x(t) &= e^{-at} u(-t) \\
 X(s) &= \int_{-\infty}^{\infty} x(t) e^{-st} dt \\
 &= \int_{-\infty}^0 e^{-at} \cdot e^{-st} \cdot u(-t) dt \\
 &= \int_{-\infty}^0 e^{-at} \cdot e^{-st} \cdot u(-t) dt \\
 &\quad - \int_0^\infty e^{-at} \cdot e^{-st} \cdot u(-t) dt
 \end{aligned}$$

Page No. _____
Date _____

$$\begin{aligned}
 &\int_{-\infty}^0 e^{-at} \cdot e^{-st} \cdot u(-t) dt = 0 \\
 &= - \int_{-\infty}^0 e^{-at} \cdot e^{-st} \cdot u(-t) dt \\
 &= - \int_{-\infty}^0 e^{-(s+a)t} dt \\
 &= -\frac{1}{s+a} \left[e^{-(s+a)t} \right]_{-\infty}^0 \\
 &= -\frac{1}{s+a} [1 - 0] \\
 &= \frac{1}{s+a} \\
 &\boxed{\int -e^{-at} \cdot u(-t) \leftrightarrow \frac{1}{s+a}} \\
 x(t) &= e^{-2t} u(t) - e^{-3t} u(t) \\
 &\text{find Laplace Transform & ROC.} \\
 X(s) &= \frac{1}{s+2} - \frac{1}{s+3} \\
 &= \frac{s+3 - s-2}{(s+2)(s+3)} \\
 &= \frac{1}{(s+2)(s+3)} \\
 s = -2 & s = -3
 \end{aligned}$$

Page No. _____
Date _____

Page No. _____
Date _____

Q. $x(t) = -e^{-2t} \cdot u(-t) + e^{-3t} u(-t)$

$$X(s) = \frac{1}{s+2} + X \left[e^{-3t} u(-t) \right]$$

\Rightarrow

$$= \int_{-\infty}^{\infty} e^{-3t} \cdot e^{-st} \cdot u(-t) dt$$

$$= \int_{-\infty}^{0} e^{-3t} \cdot e^{-st} dt$$

$$= \int_{-\infty}^{0} e^{-(s+3)t} dt$$

$$= -\frac{1}{s+3} \left[e^{-(s+3)t} \right] \Big|_{-\infty}^0$$

$$= -\frac{1}{s+3} (1 - 0)$$


$$= -\frac{1}{s+3}$$

Page No. _____
Date _____

$$\therefore X(s) = \frac{1}{s+2} - \frac{1}{s+3}$$


$$= \frac{s+3 - s-2}{(s+2)(s+3)}$$

$$= \frac{1}{(s+2)(s+3)}$$

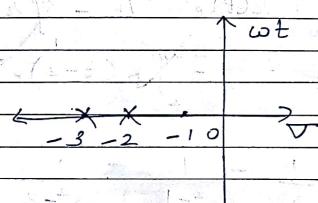

$$x(t) = -e^{-2t} \cdot u(t) - (-e^{-3t} u(t))$$

$$\frac{1}{s+2} - \frac{1}{s+3}$$

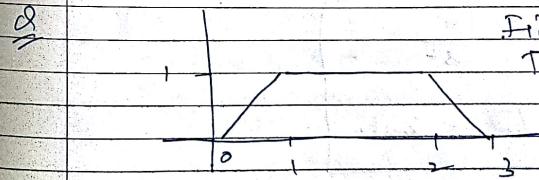

Find Laplace
Transform.

$$x(t) = r(t) - r(t-1) - r(t-2) + r(t-3)$$

$$X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$

$$= \int_{-\infty}^{\infty} [r(t)e^{-st} - r(t-1)e^{-s(t-1)} - r(t-2)e^{-s(t-2)}] dt$$

$$= \int_0^1 r(t)e^{-st} dt - \int_1^2 r(t-1)e^{-s(t-1)} dt$$

$$- \int_2^{\infty} r(t-2)e^{-s(t-2)} dt$$

$$= \frac{1}{s^2} - \frac{1}{s^2-1} - \frac{1}{s^2-2} + \frac{1}{s^2-3}$$

Unit - $\frac{1}{s}$

Ramp - $\frac{1}{s^2}$

Impulse \rightarrow Const.

Q. $R-L$

$$R = 2 \Omega$$

$$L = 10 \text{ H}$$

$$V = 100 \text{ V}$$

i? at $t = 5$

$$T = \frac{L}{R} = \frac{10}{2} = 5 \text{ sec}$$

$$i = I(1 - e^{-t/T})$$

$$= \frac{100}{2} (1 - e^{-5/5})$$

$$= 50 (1 - e^{-1})$$

$$\boxed{i = 31.60 \text{ A}}$$

Q. $R = 25 \Omega$

$$L = 5 \text{ H}$$

$$V = 100 \text{ V} \text{ at } t = 0$$

Find - (i) ~~i~~ and V across R and L

(ii) i after $t = 0.5$

(iii) t at which voltage drop across R & L is same.

$$(i). i = I(1 - e^{-t/T}) \quad \frac{25t}{5} \frac{t}{T} = R$$
$$= \frac{25}{100} (1 - e^{-t/0.5}) \quad L$$

$$i = 4(1 - e^{-5t}) \text{ A}$$

$$V_R = 100(1 - e^{-5t}) \text{ V}$$

$$\left[\frac{d}{dt} e^{-st} = -se^{-st} \right]$$

Page No. _____
Date _____

$$-5 \times \left(\frac{-1}{5} \right) \cdot 4(1 - e^{-st})$$

$$= 4(1 - e^{-st})$$

$$5 \times \left(\frac{-1}{5} \right) (-e^{-st})$$

$$= -e^{-st}$$

$$5 \times \frac{d}{dt} (4(1 - e^{-st}))$$

$$V \Rightarrow 5 \times \frac{d}{dt} (4 - 4e^{-st})$$

$$= 5 \times (0 + 20e^{-st})$$

$$= 100e^{-st} V$$

(ii) i after $t = 0.5\text{s}$

$$i = 4(1 - e^{-st})$$

$$= 4(1 - e^{-0.5 \times 5})$$

$$i = 3.67 A$$

(iii)

V_i at $V = 50$

$$100e^{-st} = 50$$

$$e^{-st} = \frac{1}{2}$$

$$e^{5t} = 2$$

$$5t = 0.6931$$

$$\text{or } t = \frac{0.6931}{5}$$

$$t = 0.138 \text{ sec}$$

8.11

L-R

$$V = 200 V$$

$$R = 20 \Omega$$

$$L = 0.2 H$$

$$V = ? \text{ at (i) } t = 0 \text{ (ii) } t = 0.02$$

Ans.

$$V = iR + L \frac{di}{dt}$$

$$200 = 20i + 0.2 \cdot \frac{di}{dt}$$

$$i = I(1 - e^{-t/T}) \quad T = \frac{L}{R} \\ = \frac{200}{20}(1 - e^{-t/0.2}) \quad = 0.01$$

$$i = 10(1 - e^0)$$


$$i = 10(1 - e^{-0.02 \times 0.02})$$

$$= 10(1 - e^{-0.0004})$$


$$i = 10(1 - e^{-0.0004}) \approx 8.64 A$$

$$\text{Voltage Drop} = 200 - 172.93 = 27.07 V \\ \frac{di}{dt} = \frac{200 - 172.93}{0.2} = 135.35 A/\text{sec}$$


Transient Response

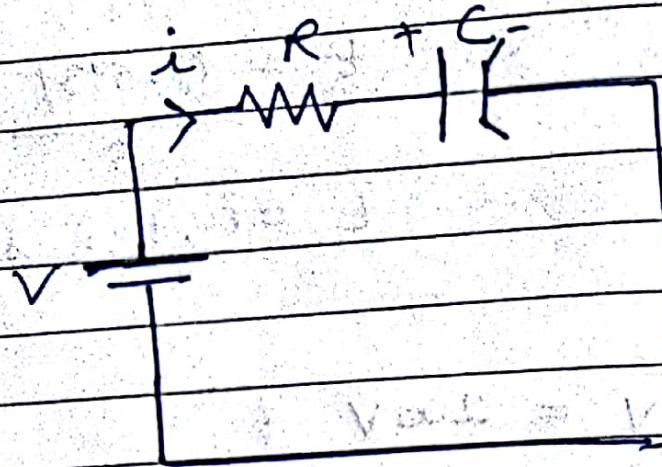

Paper Capacitor
(unidirectional)

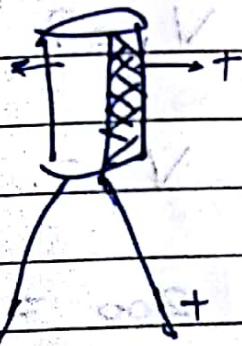

Ceramic Cap.
Positivo

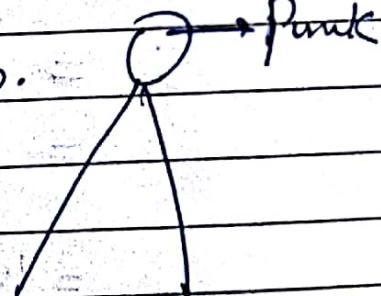

$$V = iR + \frac{1}{C} \int idt$$

$$\Delta V = R di + \frac{i}{C} dt$$

Q. $R = 2000 \text{ k}\Omega = 2000000 \Omega$
 $C = 5 \mu\text{F} = 5 \times 10^{-6} \text{ F}$
 $t = ?$
 $T = R.C = 10 \text{ sec}$
 $q = (50\%)Q$


$$q = Q \cdot (e^{-t/T})$$

$$\frac{50}{100} Q = Q \cdot e^{-t/10}$$

$$0.5 = e^{-t/10}$$

$$\frac{t}{10} = -0.6931$$

$$\Rightarrow t = 6.931 \text{ sec}$$

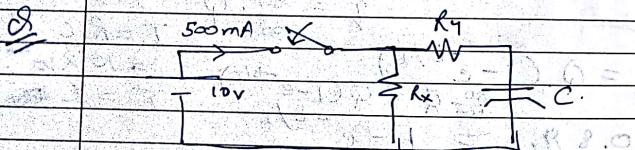


$t = ?$ when $I = 500 \text{ mA} = 500 \times 10^{-3} \text{ A}$
 $R_x = 50 \Omega$

$$R_y = 70 \Omega$$

$$C = 100 \mu\text{F} = 100 \times 10^{-6} \text{ F}$$

$$V = 10 \text{ V}$$

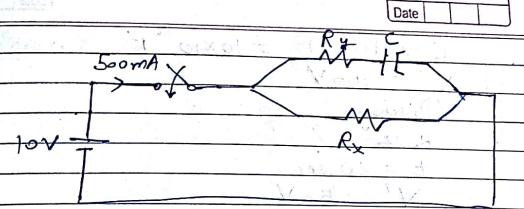

$$I_y = I e^{-t/T} = 70 \times 100 \times 10^{-6} = 7 \times 10^{-3} \text{ sec}$$

$$I_x = V_x / R_x = 500 / 50 = 25 \text{ A}$$

$$I_x = \frac{V_x}{R_x} = \frac{25}{50} = 0.5 \text{ A}$$

$$\text{Total Current} = I_x + I_y = 500 \text{ mA}$$

$$I_x = \frac{10}{50} = 200 \text{ mA}$$

$$I_y = 300 \text{ mA} = 0.3 \text{ A}$$

$$0.13 = \frac{10}{70} e^{-t/(7 \times 10^{-3})}$$

$$2.1 = e^{-t/(7 \times 10^{-3})} + (7 \times 10^{-3}) = 0.4761$$

$$0.74 = \frac{-t}{7 \times 10^{-3}} \quad t = -0.7419$$

$$-5.18 \times 10^{-3} \quad t =$$

$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}$$

$$\frac{R}{L} \frac{di}{dt} + \frac{d^2i}{dt^2} + \frac{i}{LC} = 0$$

$$T \left(\frac{R}{L} P + P^2 + \frac{1}{LC} \right) i = 0$$

$$\alpha = \frac{-b \pm \sqrt{b^2 - 4AC}}{2a}$$

$$L(t) = k_1 e^{-P_1 t} + k_2 e^{-P_2 t}$$

P_1, P_2 are roots of T

wkt. at $t = 0$,

$$\Rightarrow k_1 + k_2 = 0$$

$$k_1 = -k_2$$

②

at $t = 0$,

$$V = L \frac{di}{dt}$$

$[i=0]$

$$5k_1 = 20$$

$$\Rightarrow k_1 = 4$$

$$k_2 = -4$$

$$i(t) = 4e^{4.791t} - 4e^{-208t}$$

Sinusoidal Response of RLC Circuit

ϕ is the angle b/w voltage & current or the reactance & resistance.

$$\omega L = X_L = 2\pi f \cdot L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f \cdot C}$$

Parallel R-C

$$I_R = \frac{V}{R}$$

$$I_C = \frac{V}{j\omega C} = V \cdot j\omega C$$

$$\theta = \tan^{-1}(\omega RC)$$

RLC Circuit

Series

$$V = IZ = I \left(\frac{1}{j\omega C} + j\omega L + R \right)$$

$$\theta = \tan^{-1} \left[\omega L - \frac{1}{j\omega C} \right] / R$$

Parallel

$$\theta = \tan^{-1} \left(\omega C - \frac{1}{\omega L} \right) / R$$

↓
Phase ↘

$$(ii) \quad I = \frac{V}{Z} = \frac{100}{5,08 \angle -38.14^\circ}$$

$$I = 19.685 \angle (-38.14^\circ)$$

$$(iii) \quad V_R = I.R \\ = +19.685 \angle -38.14^\circ \times 4 \\ = +78.74 \angle -38.14^\circ V$$

~~$$P_S = 19.685 \angle -38.14^\circ \times 10 \times 10^{-3}$$~~


$$\begin{aligned} V_L &= 19.685 \angle -38.14^\circ (100\pi \times 10^{-2}) \\ &= 61.842 \angle -38.14^\circ V \\ &\quad \text{90}^\circ - 38.14^\circ \end{aligned}$$

$$\because R \perp L \times \text{Ind}$$

$$= 61.842 \angle 51.86^\circ$$

$$(iv) \quad P_F = \cos(\phi) \\ = \cos(-38.13^\circ) \\ = 0.786 \\ = 78.6\%$$
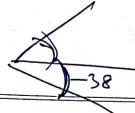
$$(v) \quad \text{Real Power} = P = IV \cos(\phi) \\ = 19.685 \angle -38.14^\circ \times 100 \times 0.786 \\ = 1547.241 \text{ W}$$



Page No. _____
Date _____

$$(vi) \quad \text{Total Power} = I.V = 100 \times 19.685 \angle -38.14^\circ$$

$$= 1968.5 \angle -38.14^\circ \text{ W}$$

H.W Eg. 4.3, 4.4, 4.6

$$\begin{aligned} 4.2 \quad R &= 20 \Omega \\ L &= 60 \text{ mH} \\ \phi &= 60^\circ \\ f &=? \end{aligned}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$\tan(60) = \omega \cdot \frac{60 \times 10^{-3}}{20}$$


$$\omega = \frac{\sqrt{3} \times 20}{0.06}$$

$$\omega = 577.350 \text{ rad/sec} \\ = 2\pi f$$

$$\Rightarrow f = \frac{577.35}{2\pi}$$

$$f = 91.88 \text{ Hz}$$

4.25

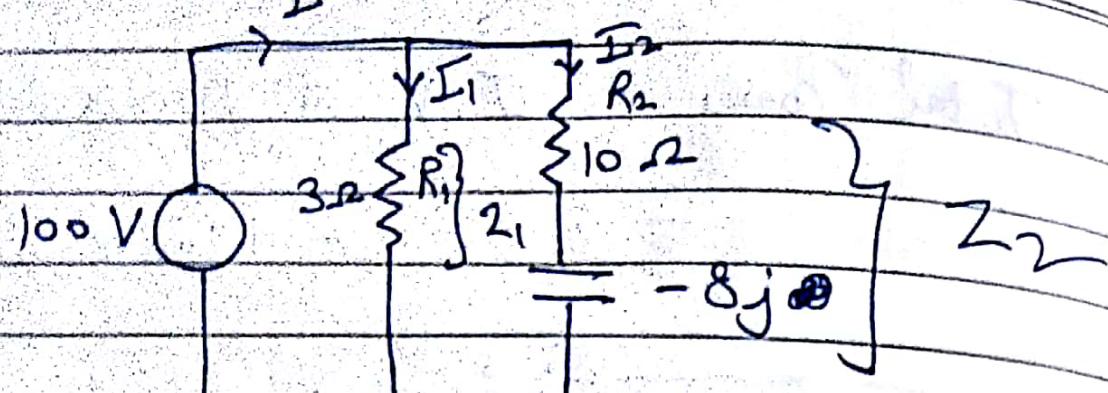

$$I = ? \quad I_1 = ? \quad I_2 = ?$$

$$R_{\text{load}} = ?$$

$$Z_1 = 3$$

$$Z_2 = 10 - 8j$$

$$|Z_2| = \sqrt{8^2 + 10^2} \cdot \tan^{-1}\left(\frac{8}{10}\right)$$

$$= \sqrt{64+100} \tan^{-1}\left(\frac{8/10}{\cancel{10}-8j}\right)$$

$$= 12.80 \times \tan^{-1}(0.80)$$

~~$$= 12.80 \angle 38.65^\circ$$~~

$$Z_1 = 3 \angle 0^\circ$$

$$I_1 = \frac{100}{3} = 33.33 \angle 0^\circ$$

$$I_2 = \frac{100}{12.80 \angle 38.65^\circ} = 7.812 \angle -38.65^\circ$$

E4.4

$$I = 1 A$$

$$V = 10 V$$

$$f = 500 \text{ Hz}$$

$$R = 5 \Omega$$

$$\omega = 2\pi f = 2\pi \times 10 = 20\pi$$

$$Z = \sqrt{R^2 + (\omega L)^2}$$

$$\frac{V}{I} = \sqrt{R^2 + (\omega L)^2}$$

$$10 = \sqrt{25 + 400\pi^2 L^2}$$

$$100 = 25 + 400\pi^2 L^2$$

$$\Rightarrow L^2 = \frac{75}{2500\pi^2} = \frac{75}{4\pi^2 \times 50^2} = 0.027 \text{ H}$$

$$\Rightarrow L = \sqrt{0.027} = 0.027 \text{ H}$$

$$PF \Rightarrow \cos \phi = \frac{R}{Z}$$

$$= \frac{5}{10} = \frac{1}{2} = 0.5$$

Page No.
Date

4.6

$$R = 4 \Omega$$

$$L = 0.01 \text{ H}$$

$$f = (i) 100 \text{ Hz} \quad (ii) 500 \text{ Hz}$$

$$Z = ?$$

$$\begin{cases} X_L = \omega L \\ X_C = \frac{1}{\omega} \end{cases}$$

Page No.
Date

$$Z_{100} = R + jX_L$$

$$= 4 \Omega + j100\pi \times 0.01$$

$$Z_{100} = 4 \Omega + j6.28$$

$$Z_{100} = \sqrt{R^2 + (\omega L)^2} / \tan^{-1} \frac{\omega L}{R}$$

$$= \sqrt{16 + (2\pi)^2} \angle \tan^{-1} \left(\frac{2\pi}{4} \right)$$

$$= 7.44 \angle 57.51$$

$$Z_{500} = R + jX_L$$

$$= 4 + j500 \times 2\pi \times 0.01$$

$$= 4 + j10\pi$$

$$= 4 + 31.4j$$

$$Z_{500} = \sqrt{R^2 + (\omega L)^2} \angle \tan^{-1} \left(\frac{10\pi}{4} \right)$$

$$= 31.66 \angle 82.74$$

~~Q4.3~~
 ~~$f = 50 \text{ Hz}$~~
 ~~$V = 311 \sin \omega t$~~
~~(R-L series)~~
 $R = 5 \Omega$
 $L = 0.02 \text{ H}$
 Steady state I/V values

- (i) $I_{\text{rms}} = ?$
- (ii) ϕ
- (iii) $i = ?$
- (iv) V across each ckt. element.


Aus.

~~$I_{\text{rms}} = \sqrt{V_{\text{rms}}}$~~

$\sqrt{V_{\text{rms}}} = 311 \sqrt{2} \approx 220 \text{ V}$

$Z = R + jX_L$
 $X_L = \omega L$
 $\Rightarrow Z = 5 + j(2\pi \times 50 \times 0.02)$
 $= 5 + j6.28$

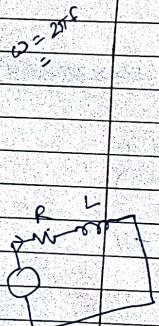$Z = \sqrt{R^2 + (\omega L)^2} \angle \tan^{-1} \left(\frac{\omega L}{R} \right)$
 $= \sqrt{25 + 4\pi^2} \angle \tan^{-1} \left(\frac{2\pi}{5} \right)$
 $= 8.029 \angle 51.488^\circ$



$\sqrt{311^2}$
 $V(1) = 311 \times \sin(90^\circ)$
 $= 311$

$I_{\text{rms}} = \frac{220}{8.029 / 51.488}$

$= 27.40 \angle -51.488^\circ \text{ A}$

- ✓ Divide angle - sign reverse
- ✓ Multiply angle - $90 - \phi$

(ii) $\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = 51.488^\circ$
 (iii) $I = I_{\text{rms}} \sqrt{2} \sin(\omega t + \phi)$
 $= I_{\text{rms}} \sqrt{2} \sin(\omega t + 51.488^\circ)$
 $= 27.40 \sqrt{-51.488 \times \sqrt{2} \sin(100\pi t + 51.488^\circ)}$
 $= 38.749 \angle -51.488^\circ \sin(100\pi t + 51.488^\circ)$

$I(t) = 38.75 \sin(\omega t - 51.488^\circ)$

HW 4B34, 4.37

Page No. _____
Date _____

$$V_R = I_{rms} \times R \\ = 27.40 \angle -51.488 \times 5 \\ \angle -51.488$$

$$\Rightarrow V_R = 137 \angle -51.488 \text{ V}$$

$$V_L = I_{rms} \times jX_L \\ = 27.40 \angle -51.488 \times j(10\pi \times 0.02) \\ = 27.40 \angle -51.488 \times j2\pi \\ = 172.15 \angle 38.512 \text{ V}$$


E.4.35

Series RL

$$I = 1 \cos(314t - 20)$$

$$V = 10 \cos(314t + 10)$$

$$L = ? \quad R = ?$$

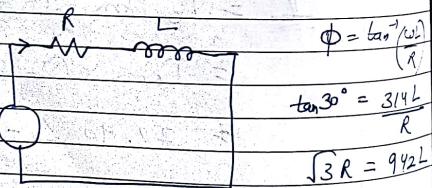

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\tan 30^\circ = \frac{314L}{R}$$

$$\sqrt{3}R = 942L$$

$$Z = \sqrt{R^2 + (\omega L)^2} \\ Z = \frac{V_0}{I} = \sqrt{R^2 + (314L)^2} \\ 10 = \sqrt{R^2 + (314L)^2} \\ R^2 + (314L)^2 = 100$$

✓ Kilo - 10^3
✓ Mega - 10^6
✓ nano - 10^{-9}
✓ milli - 10^{-3}

✓ micro - 10^{-6}
✓ pico - 10^{-12}

Page No. _____
Date _____

$$R = 9.02 \Omega$$

$$(314L)^2 = 100 - \left(\frac{942L}{\sqrt{3}}\right)^2$$

$$985.96 L^2 = 100 - 2957.88 L^2$$

$$3943.84 L^2 = 100$$

$$L = 0.015 = 15 \text{ mH}$$

$$R = \frac{942 \times 0.015}{\sqrt{3}}$$

$$R = 8.66 \Omega$$

(Q) 4.36 Series R-C circuit

$$R = 10 \Omega$$

$$C = 25 \text{ nF}$$

$$X_C = 25 \Omega$$

$$f = 50 \text{ MHz}$$

$$V_{max} = 2.5 \text{ V} \rightarrow \text{across C.}$$

$$V_c = IX_c = \frac{I}{\omega C}$$

$$I = V_c / \omega C$$

$$= 2.5 \times 2\pi \times 50 \times 10^6 \times 25 \times 10^{-9}$$

$$= 2.5 \times 100\pi \times 25 \times 10^{-9}$$

$$= 2.5 \times 2.5 \times \pi$$

$$I_{max} = 19.63 \text{ A}$$

$$V_{max} = I_{max} \times \frac{Z}{R^2 + (\frac{1}{\omega C})^2}$$

$$= 19.63 \sqrt{100 + \left(\frac{1}{2.5\pi}\right)^2} = 196.31 \text{ V}$$

$$= \tan^{-1} \left(\frac{314 \times 2 \phi \times 10^{-3}}{10} \right)$$

$$\boxed{\Phi = 32.12^\circ}$$

$$V = I \times Z$$

$$= I \times \sqrt{R^2 + (\omega L)^2} \sin(\omega t + \phi)$$

$$= 10 \times \sqrt{100 + (314 \times 400 \times 10^{-6})^2} \sin(314t + \phi)$$

~~$$= 10 \times 10.0006 \sin(314t + 32.12^\circ)$$~~

~~10.0006~~

$$= 10 \times 11.808 \sin(\text{"})$$

$$V = 118.08 \sin(314t + 32.12^\circ) V$$

$$\frac{100}{100+150} \cdot 50\omega C - 100 \cdot \frac{1}{\omega L} = 0$$

$$4(50C - 100L) = 100$$

$$C = 2L$$

$$\frac{1}{C} = 2L$$


$$50\omega C = \frac{100 \cdot 2L}{\omega L}$$

$$\omega^2 LC = 2$$

Laplace Transform

$$x(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt$$

(1) step function

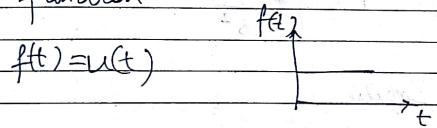

$$F(s) = \int_0^{\infty} u(t) e^{-st} dt$$

$$= -\frac{1}{s} \left[e^{-st} \right]_0^{\infty}$$

$$= -\frac{1}{s} (0 - 1) = \frac{1}{s}$$

(2) Exponential function

$$f(t) = e^{-at}$$

$$F(s) = \frac{1}{s+a}$$

(3) Sinusoidal

$$f(t) = \sin \omega t$$

$$F(s) = \frac{\omega}{s^2 + \omega^2}$$

$$\textcircled{4} \quad f(t) = \cos \omega t$$

$$F(s) = \frac{s}{s^2 + \omega^2}$$

\textcircled{5} Ramp

$$f(t) = t$$

$$F(s) = \frac{1}{s^2}$$

\textcircled{6} Impulse

$$f(t) = \delta(t)$$

$$F(s) = 1$$

\textcircled{7} Parabolic

$$f(t) = t^n$$

$$F(s) = \frac{1}{s^{n+1}}$$

$$\textcircled{8} \quad f(t) = 1 - e^{-at}$$

Find $F(s)$.

Ans.

$$F(s) = \int_{-\infty}^{\infty} e^{-st} dt - \frac{1}{s+a}$$

$\cancel{X^2 - 1}$

$$= -\frac{1}{s} (0 - 0) - \frac{1}{s+a}$$

$$= \frac{1}{s} - \frac{1}{s+a}$$

s²

q.11

Find Laplace of half cycle sine wave.

$$f(t) = \int_0^{t/2} \sin \omega t \, dt$$

$$\begin{aligned} F(t) &= \int_0^{t/2} \sin \omega t \cdot e^{-st} \, dt \\ &= \frac{\omega}{\omega^2 + s^2} \left[e^{-st/2} - 1 \right] \Big|_0^{t/2} \\ &= \frac{\omega}{\omega^2 + s^2} \left(e^{-st/2} - 1 \right) \end{aligned}$$

a t

1

$\pi/2$ π

$t/4$ $t/2$

q.12

f(t) ↑

1

0

-1

↓

T 2T 3T 4T t

$$f(t) = u(t) - 2u(t-T) + 2u(t-2T) - 2u(t-3T) + 2u(t-4T)$$

$$= \frac{1}{s} - \frac{2}{s} e^{-sT} + \frac{2}{s} e^{-2sT} - \frac{2}{s} e^{-3sT} + 2e^{-4sT}$$

$$= \frac{2}{s} \left[\frac{1}{2} - e^{-sT} + e^{-2sT} - e^{-3sT} + e^{-4sT} \right]$$

\Rightarrow ~~Q.E.D.~~

$$= \frac{1}{s} \left[1 - 2e^{-sT} (1 + e^{-sT} - e^{-2sT} + e^{-3sT}) \right]$$

T

~~A~~ s

①

V

V

s

②

I(t)

~~I(s)~~(s)

s

or

i

$\frac{I}{s}$

✓

③

R

R

④

C

1

⑤

$$V_C = 1 \int_{C}^t i dt$$

$$\frac{Cs}{Ls} I + V_0$$

⑥

L

Ls

⑦

$$V_L = L \frac{di}{dt}$$

$$L [s I(s) - i(0)]$$

Q.

$$\frac{10^4}{s(s+250)}$$

Find L^{-1}

$$= 10^4 \left[\frac{1}{s} - \frac{1}{s+250} \right]$$


$$\Rightarrow \frac{10^4}{s(s+250)} = \frac{A}{s} + \frac{B}{s+250} \quad (1)$$

- Partial fraction

HW → 9.18, 9.19, 9.23 =

Page No. _____
Date _____

Step Response in R-C & R-L

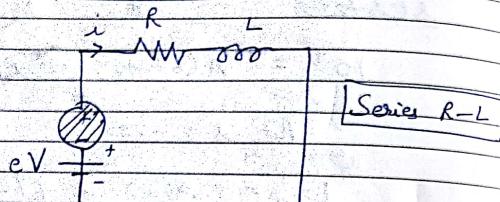

$$\text{Ques} \# 14 \quad e_{ul}(t) = iR + L \frac{di}{dt}$$

Applying L.T.

$$\frac{e}{s} = I(s) \cdot R + L [sI(s) - I(0)]$$

$$\frac{e}{s} = I(s)R + LsI(s) - LI(0)$$

$$I(s)[R + LS] = \frac{e}{s} + LI(0)$$

$$I(s) = \frac{e}{s(R+Ls)} + \frac{LI(0)}{R+Ls}$$

$$I(s) = \frac{e}{s(R+Ls)}$$

$$= \frac{e}{s(R+Ls)/L}$$

$$\frac{1}{s(Cs+a)} = a + \frac{1}{s} e^{-at}$$

Page No. _____
Date _____

$$I(s) = \frac{e}{L} \frac{1}{s(R+s)}$$


$$= \frac{A}{s} + \frac{B}{s(R+s)} = \frac{e}{L} \frac{1}{s(L+s)}$$

$$= \frac{R \times E}{R+s} \quad A = \frac{E}{R} \quad B = -\frac{E}{R}$$

$$V(t) = E - \frac{E}{R} e^{-\frac{t}{L}}$$

$$V = \frac{E}{R} e^{-\frac{t}{L}}$$

9.22

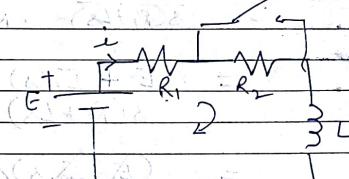

$$E = 10 \text{ V} \quad R_1 = 1 \Omega$$

$$L = 1 \text{ H} \quad R_2 = 2 \Omega$$

$$i = 1 \text{ A}$$

Ques # 15

$$+ E + iR_1 + iR_2 - i \cdot \frac{L di}{dt} = 0$$

$$E u(t) = i R_1 + L \frac{di}{dt}$$

$$\frac{E}{s} = I(s) \cdot R_1 + L [s I(s) - I(0)]$$

$$\frac{E}{s} = I(s) R_1 + L s I(s) - \underline{I(0)}$$

$$I(s) [R_1 + Ls] = \frac{E}{s} + \underline{\frac{I(0)}{R_1 + Ls}}$$

$$I(s) = \frac{E}{s(R_1 + Ls)} + \frac{I(0)}{R_1(R_1 + Ls) R_2(R_1 + Ls)}$$

$$I(s) = \frac{E}{s(R_1 + Ls)} + \frac{L I_0}{R_1 + Ls}$$

$$= \frac{E + I_0(s)}{s(R_1 + Ls)}$$

$$= \frac{(E + I_0 s)/L}{s(\frac{R_1}{L} + s)}$$

$$I(s) = \frac{E}{s} + \frac{I_0 \cdot s}{s(\frac{R_1}{L} + s)}$$

$$= \frac{A}{s} + \frac{B}{s(\frac{R_1}{L} + s)}$$

$$\frac{s(R_1 + Ls)}{s(\frac{R_1}{L} + s)} = \frac{R_1}{L} + s$$

Put $s = 0$,

$$\cancel{R_1} - 0 = A + \frac{BL}{R_1}$$

(*)

$$\frac{E + I_0 s}{s} = A + \frac{Bs}{R_1 + s} \quad | \cdot L$$

Put $s = 0$,

$$\cancel{R_1} - 0 = 2A$$

$$\frac{E \times L}{R_1} = A$$

$$A = \frac{E}{R_1} = 10$$

$$\textcircled{1} \times \left(\frac{R}{L} + s \right)$$

$$\Rightarrow \frac{E}{L} + I_0 \cdot s = \frac{A}{s} \cdot \left(\frac{R}{L} + s \right) + B$$

Put $s = -R/L$

$$\frac{E - I_0 \left(\frac{R}{L} \right)}{L} = A(0) + B$$

$$\Rightarrow B = -\left(\frac{E - I_o}{R}\right)$$

$$B = -\left(\frac{E - I_o}{R_1}\right)$$


$$= -\left(10 - \frac{10}{3}\right)$$

~~(R. 29)~~

$$B = -6.67$$

$$I(t) = \frac{10}{s} + \frac{(-6.67)}{s+1}$$

$$= 10 u(t) - 6.67 e^{-st}$$

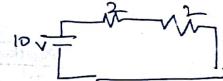

$$I = \frac{10}{2} + \frac{10}{2} = 5 + 5 = 10 A$$

$$I = 10 = 2.5 A$$

9.18

$$f(s) = \frac{50}{s^2 + 2s + 2}$$

$$= \frac{50}{(s+1)^2 + 1^2}$$

$$f(t) = 50 e^{-t} \sin t$$

9.19

$$I(s) = \frac{s+1}{s(s^2 + 4s + 4)}$$

$$= \frac{s+1}{s(s+2)^2}$$

$$\frac{s+1}{s(s+2)^2} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{(s+2)^2} \quad (1)$$

(X)

$$\frac{s+1}{(s+2)^2} = \frac{A}{s} + \frac{Bs}{s+2} + \frac{Cs}{(s+2)^2}$$

Put s = 0

$$A = \frac{1}{4}$$

$$\textcircled{1} \quad \times (s+2)^2$$

$$\Rightarrow \frac{s+1}{s(s+2)} = \frac{A(s+2)^2 + B(s+2) + C}{s(s+2)}$$

$$\frac{s+1}{s} = \frac{A(s+2)^2}{s} + \frac{B(s+2)}{s} + \frac{C}{s+2}$$

$$\text{Put } s = -2$$

$$A(0) + B(0) + C = \frac{-1}{2}$$

$$\Rightarrow C = \frac{1}{2}$$

$$\frac{s+1}{s(s+2)} = \frac{A(s+2)}{s} + \frac{B}{s+2} + \frac{C}{s}$$

$$\text{Putting } A, C, \& s = -2$$

$$\frac{2}{3} = \frac{3}{4} + B + \frac{1}{6}$$


$$B + \frac{11}{12} = 2$$

$$B = \frac{2}{3} - \frac{11}{12} = \frac{8-11}{12} = \frac{-3}{12}$$

$$B = -\frac{1}{4}$$

$R(t)$
 $R I(s)$

Eq. 24

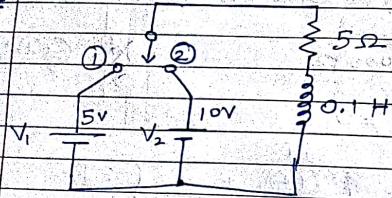

$$10 = 5i + 0.1 \times \frac{di}{dt}$$

Applying L.T.,

$$\frac{10}{s} = 5I(s) + 0.1s[sI(s) - I(0)]$$

$$\frac{10}{s} = 5I(s) + 0.1sI(s) - 0.1I(0)$$

$$\frac{5}{0.1}$$

$$I(s)[5 + 0.1s] = \frac{10}{s} + 0.1I(0)$$

$$I(s) = \frac{(10/s) + 0.1I(0)}{5 + 0.1s}$$

$$= \frac{100/s + I(0)}{50 + s}$$

$$= \frac{100 + sI(0)}{s(s + 50)}$$

$$= \frac{100 + s}{s(s + 50)}$$

Page No. _____
Date _____

Page No. _____
Date _____

Ex 14

$$\frac{100 + s}{s(s + 50)} = \frac{A}{s} + \frac{B}{s + 50}$$

$$\frac{100 + s}{s(s + 50)} = \frac{A(s + 50) + sB}{s(s + 50)}$$

$$A(s + 50) + B(s) = 100 + s$$

$$\text{Put } s = 0,$$

$$A(50) + B(0) = 100$$

$$\Rightarrow A = 2$$


$$\text{Put } s = -50,$$

$$A(0) + B(-50) = 50$$

$$\Rightarrow B = -1$$

$$I(t) = 2 \cdot 2U(t) - e^{-50t}$$

E9.27

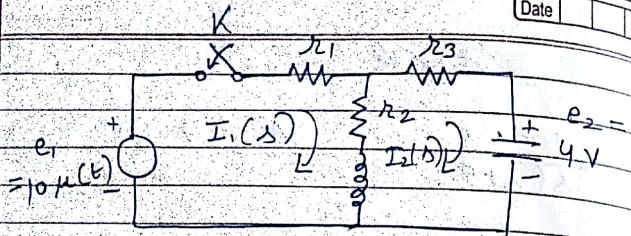

$$r_1 = r_2 = r_3 = 1\Omega$$

$$L = 1H$$

$$C = 1F$$

$$c_1 = r_1(I_1(t))$$

$$+ r_2(I_1(t) - I_2(t))$$

$$+ L \frac{d(I_1 - I_2)}{dt}$$

$$\textcircled{1}$$

$$+ e_2 + r_3 I_2(t) + r_2(I_2(t) - I_1(t))$$

$$+ L \frac{d(I_2 - I_1)}{dt} + \frac{1}{C} \int I_2 dt = 0$$

$$\textcircled{2}$$

Applying L.T. on $\textcircled{1}$ & $\textcircled{2}$,

$$\frac{c_1}{s} = r_1 I_1(s) + r_2(I_1(s) - I_2(s))$$

$$+ L[sI_1(s) - I_1(0)]$$

$$- (sI_2(s) - I_2(0))$$

$$-\frac{e_2}{s} = r_3 I_2(s) + r_2(I_2(s) - I_1(s))$$

$$+ L[(sI_2(s) - I_2(0)) - (sI_1(s) - I_1(0))]$$

$$+ \int I_2 + v_0$$

Page No. _____
Date _____

Page No. _____
Date _____

$$\frac{c_1}{s} = r_1 I_1(s) + r_2 I_1(s) - r_2 I_2(s)$$

$$+ L s I_1(s) - L s I_1(0) - L s I_2(s) + L I_2(s)$$

~~$I_1(s)$~~

$$\frac{10}{s} = I_1(s) + I_1(s) - I_2(s) + s I_1(s)$$

$$- s I_1(0) - s I_2(s) + I_2(s)$$

$$\frac{10}{s} = s I_1(s) [2+s] - I_2(s) [1+s]$$

$$I_1(s) [2+s] = I_2(s) [1+s] + \frac{10}{s}$$

$$\frac{4}{s} + I_2(s) + I_2(s) - I_1(s) + s I_2(s)$$

$$- s I_1(s) + \frac{I_2}{s} = 0$$

$$I_1(s) [1+s] - I_2(s) [2+s] + \frac{1}{s}$$

$$= \frac{4}{s} + \frac{I_2}{s}$$

$$I_1(s) = I_2(s) \left(\frac{1+s}{2+s} \right) + \frac{10}{s(2+s)}$$

$$I_2(s) \left[\frac{(1+s)}{2+s} + \frac{10}{s(2+s)} - \frac{I_2(s)}{2+s} \right] = 4$$

$$\Rightarrow I_2 \left[\frac{s+1}{s+2} + \frac{10}{s(s+2)} - \left(\frac{s+1}{s+2} \right)^2 \right] = \frac{4}{s}$$

$$\Rightarrow I_2 \left[\frac{s(s+1)+10 - s^2 - 2s + 1}{s(s+2)} \right] = 4$$

$$\Rightarrow I_2 \left[\frac{s^2 + s + 10 - (s^2 + 2s + 1)(s+2)}{s(s+2)} \right] = 4$$

$$\Rightarrow I_2 \left[\frac{s^2 + s + 10 - (s^3 + 2s^2 + 2s^2 + 4s + s + 2)}{s+2} \right] = 4$$

$$\Rightarrow I_2 \left[\frac{-s^3 - 3s^2 - 4s + 8}{s+2} \right] = 4$$

$$I_2 = -4 / \left(\frac{s^3 + 3s^2 + 4s - 8}{s+2} \right)$$

$$I_2 = \frac{-4(s+2)}{s^3 + 3s^2 + 4s - 8}$$

$$\boxed{\begin{aligned} s &= -1 \\ s &= -2 + 2i \\ s &= -2 - 2i \end{aligned}}$$